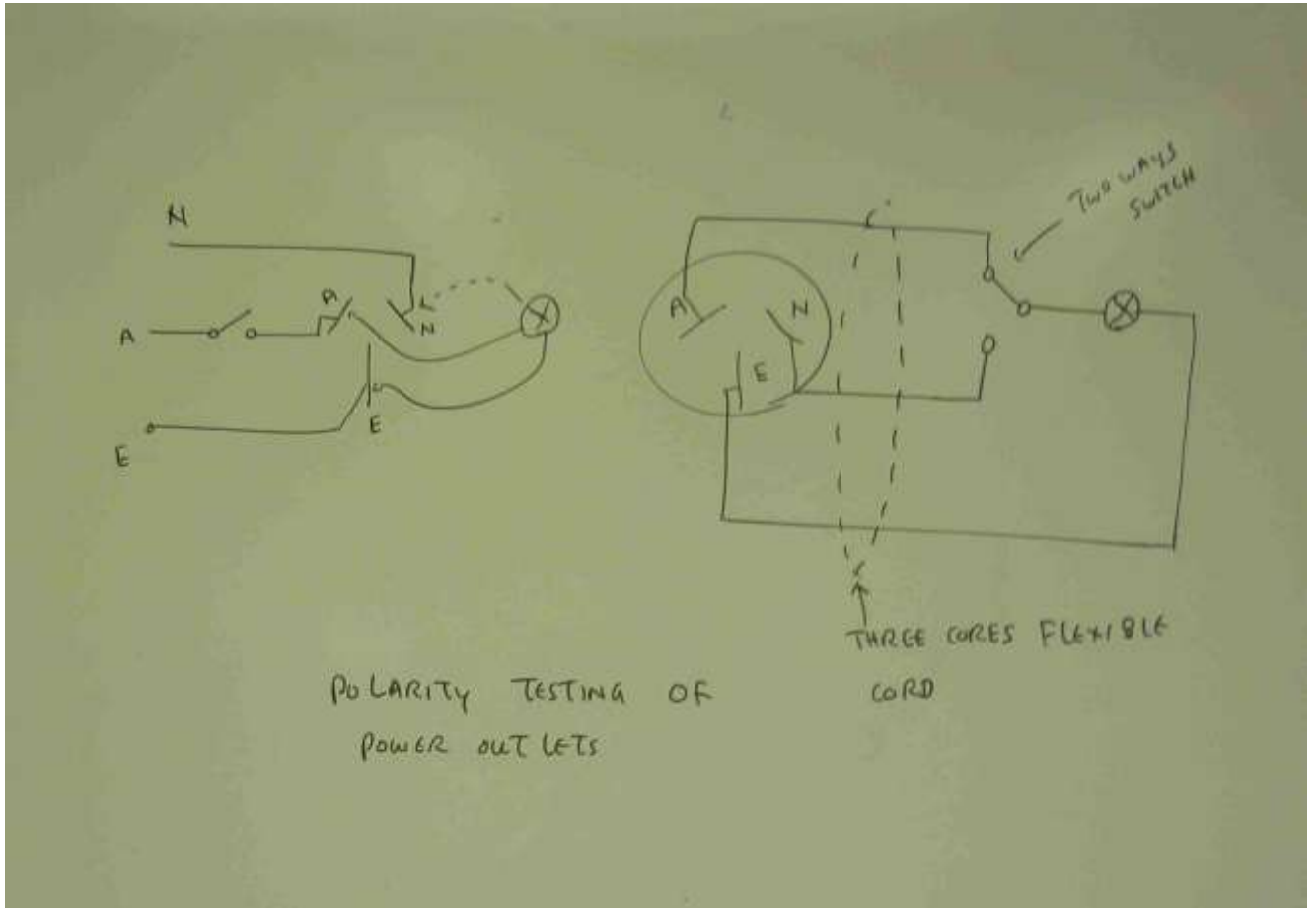


## Advanced Wiring


### Practical (1) Electrical Installation Safety Testing



Perform Electrical Safety Testing on given switch board by applying the standard safety test procedures






POLARITY TESTING OF POWER OUTLETS

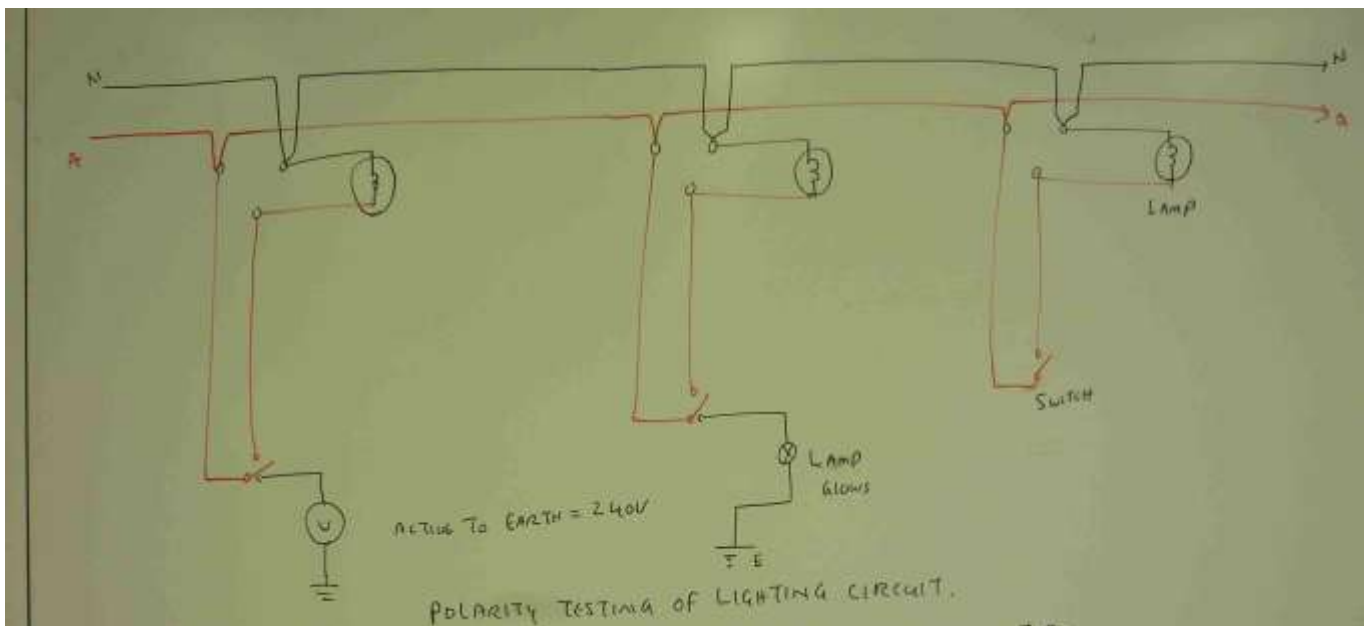

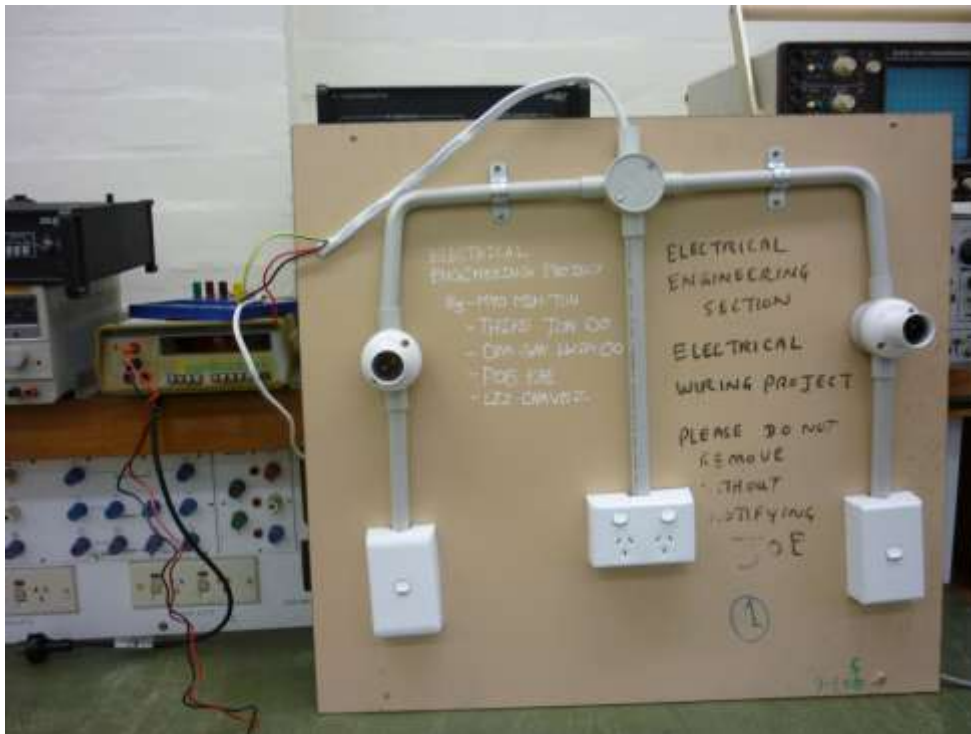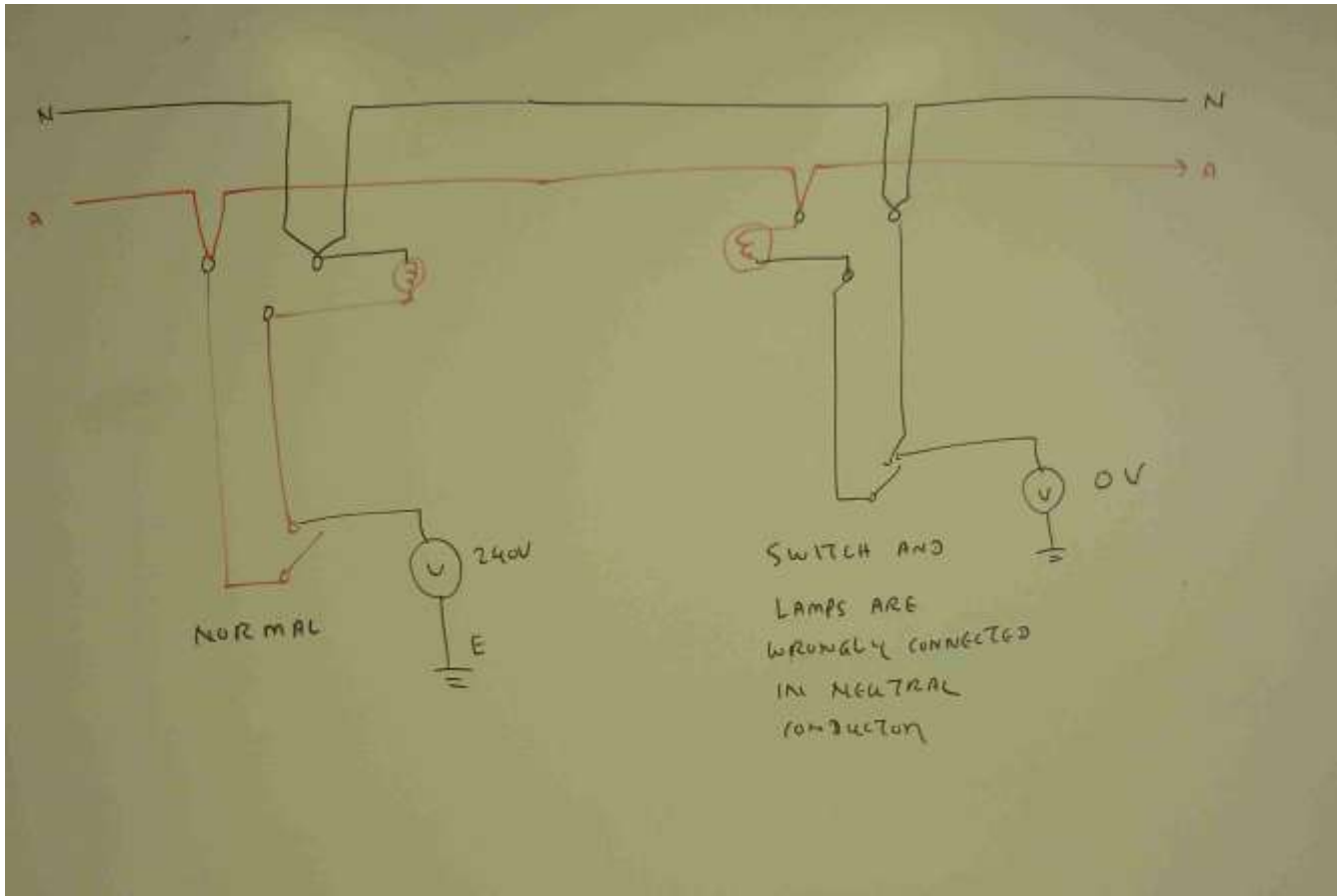
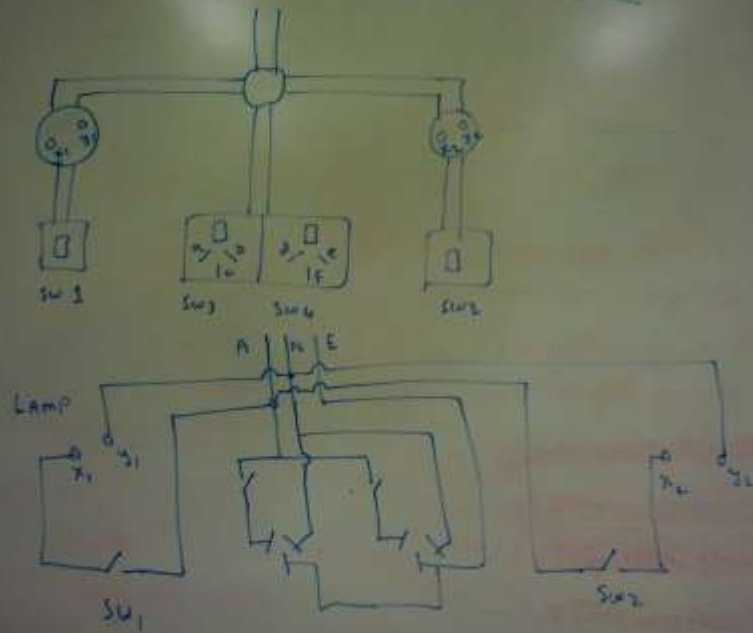
### ELECTRICAL WIRING CIRCUIT ASSEMBLY AND TESTING (1)



PROCEEDURE

1. Connect the

2. Switch 1

SW<sub>1</sub> ON

SW<sub>1</sub> OFF

SWITCH 2

SW<sub>2</sub> ON

SW<sub>2</sub> OFF

PROCEDURE

① CONNECT THE WIRE TO SUPPLY


② SWITCH 1

		VOLTAGE
SW <sub>1</sub> ON	X <sub>1</sub> → GROUND X <sub>2</sub> → GROUND	
SW <sub>1</sub> OFF	X <sub>1</sub> → GROUND X <sub>2</sub> → GROUND	

SWITCH 2

		VOLTAGE
SW <sub>2</sub> ON	X <sub>1</sub> - GROUND X <sub>2</sub> - GROUND	
SW <sub>2</sub> OFF	X <sub>1</sub> - GROUND X <sub>2</sub> - GROUND	

SW<sub>3</sub> & SW<sub>4</sub>

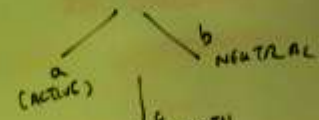


SW<sub>3</sub> ON -

VOLTAGE BETWEEN		VOLT
a - b		
b - c		
c - a		

SW<sub>3</sub> OFF


VOLTAGE BETWEEN		VOLT
a - b		
b - c		
c - a		

ALSO REPEAT FOR SWITCH 4

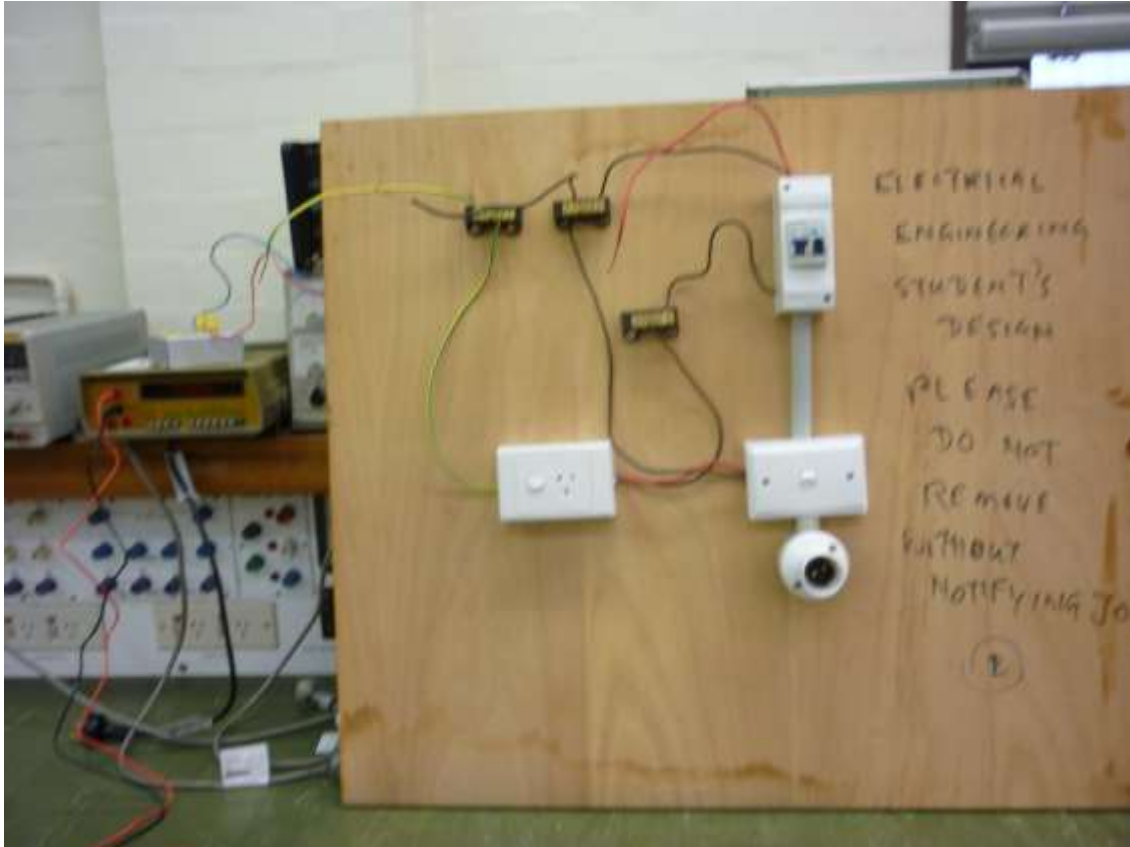


## ELECTRICAL WIRING OUTLET ASSEMBLY AND TESTING (3)

## PHYSICAL DIAGRAM

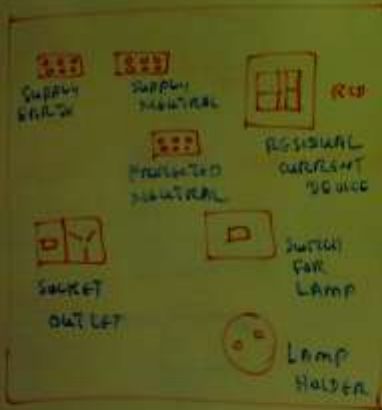

## WIRING DIAGRAM

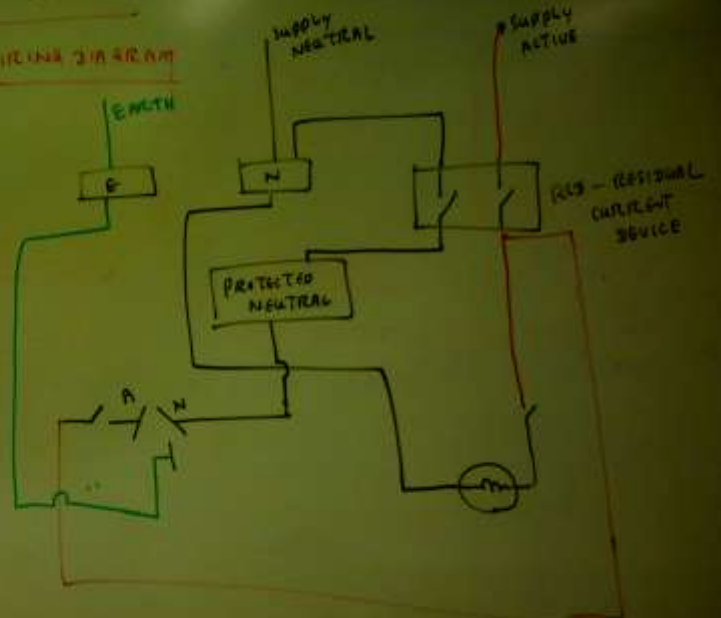

PLY  
THE

MEASURE THE RESISTANCE VALUE

RCD IS ON

THE RESISTANCE BETWEEN LAMP ACTIVE  
AND SUPPLY ACTIVE \_\_\_\_\_ Ω

- THE RESISTANCE BETWEEN LAMP NEUTRAL  
AND SUPPLY NEUTRAL \_\_\_\_\_ Ω

- THE CONNECTION BETWEEN SUPPLY  
NEUTRAL AND PROTECTED NEUTRAL  
CONNECT | DISCONNECT

- THE CONNECTION BETWEEN SOCKET OUTLET  
NEUTRAL AND SUPPLY NEUTRAL

RCD IS OFF

- THE RESISTANCE BETWEEN LAMP ACTIVE  
AND SUPPLY ACTIVE \_\_\_\_\_ Ω

- THE RESISTANCE BETWEEN LAMP NEUTRAL  
AND SUPPLY NEUTRAL \_\_\_\_\_ Ω

- THE CONNECTION BETWEEN SUPPLY NEUTRAL  
AND PROTECTED NEUTRAL CONNECT | DISCONNECT.


RCD - RESIDUAL  
CURRENT  
DEVICE


CONNECT THE CIRCUIT TO SUPPLY


RCD ON	VOLTAGE
	A - N
	A - E
	N - E
RCD OFF	A - N
	A - E
	N - E

THE CONNECTION BETWEEN  
SOCKET OUTLET NEUTRAL  
AND SUPPLY NEUTRAL  
CONNECT | DISCONNECT.





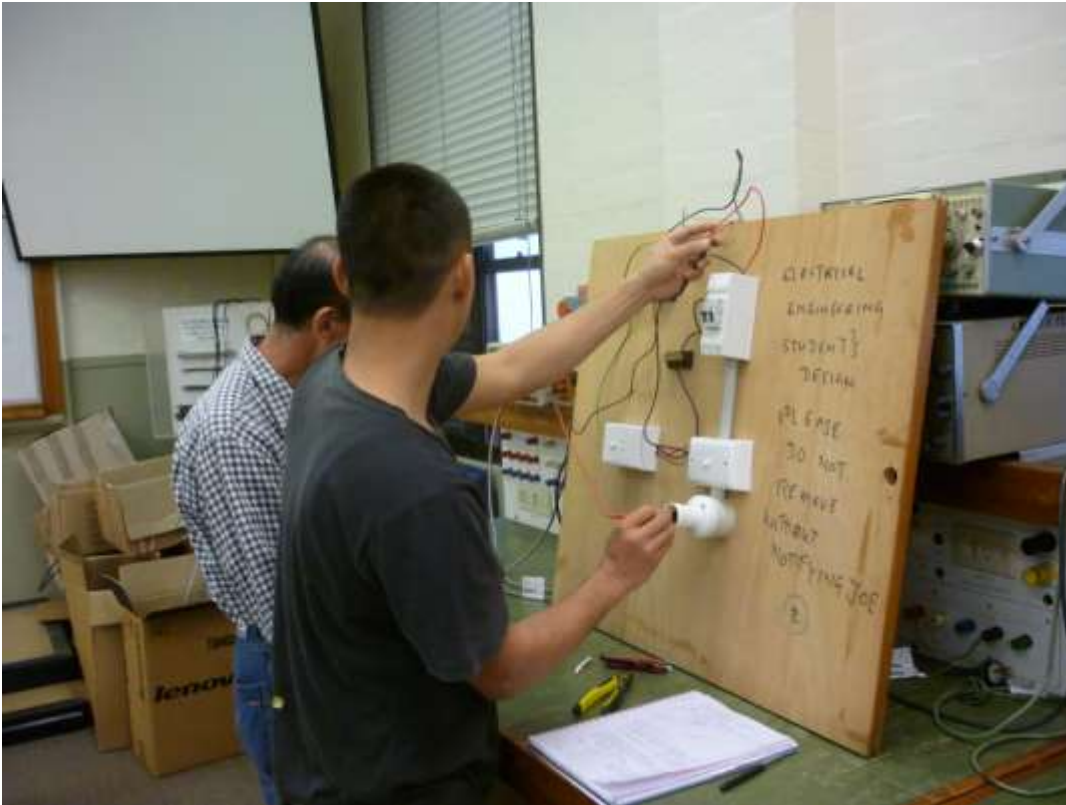


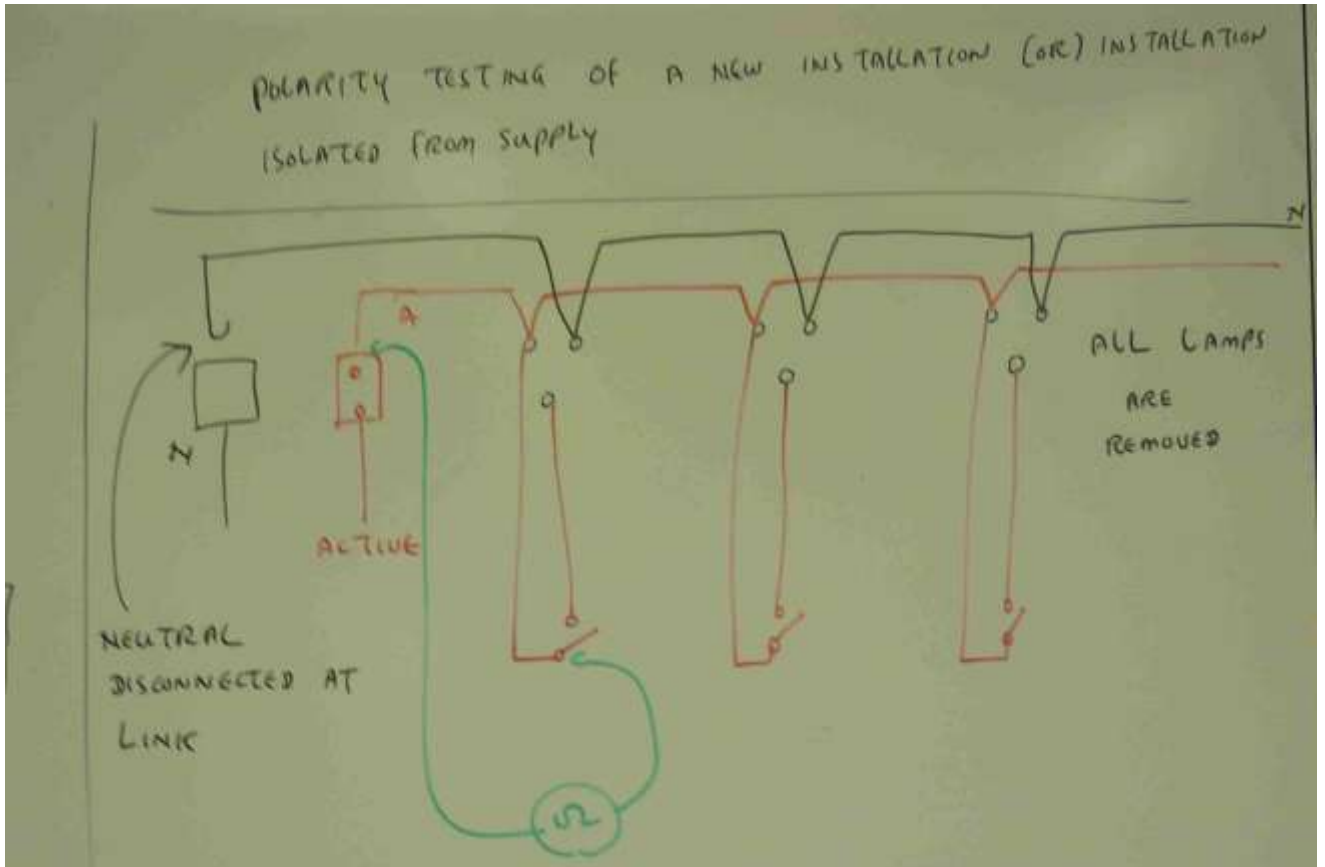


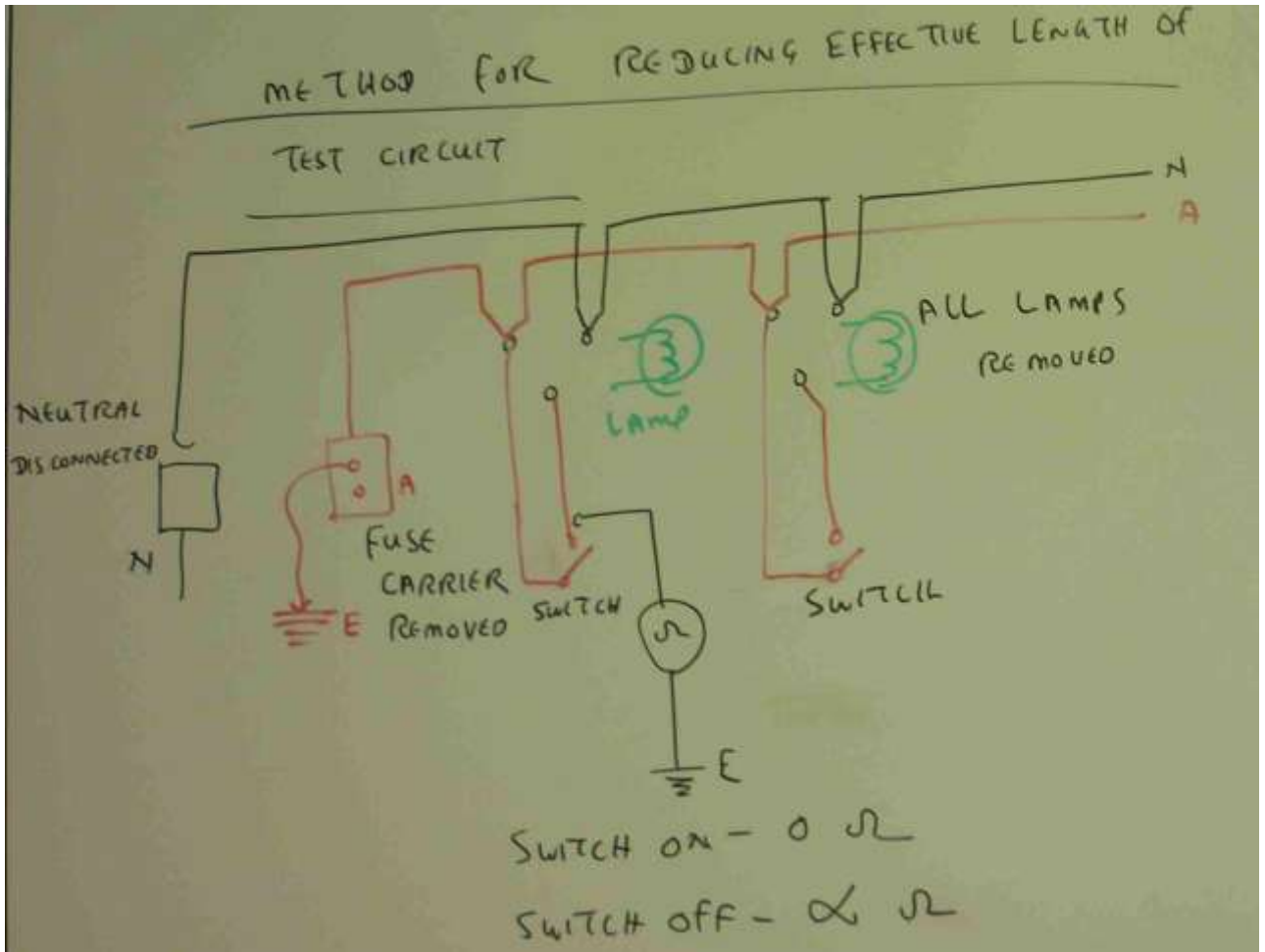




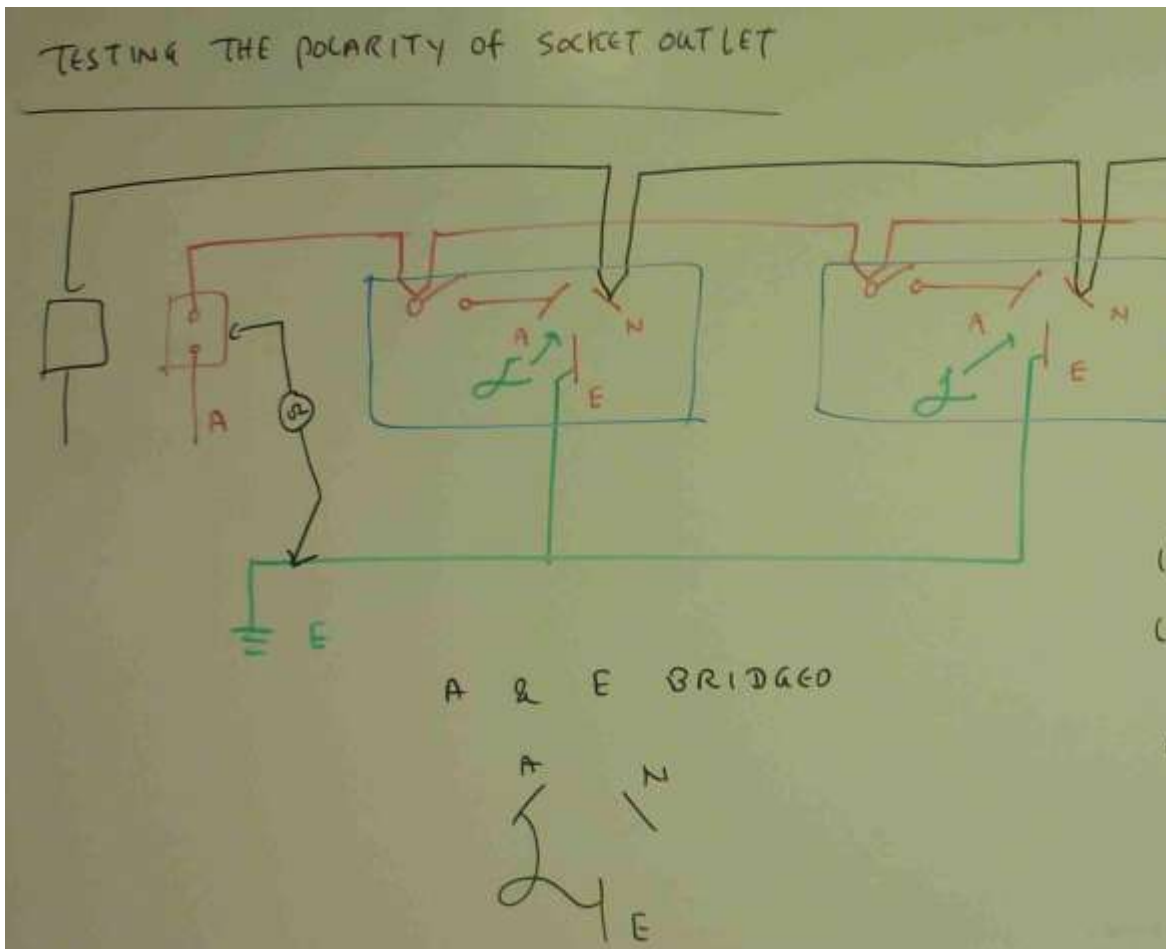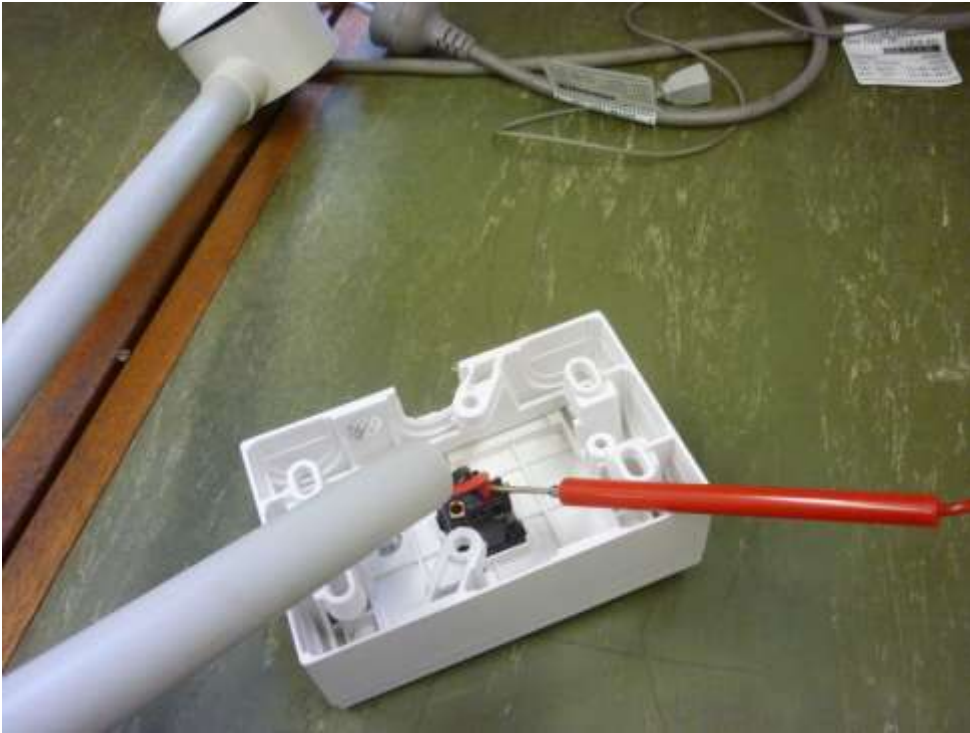


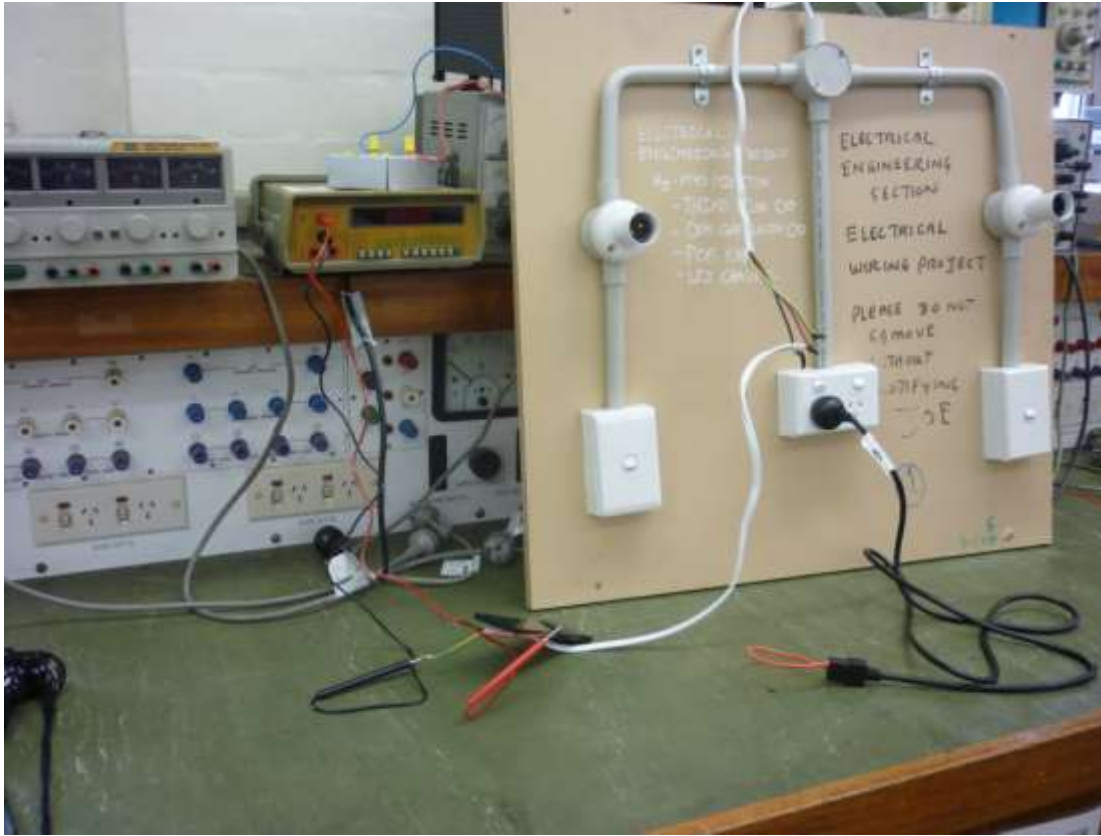


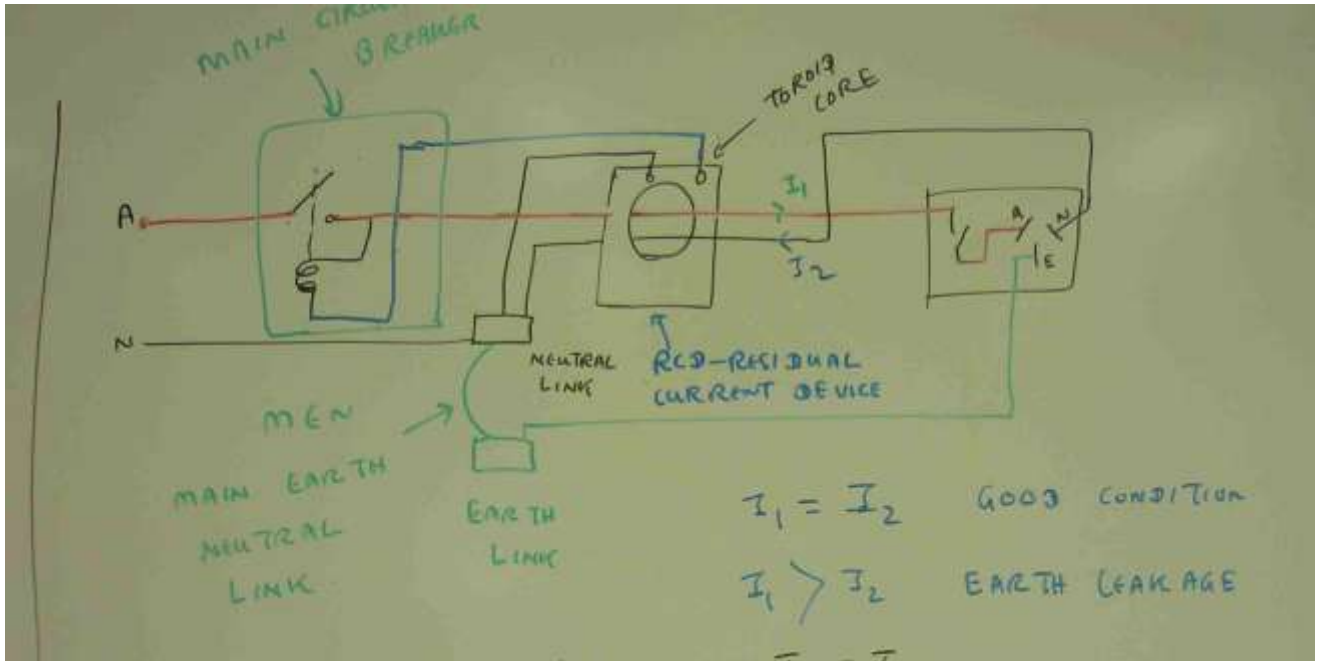


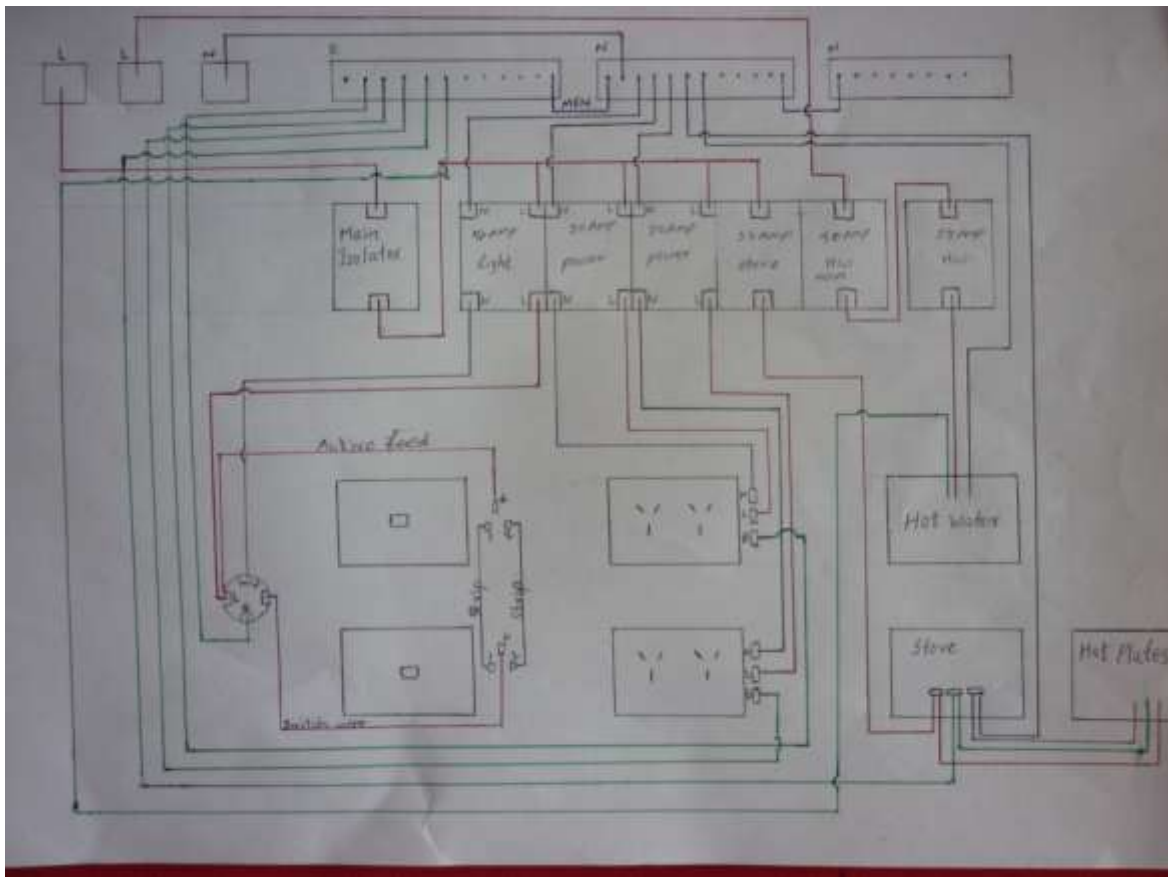Trace the following circuit connection diagram on the switch board.



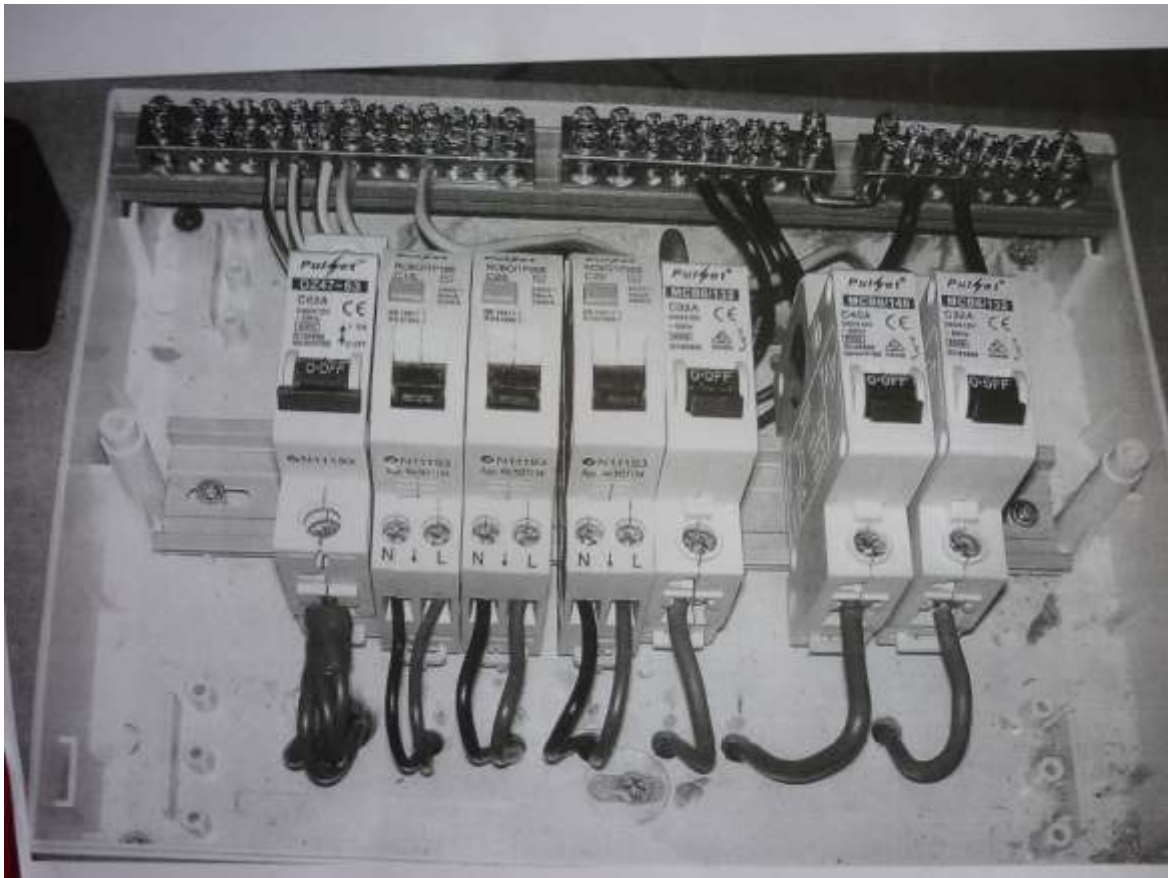



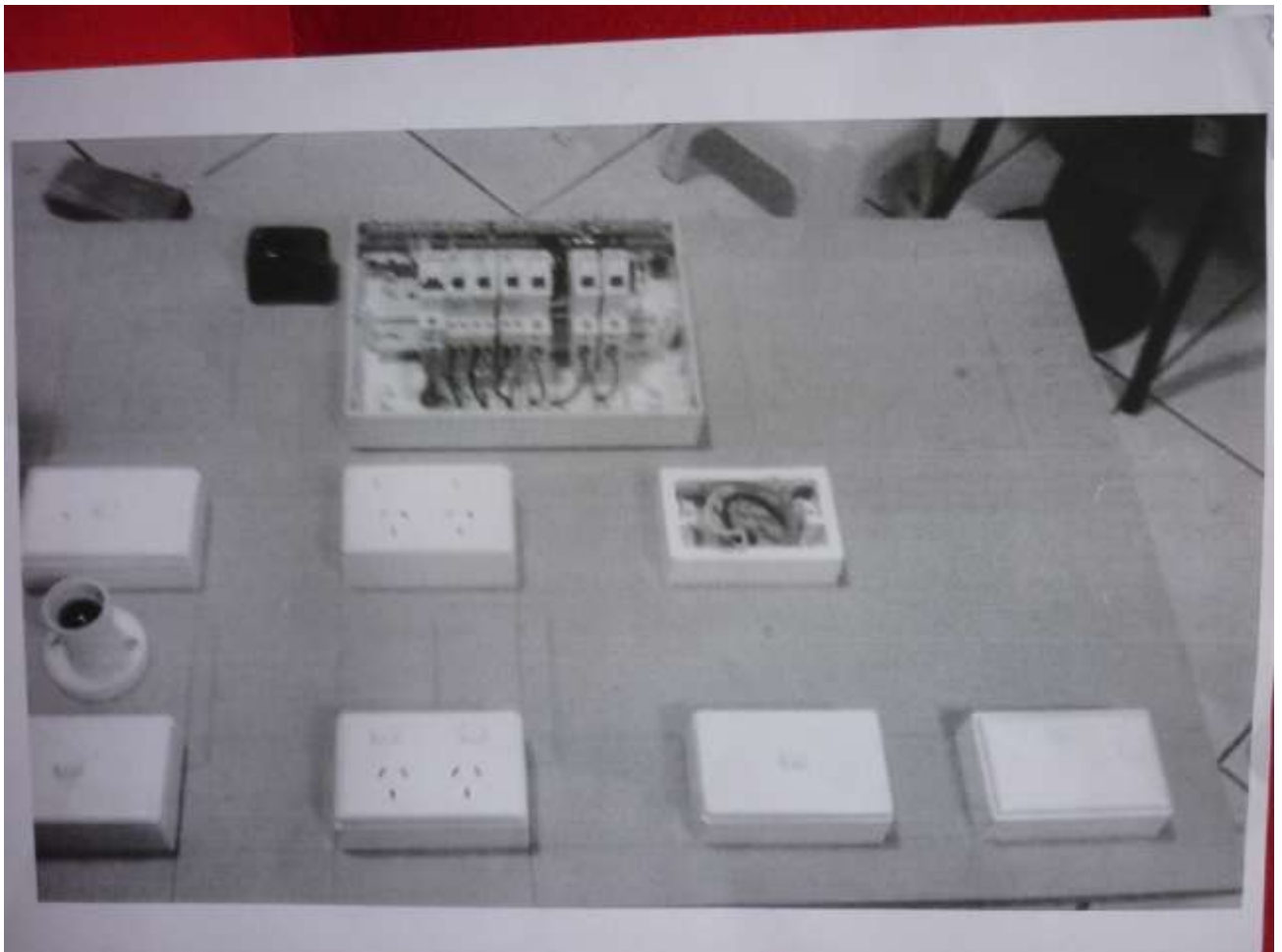
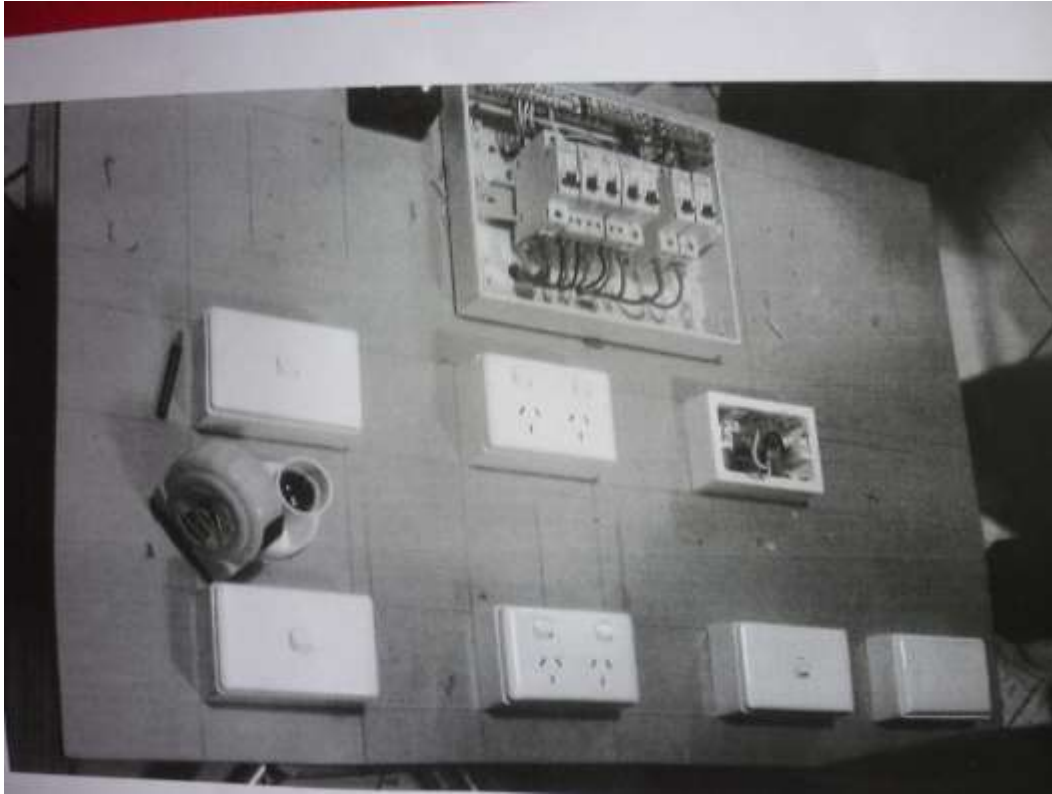





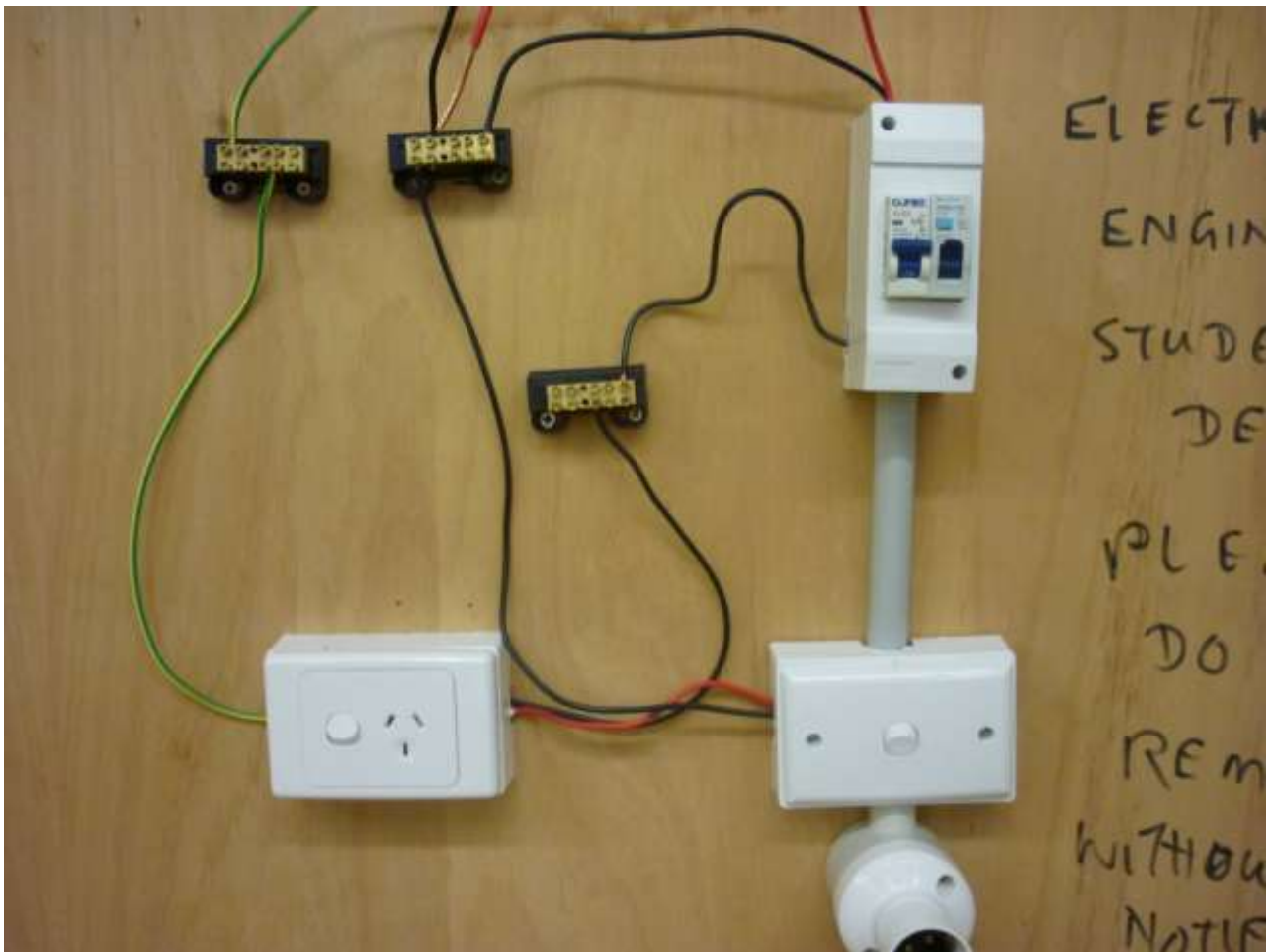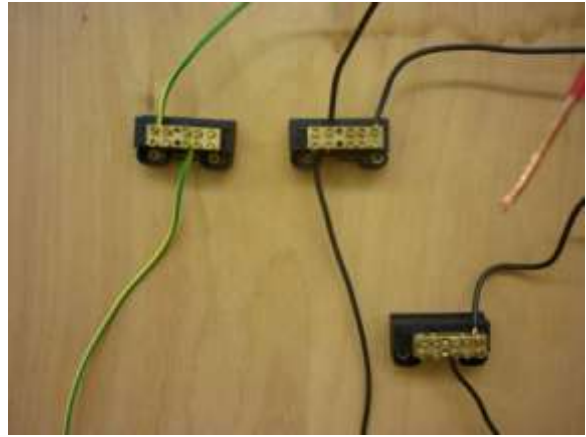
### Practical (2) RCD Protected & Unprotected neutral

Test, trace the circuit and sketch the circuit diagram for the given RCD, protected and unprotected neutral






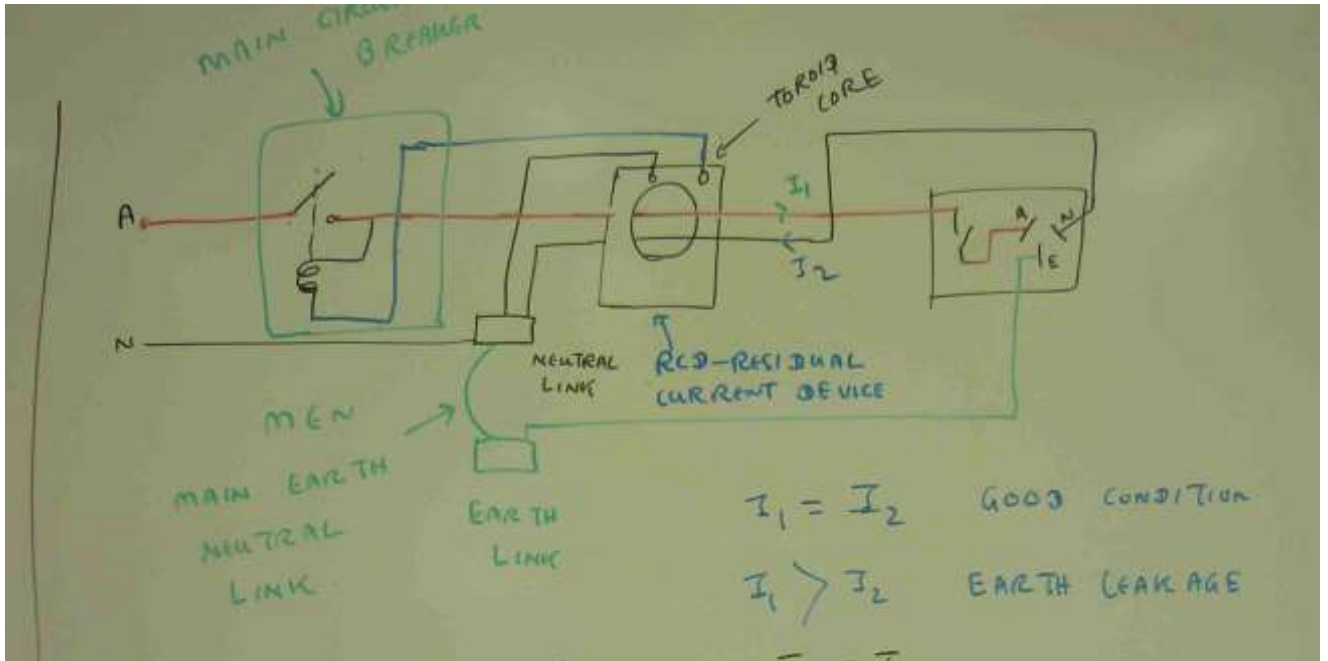

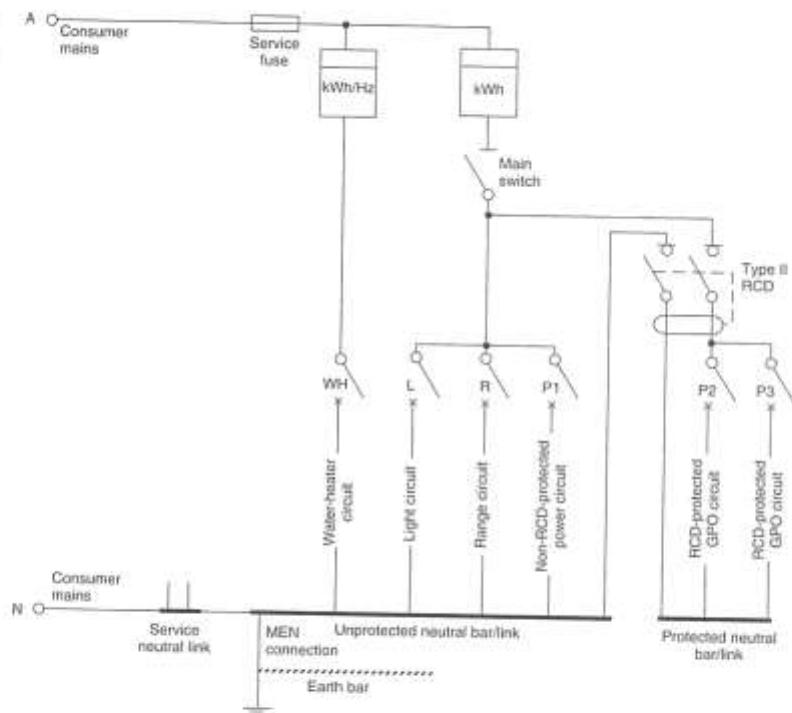

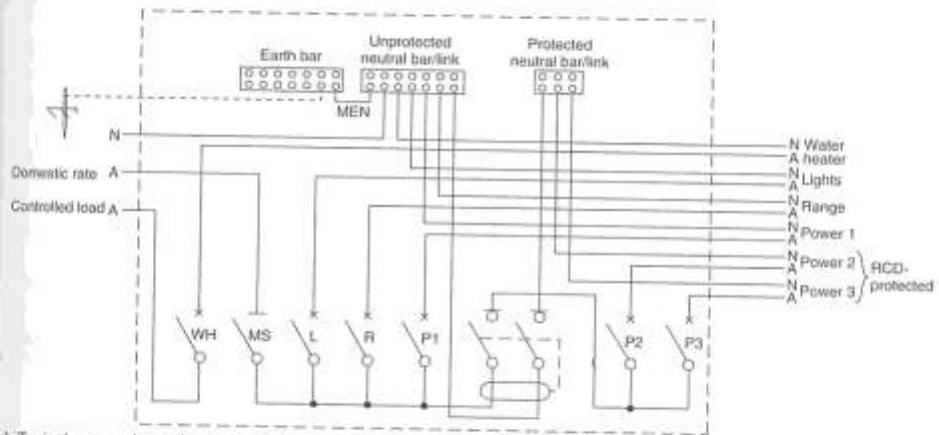(a) Typical installation circuit arrangement



(b) Typical compact switchboard wiring arrangement

**Fig. 14.14** Distribution arrangement in a single domestic dwelling for protection of two power circuits using one 2-pole RCD. Note the separate neutral bars/links for RCD-protected and non-protected portions of the installation

ected by a type II 30 mA device. The protection should be separate from any other circuit to avoid faults plunging the whole installation into darkness.

Circuits supplying equipment in spa or pool areas are usually protected adequately by type II 30 mA devices, as long as heating elements are not involved.

Figure 17.4 in Chapter 17 shows a switchboard equipped to provide RCD type IV as the main switch, RCD/MCB type II for pool area and RCD type II for two power circuits. The switchboard comes fitted with an earth bar and an unprotected neutral bar with terminals for the main earth, main neutral and MEN


2D-  
Needed


y the  
cr the

bath-  
e pro-
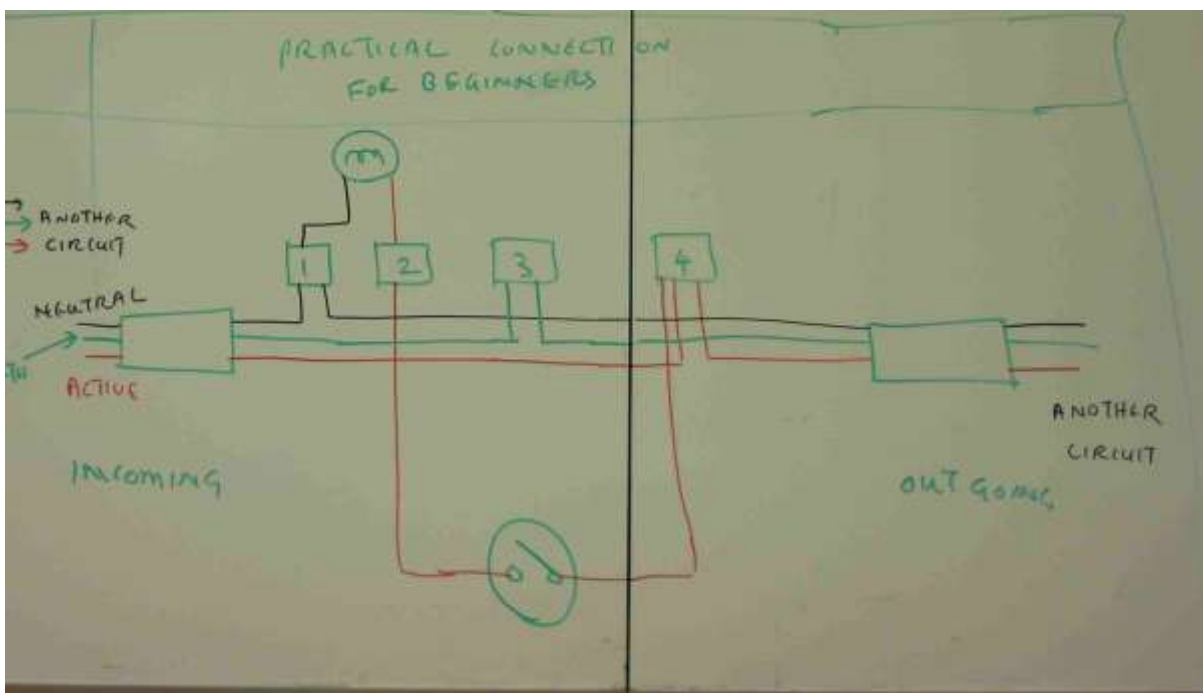
### Practical (3) Light + Socket outlet Wiring


Dismantle & reassemble the following light & socket outlet wiring system.




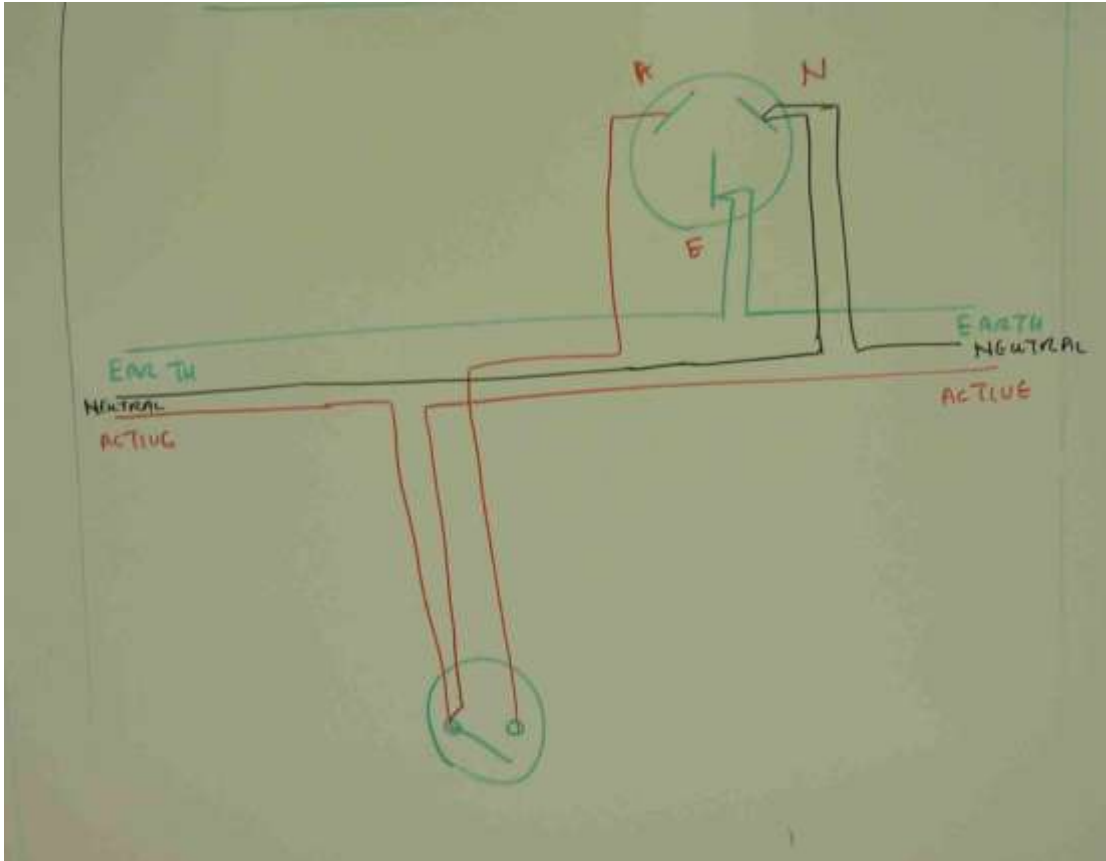
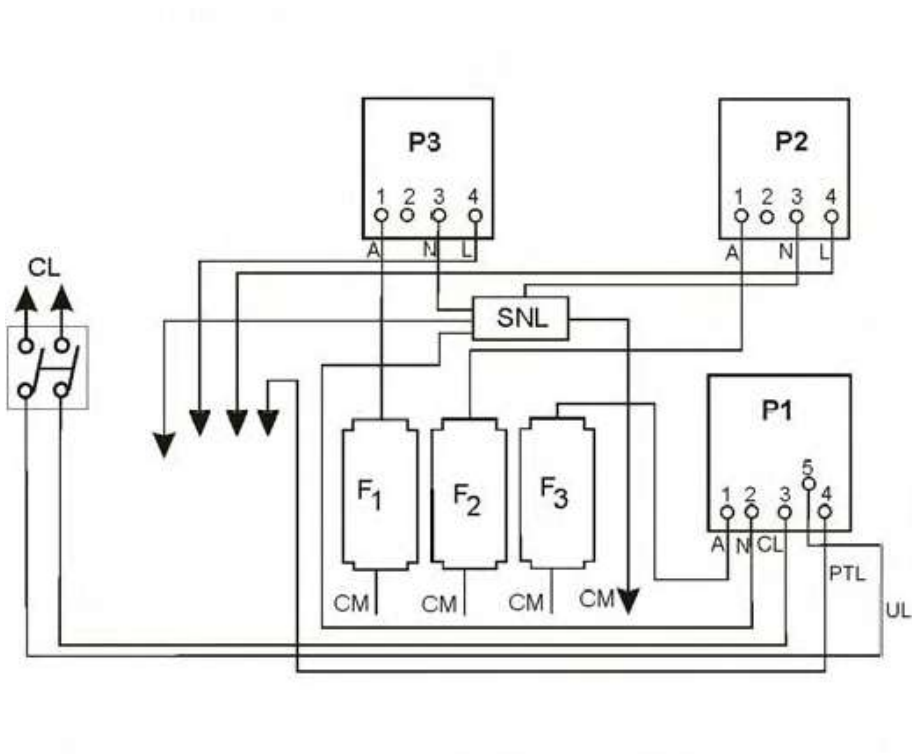
#### Practical (4) Power supply metering system

Trace the given metering control system on given assemble board.





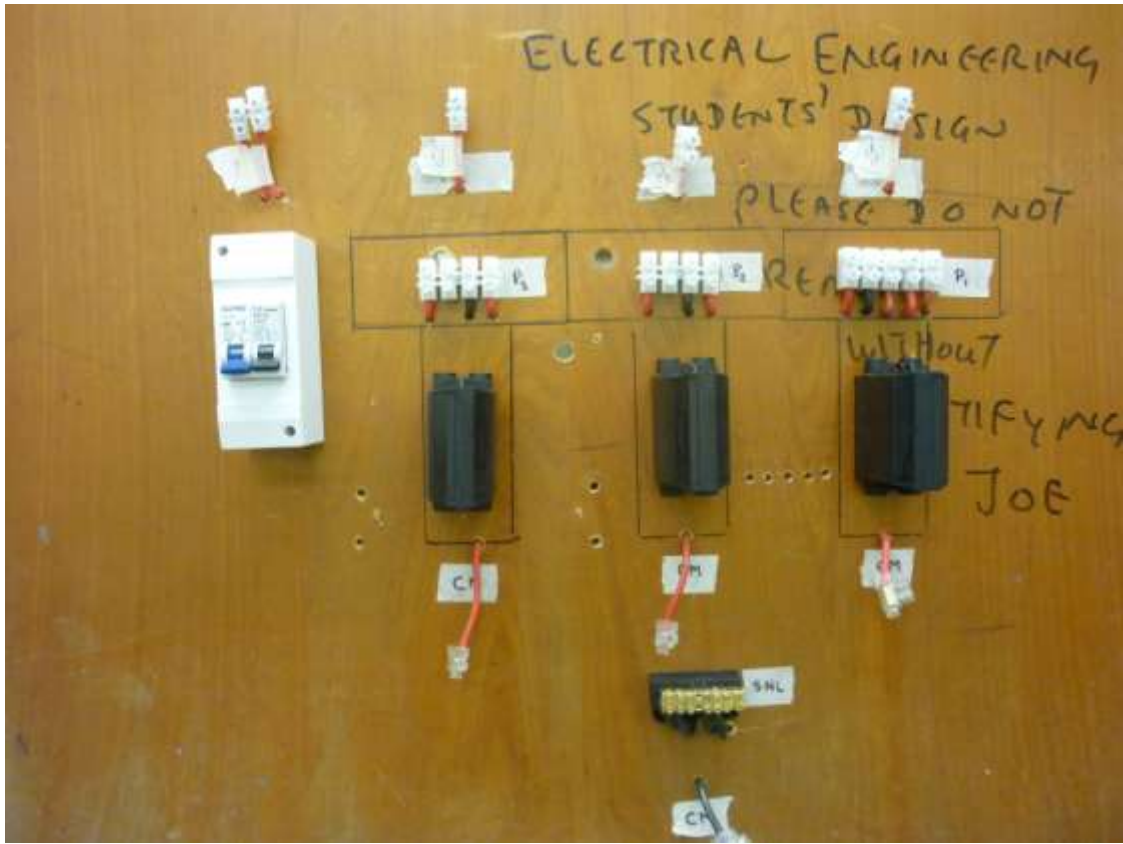



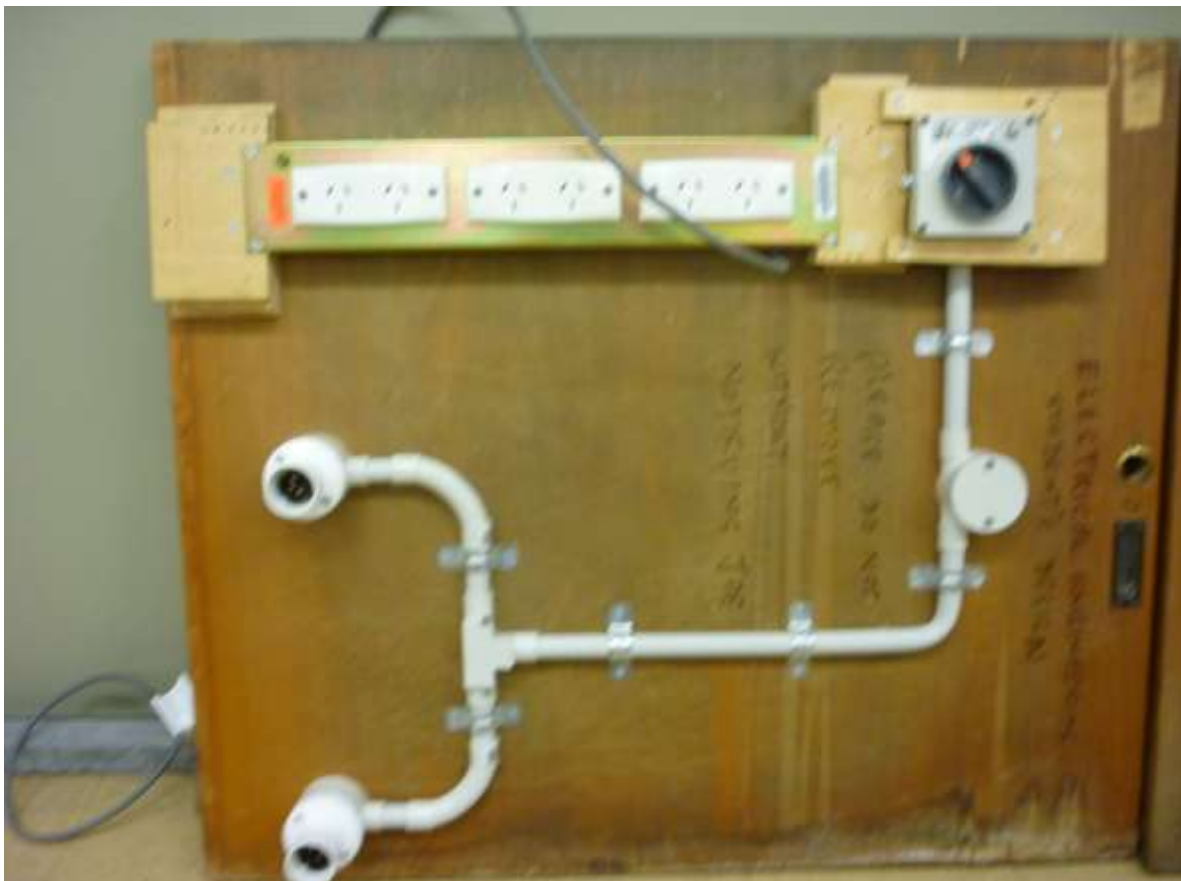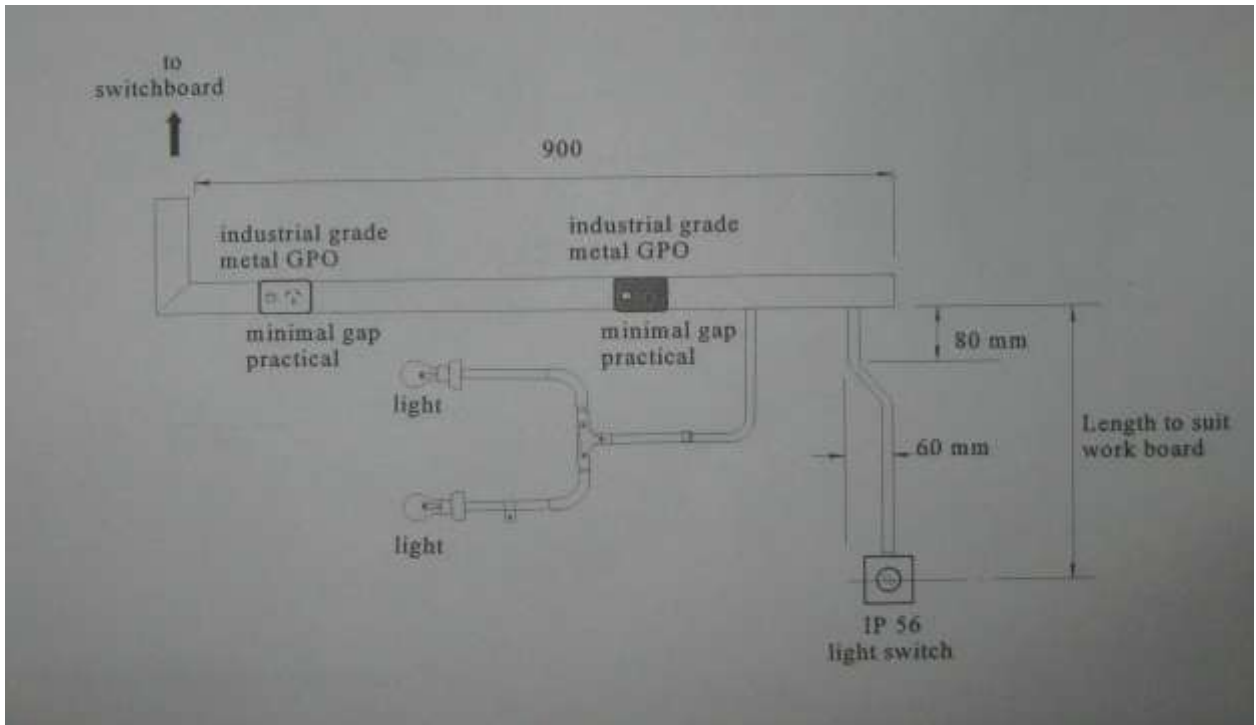
**Practical (5) Modification of design diagram to do the actual assembly**

Trace the following wiring assembly on the given wiring board. The given drawing is just an outline. The actual assembly is different from it. Sketch the actual assembly diagram & circuit diagram.



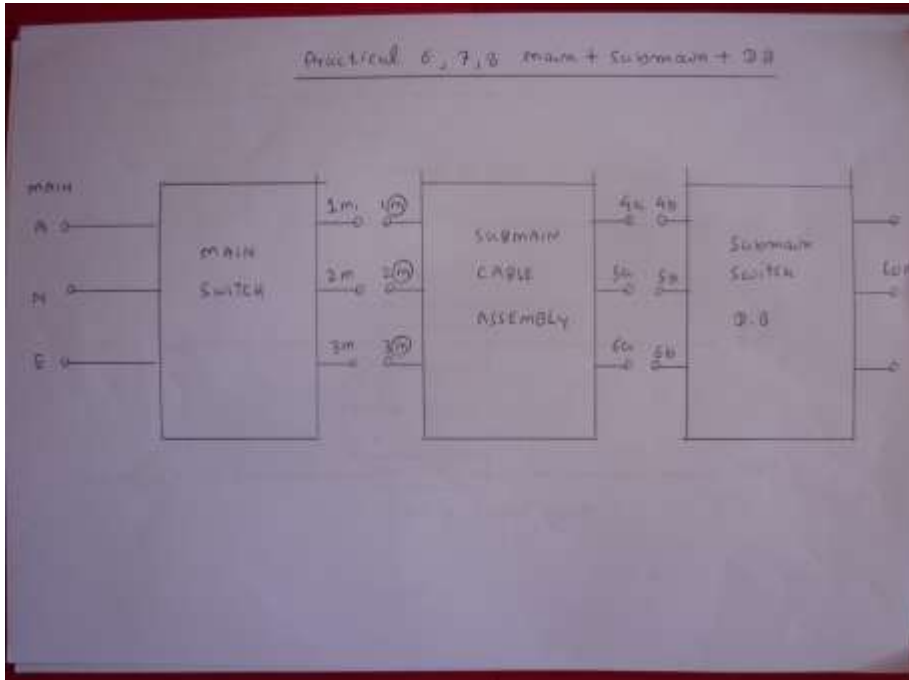
### Practical (6,7,8) Main, Sub-main & Distribution Board Wiring

Wire the main, sub-main and distribution board wiring by using the following circuit diagrams (OR) Trace the circuit & draw the circuit diagram.




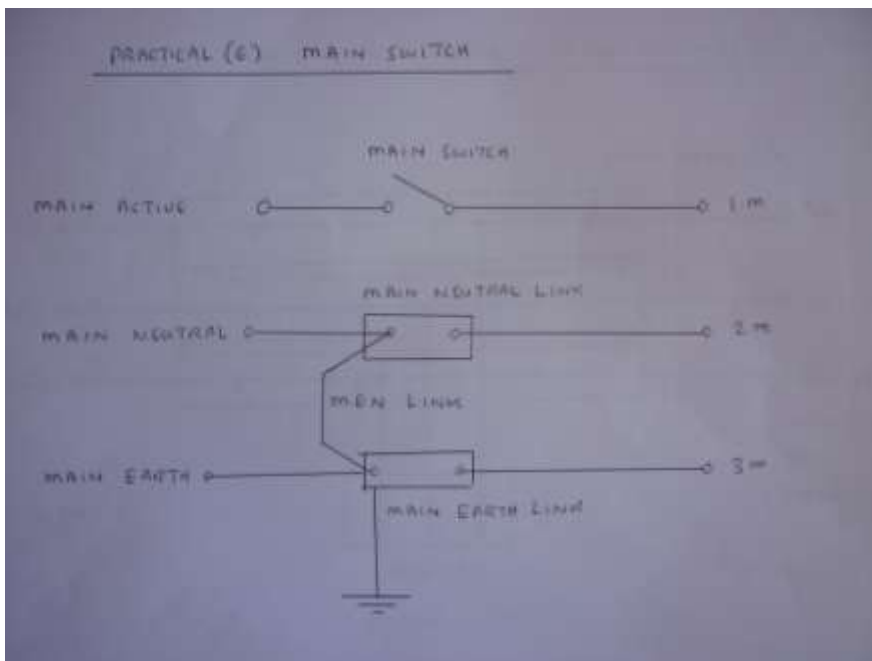
### Practical (6) Main

Wire the main board wiring by using the following circuit diagrams (OR) Trace the circuit & draw the circuit diagram.



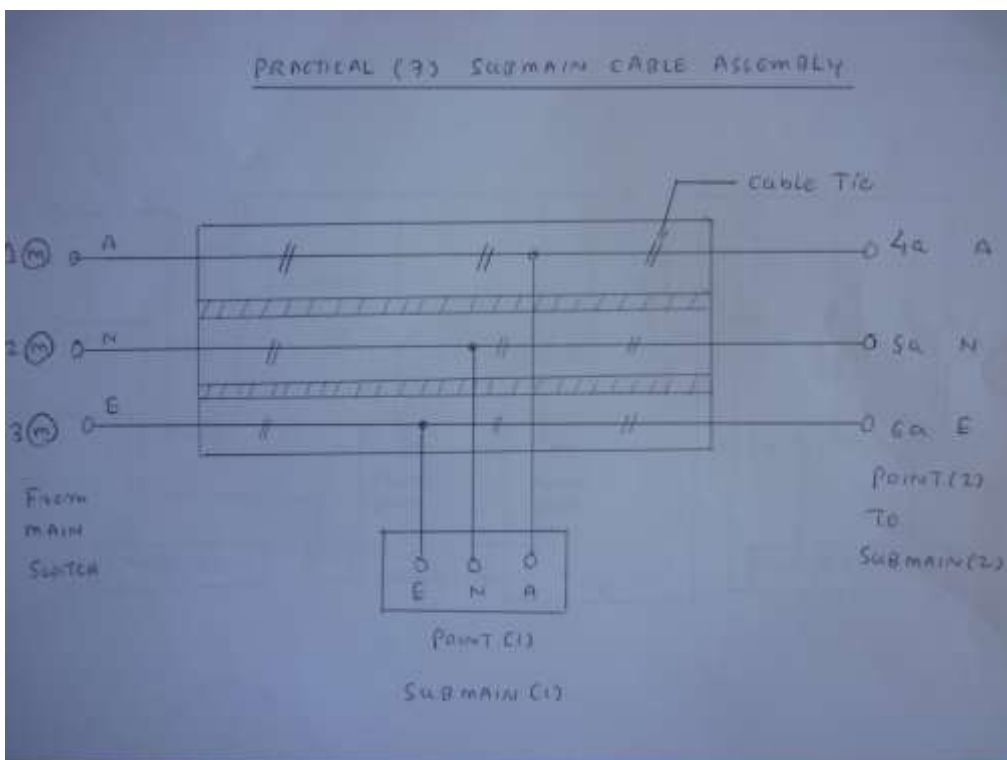
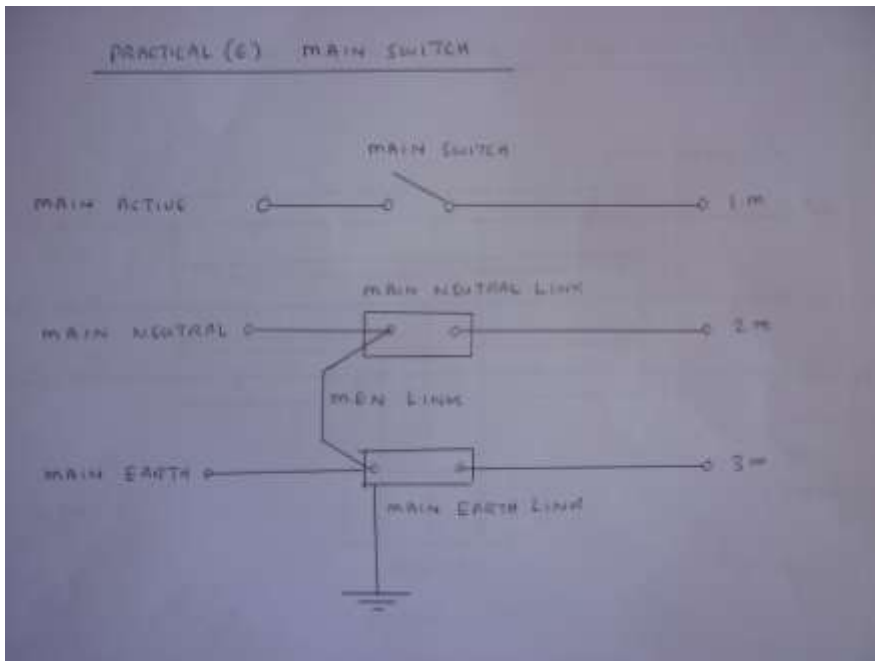
### Practical (7) Sub-main Board Wiring


Wire the main, sub-main and distribution board wiring by using the following circuit diagrams (OR)  
Trace the circuit & draw the circuit diagram.





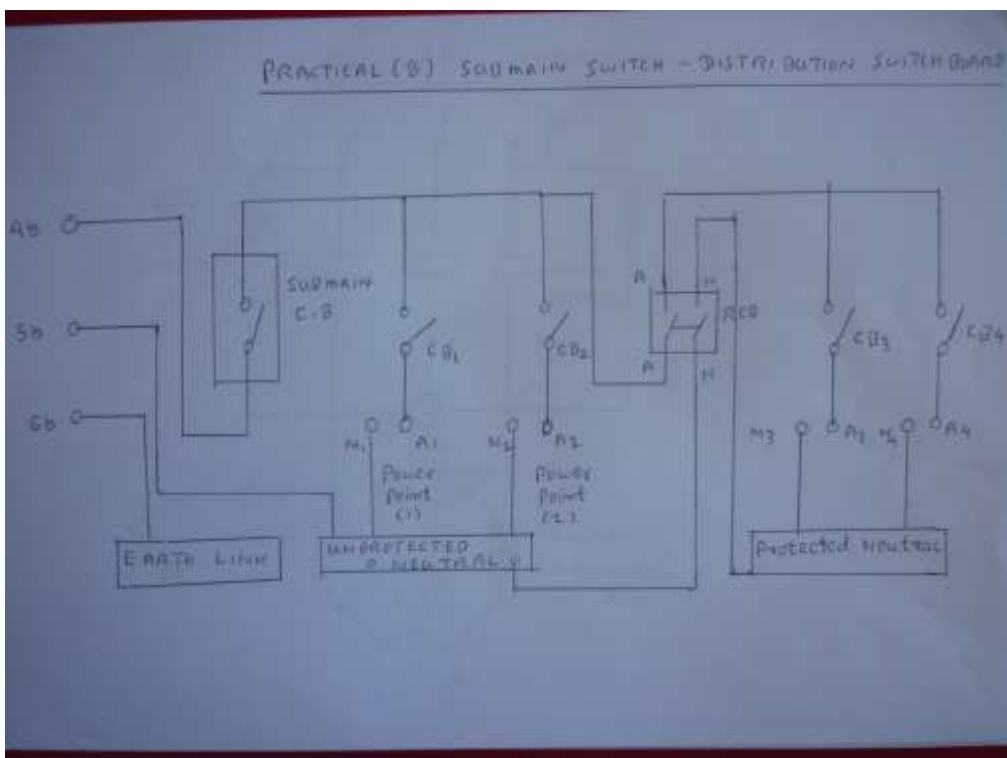
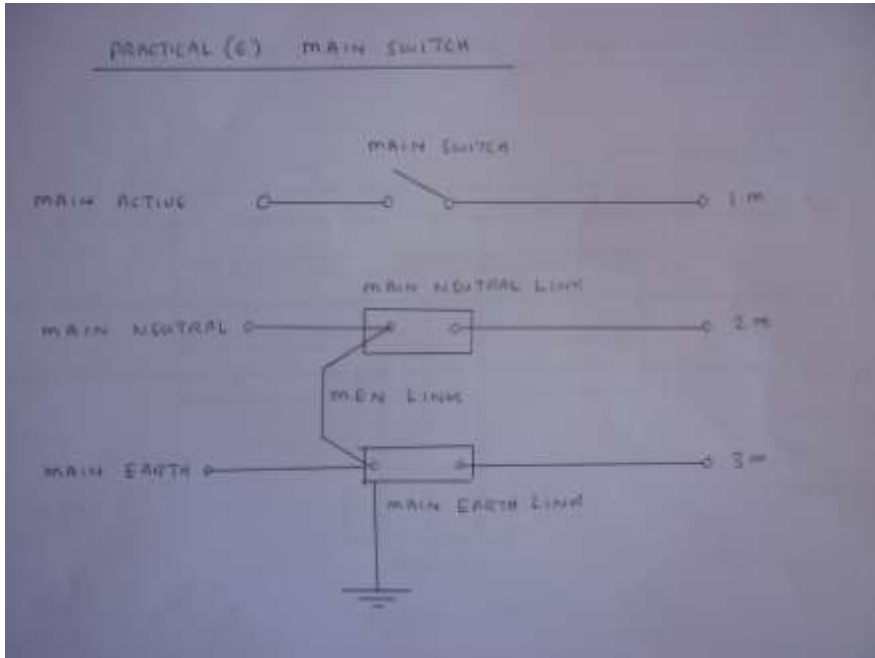
### Practical (8) Distribution Board Wiring

Wire the distribution board wiring by using the following circuit diagrams (OR) Trace the circuit & draw the circuit diagram.




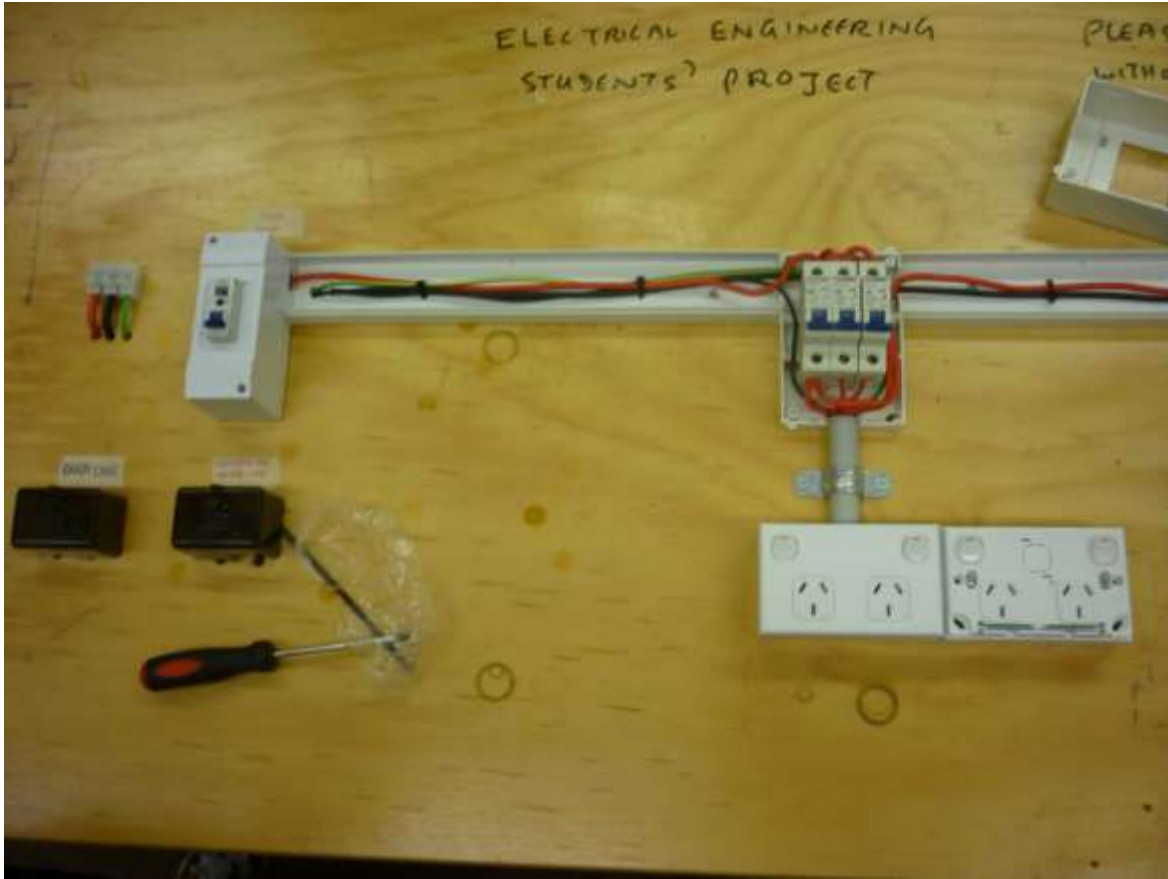


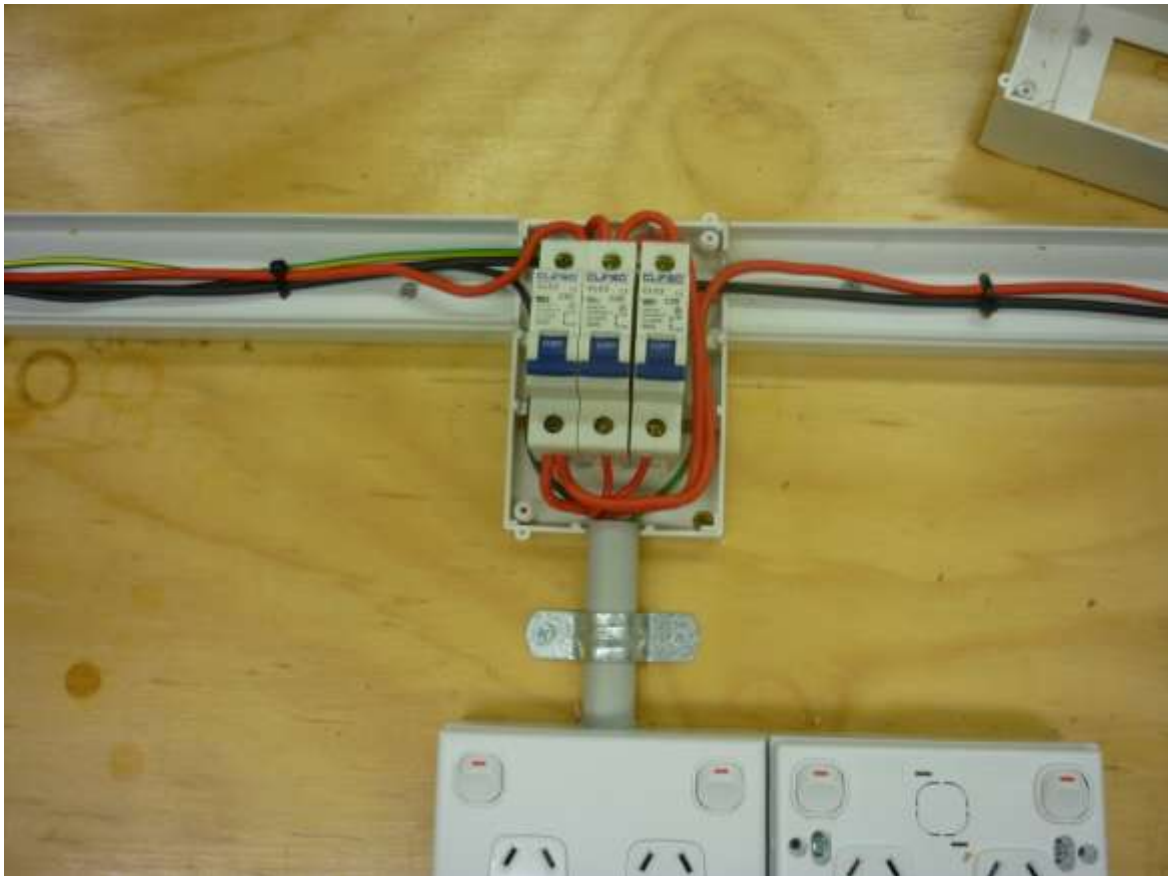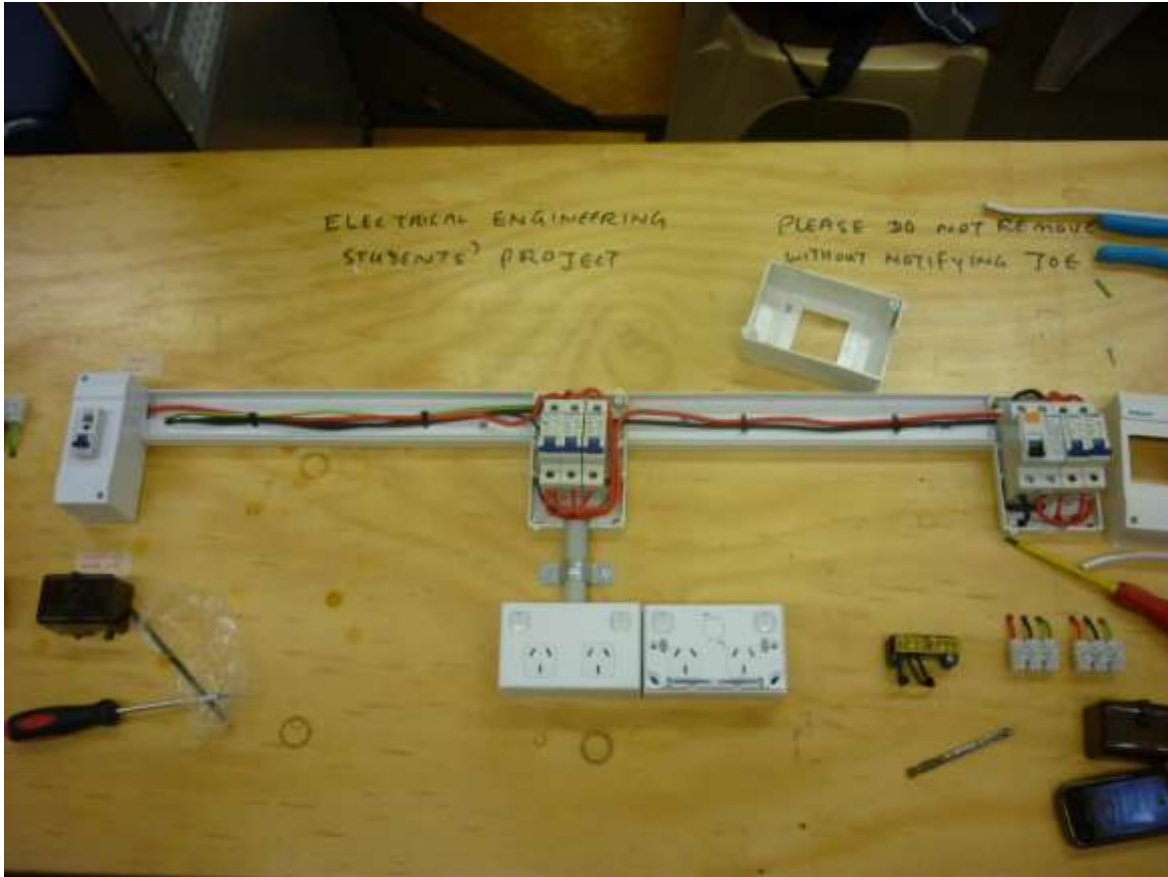

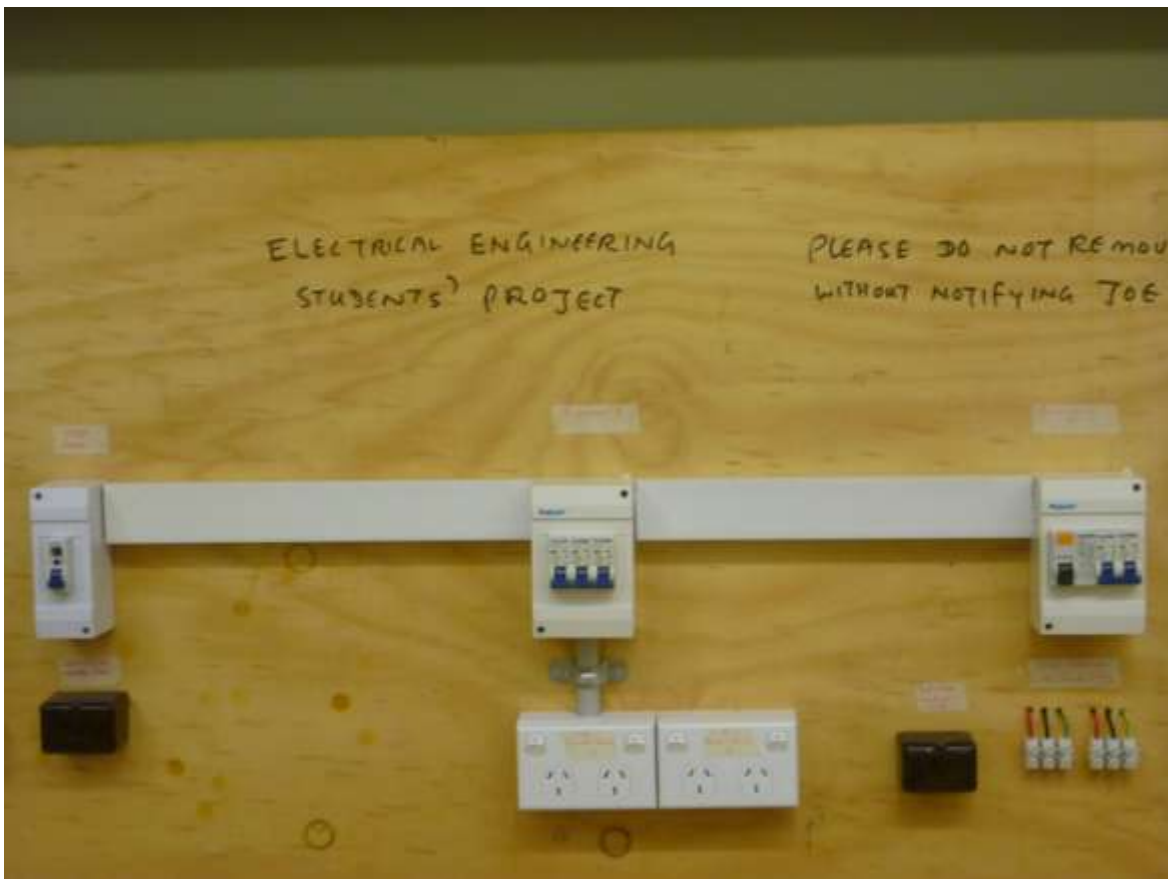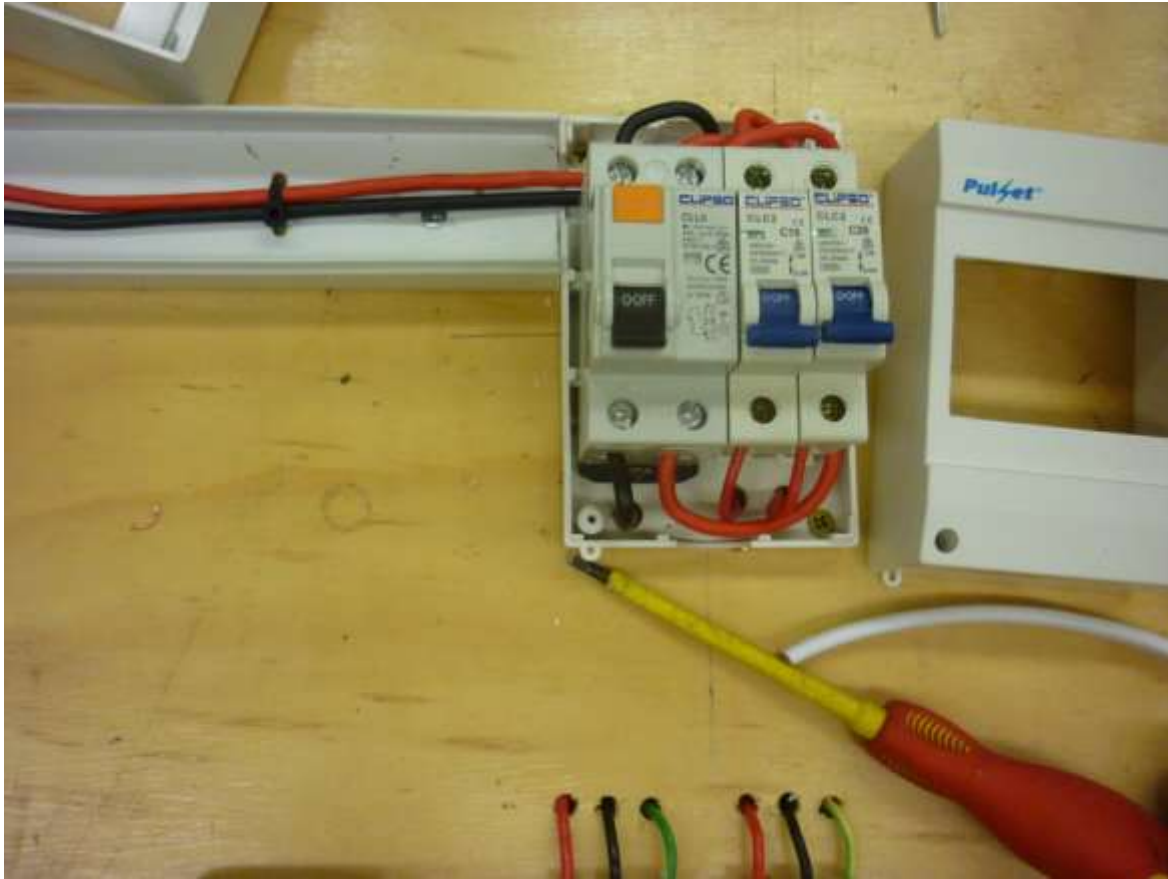
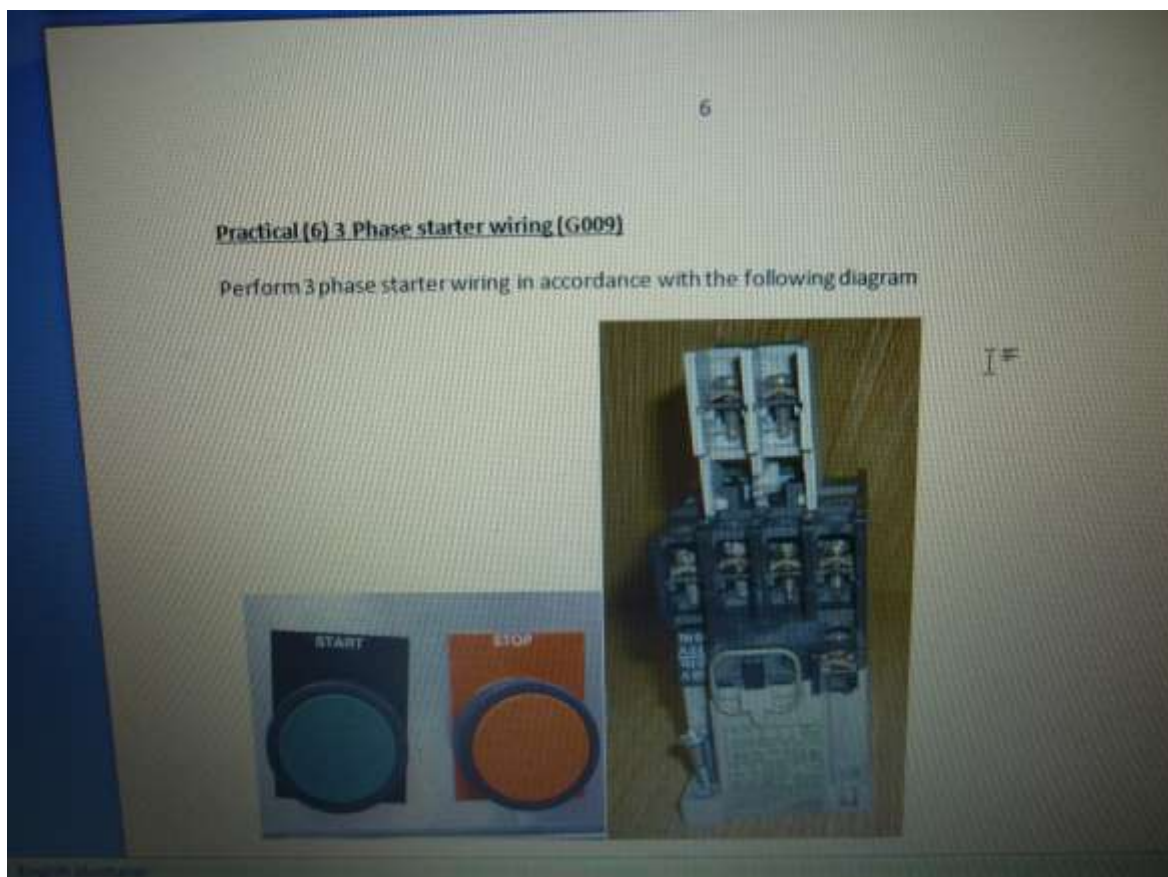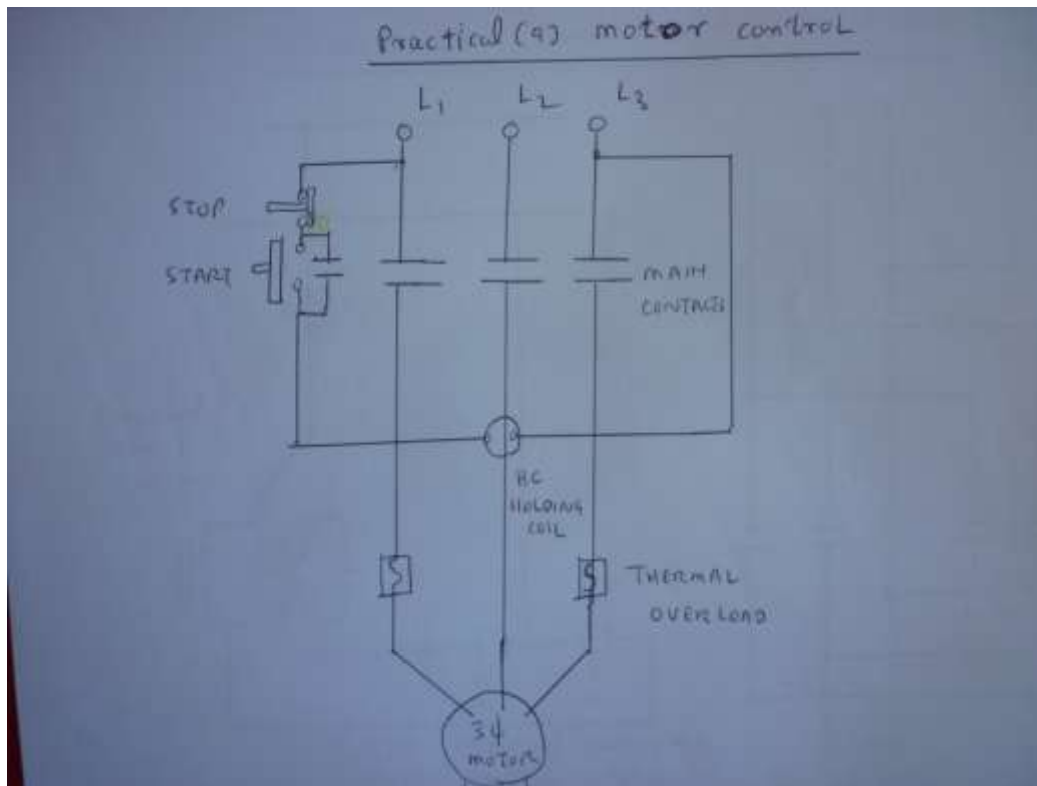
### Practical (9) Motor Control

Connect the following motor control Direct Online Starter by using the given diagram.











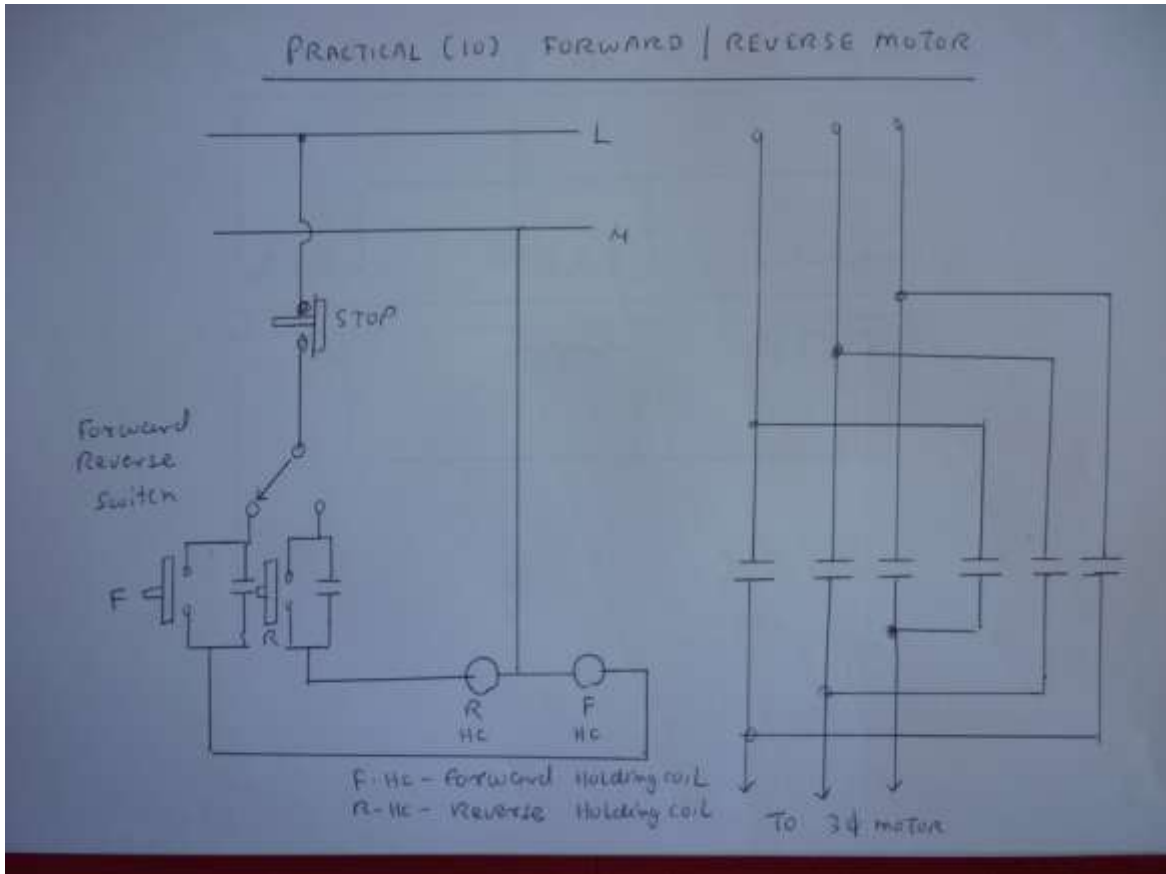
### Practical (10) Forward Reverse Connection of motor

Connect the following forward reverse Connection motor control Direct Online Starter by using the given diagram.



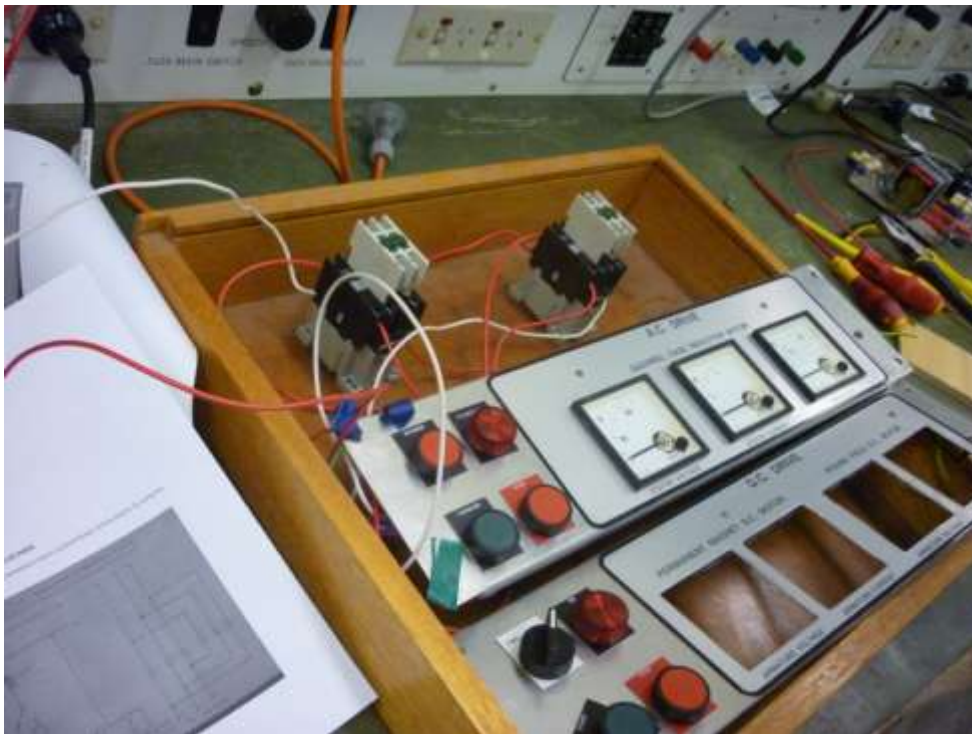

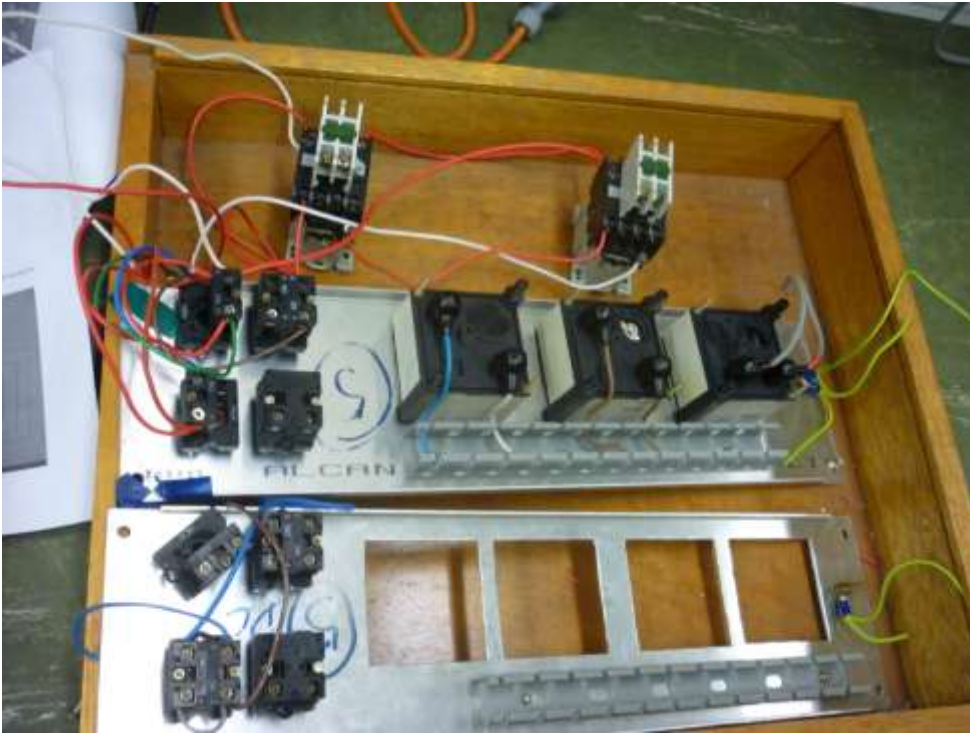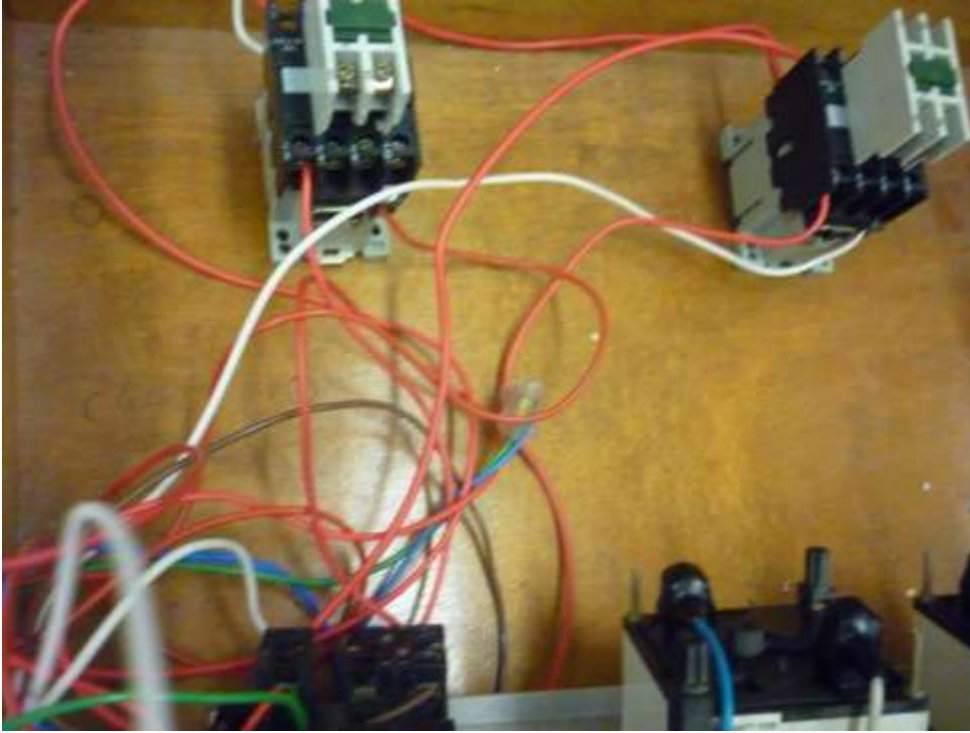


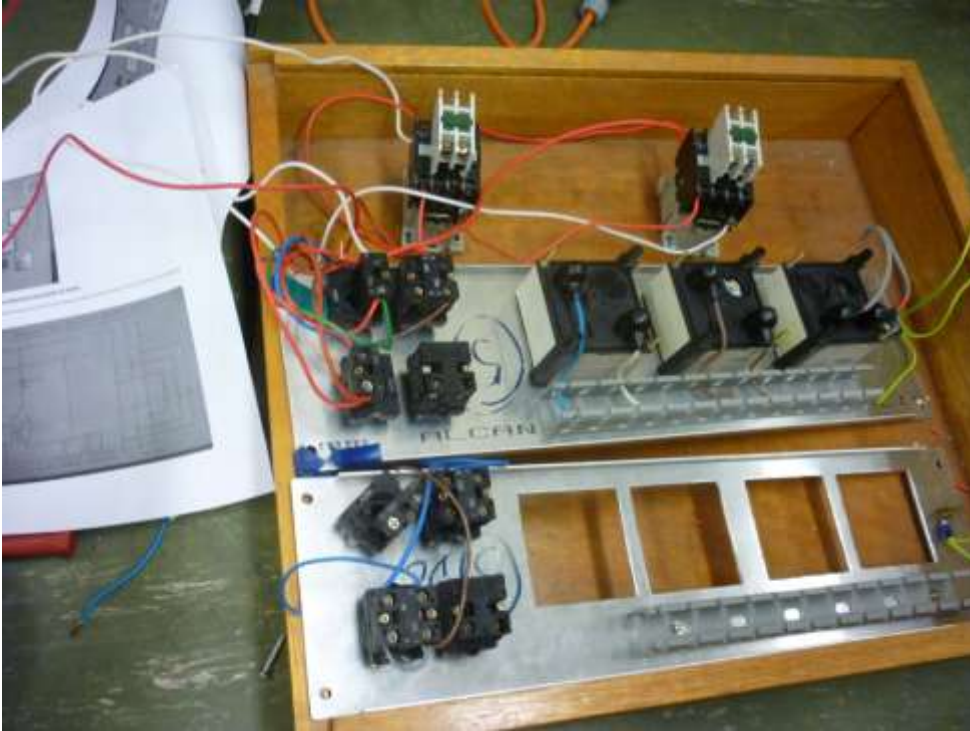

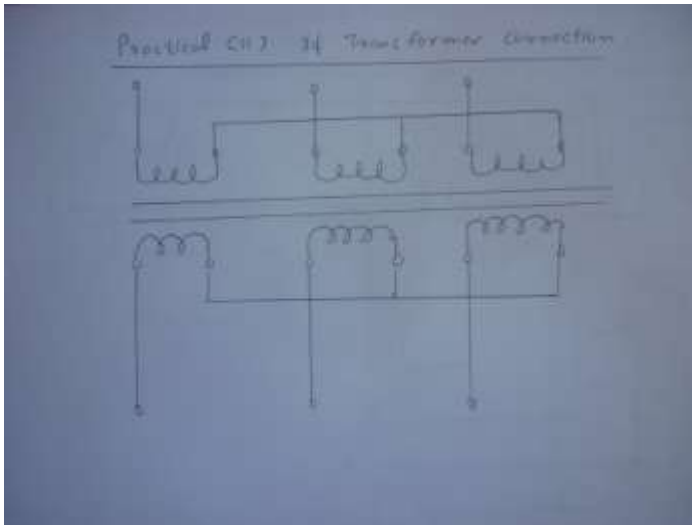**Practical (11) Three phase transformer connection.**


Connect the following three phase transformer connection by using the given circuit diagram.







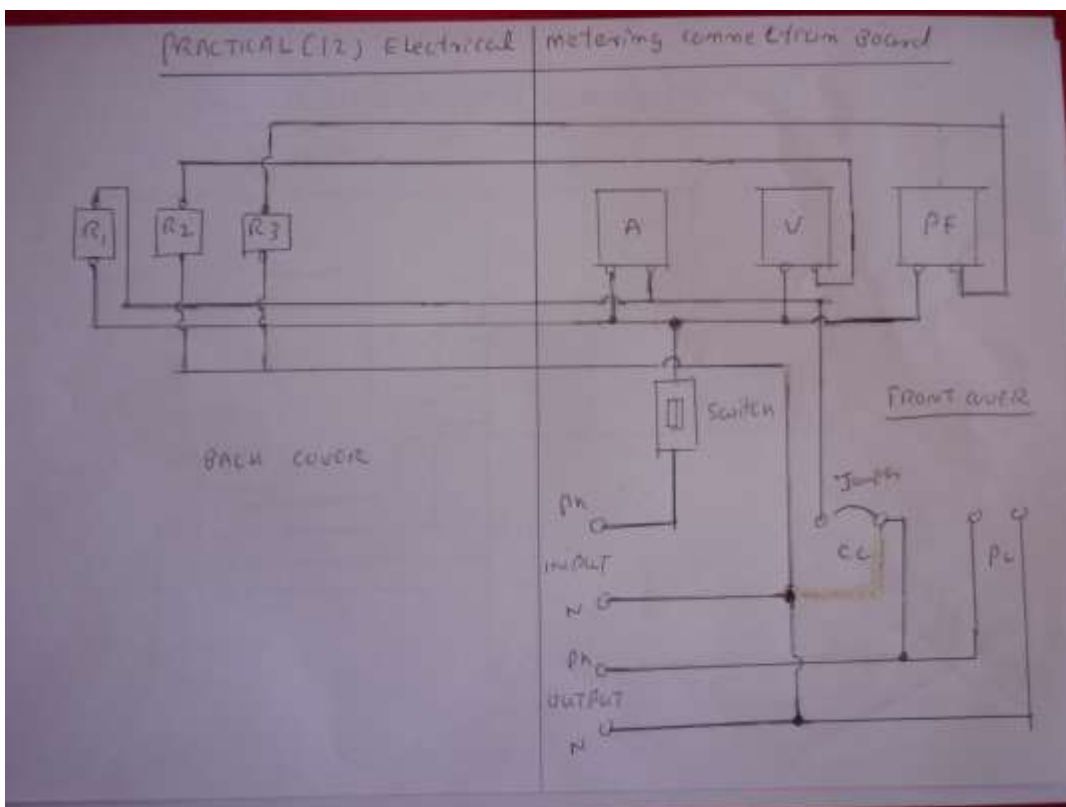
### Practical (12) Metering panel connection

Connect the following metering equipments.




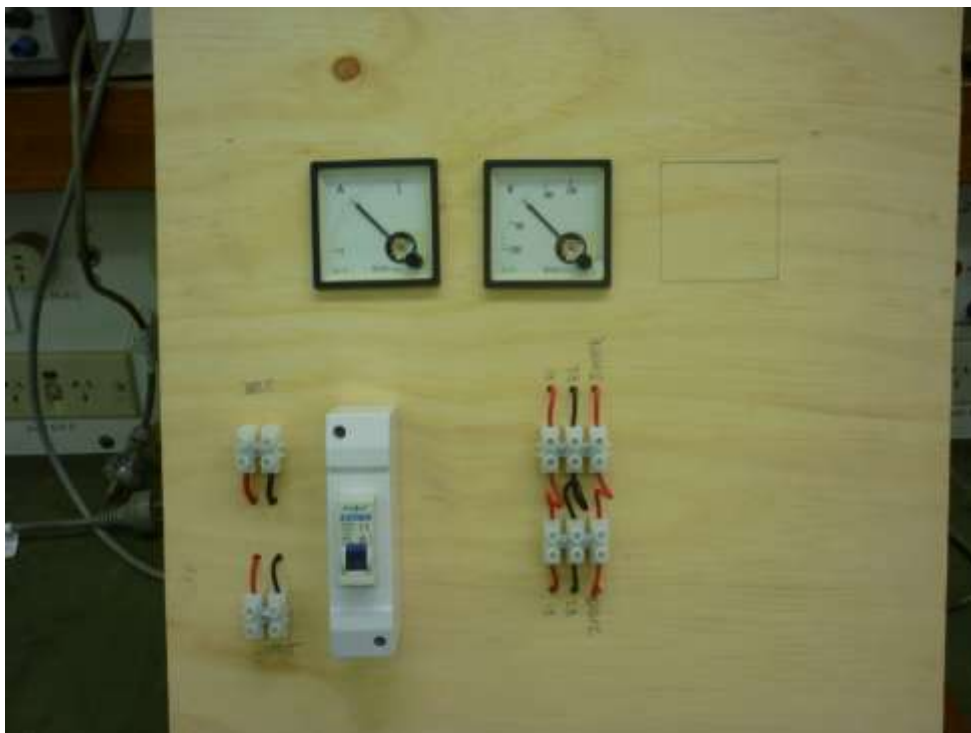
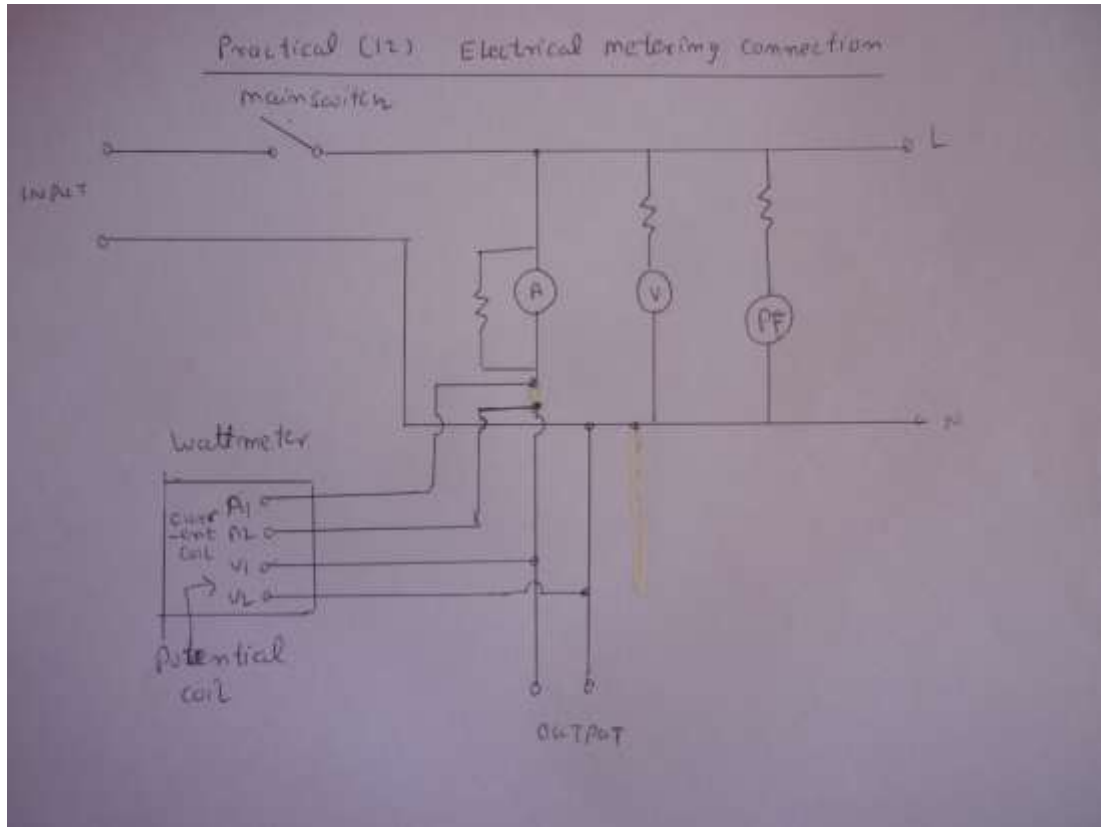


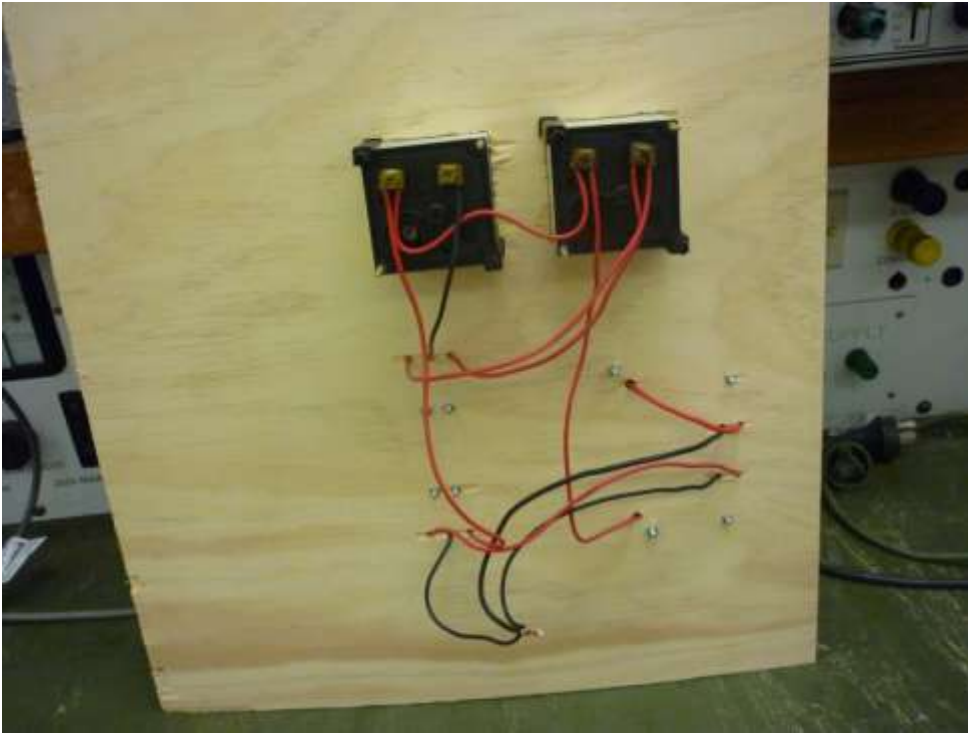
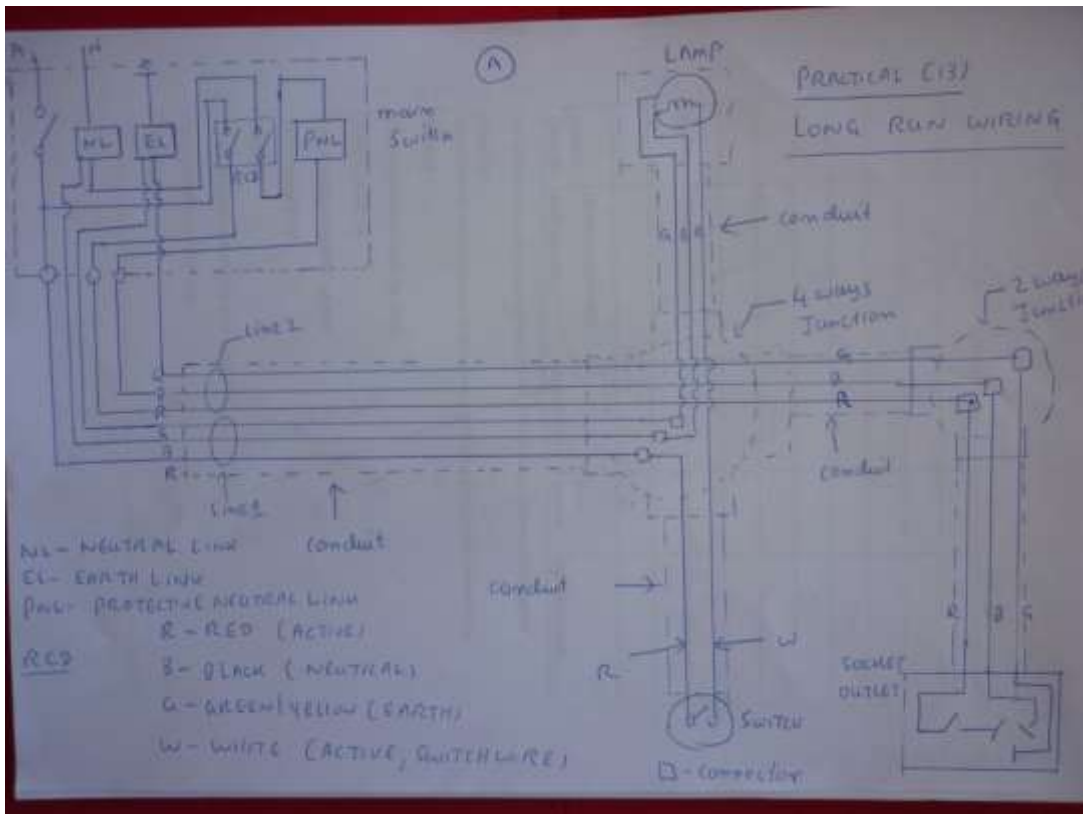
### Practical (13) Long run wiring

Install the following long run wiring by using the following circuit connection and conduit layout diagrams.



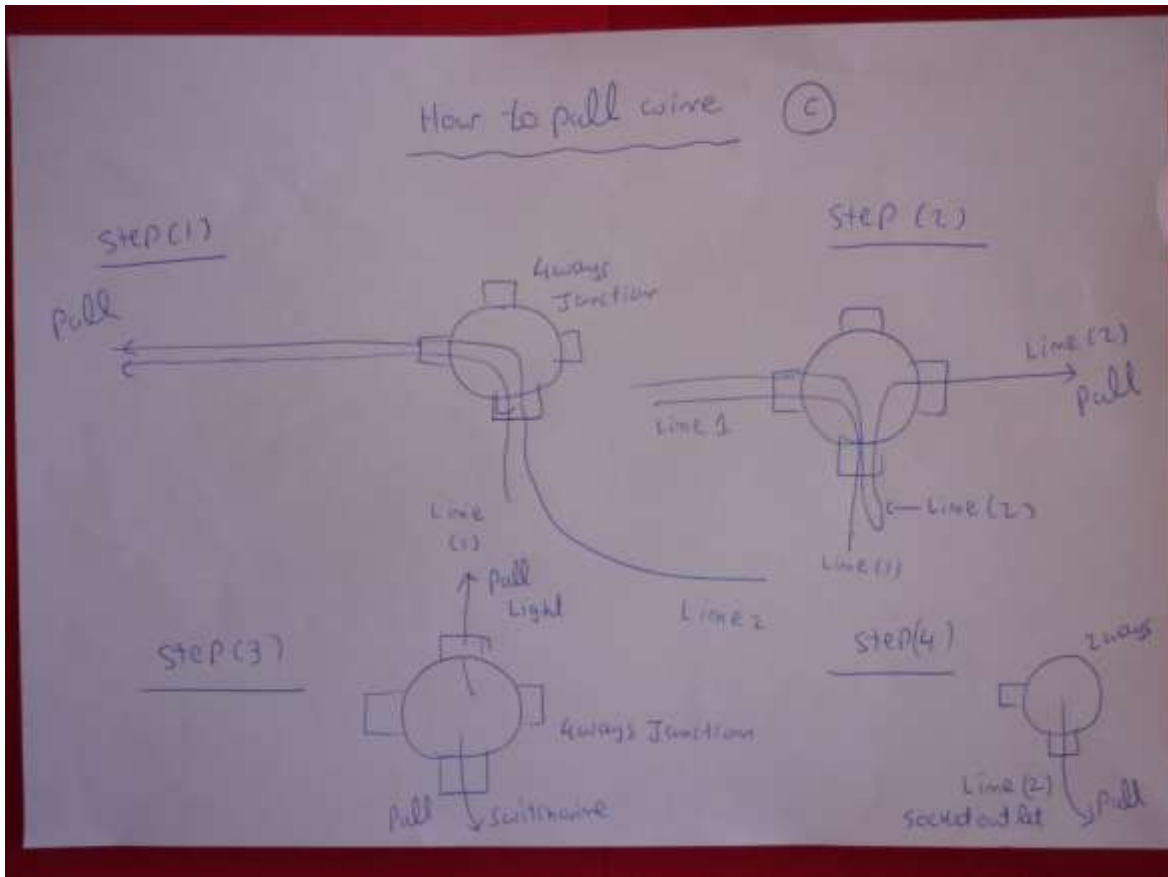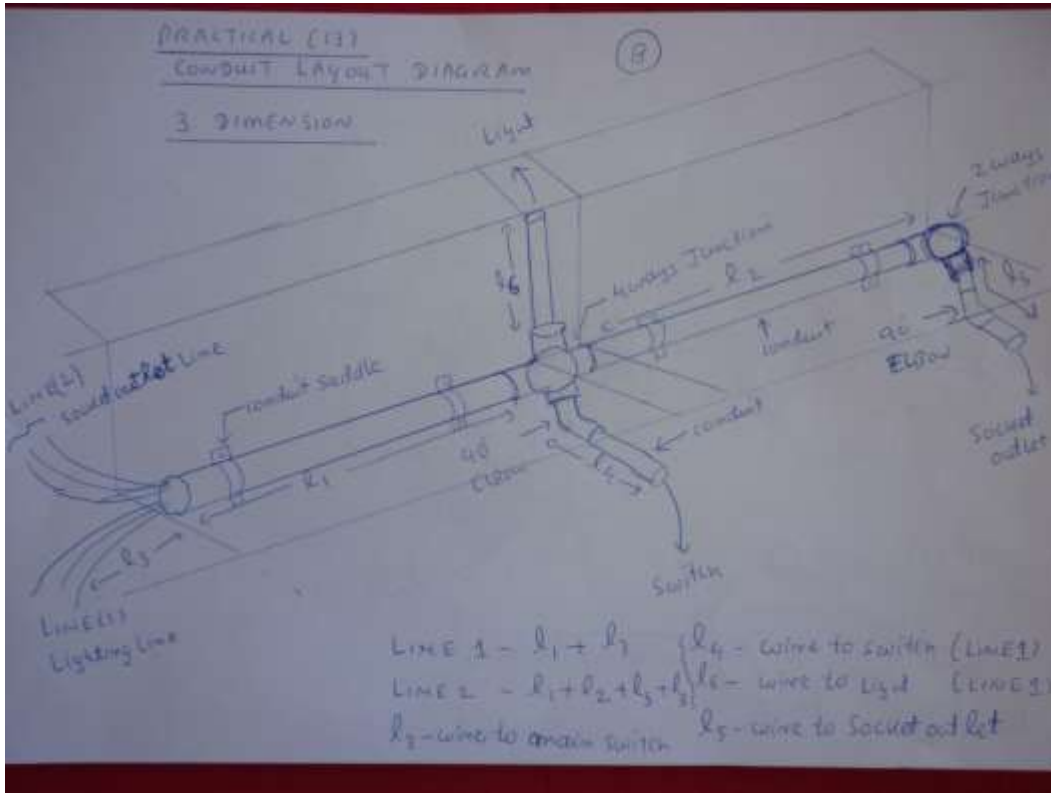












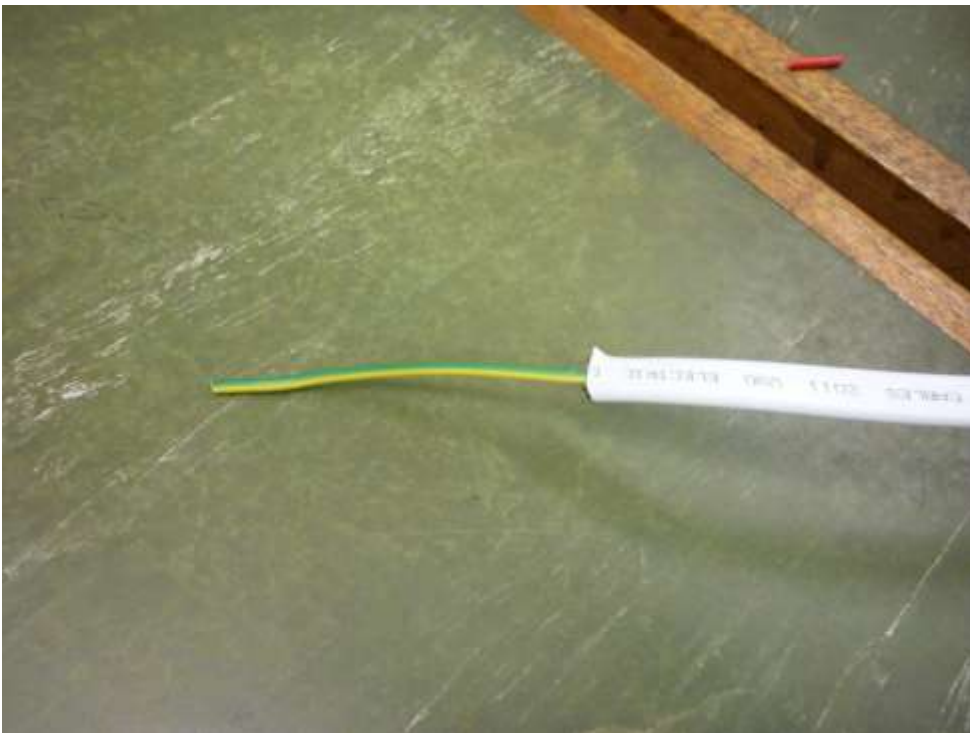




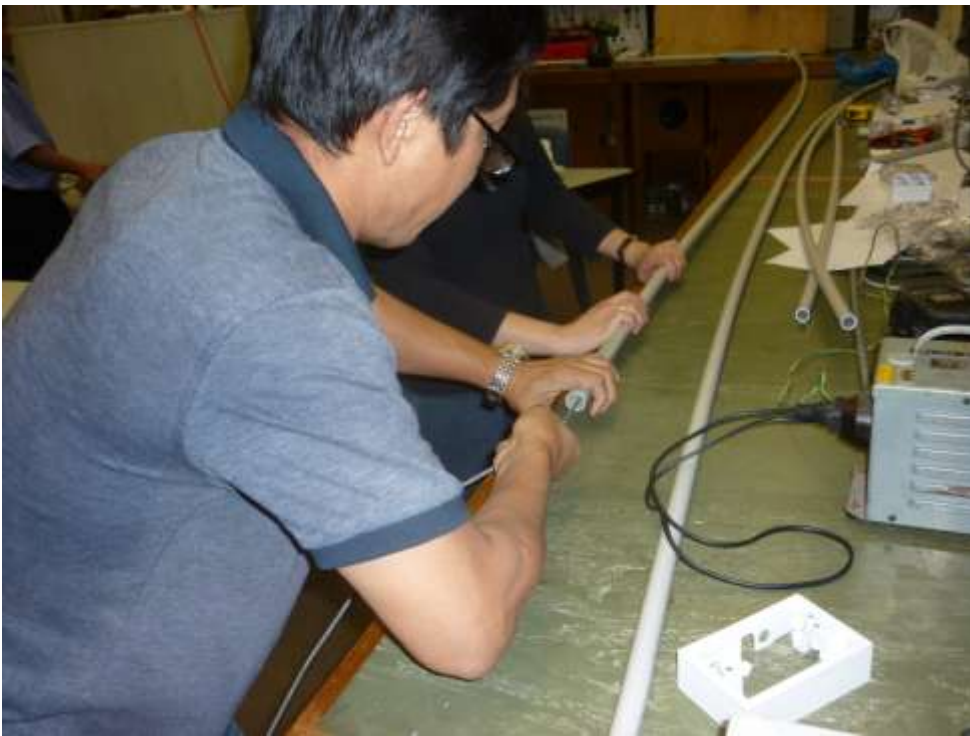

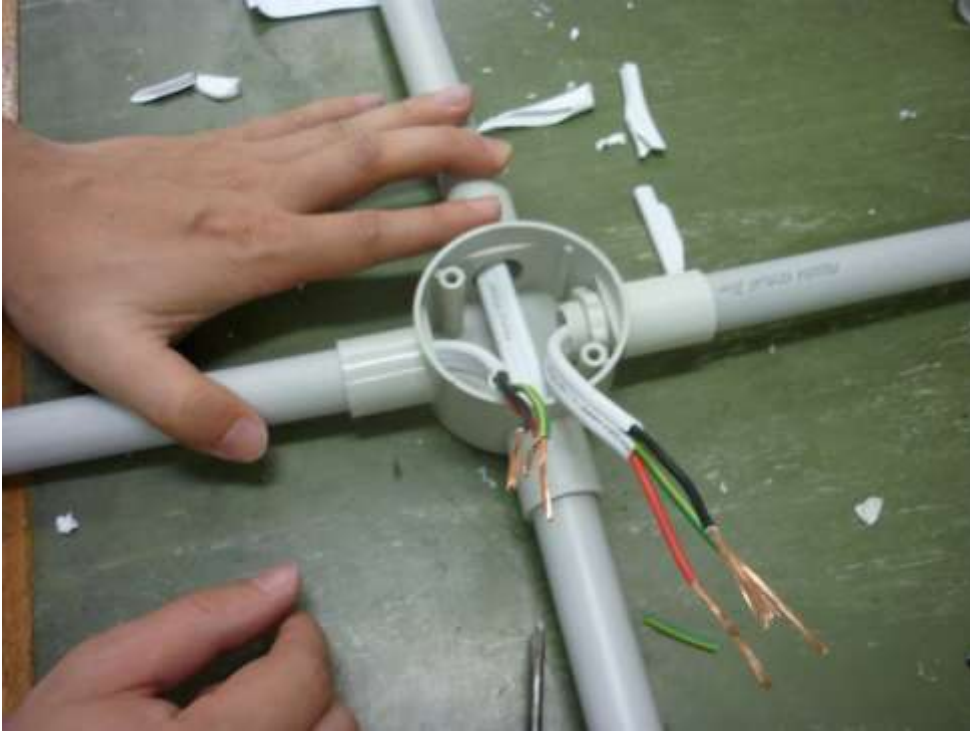





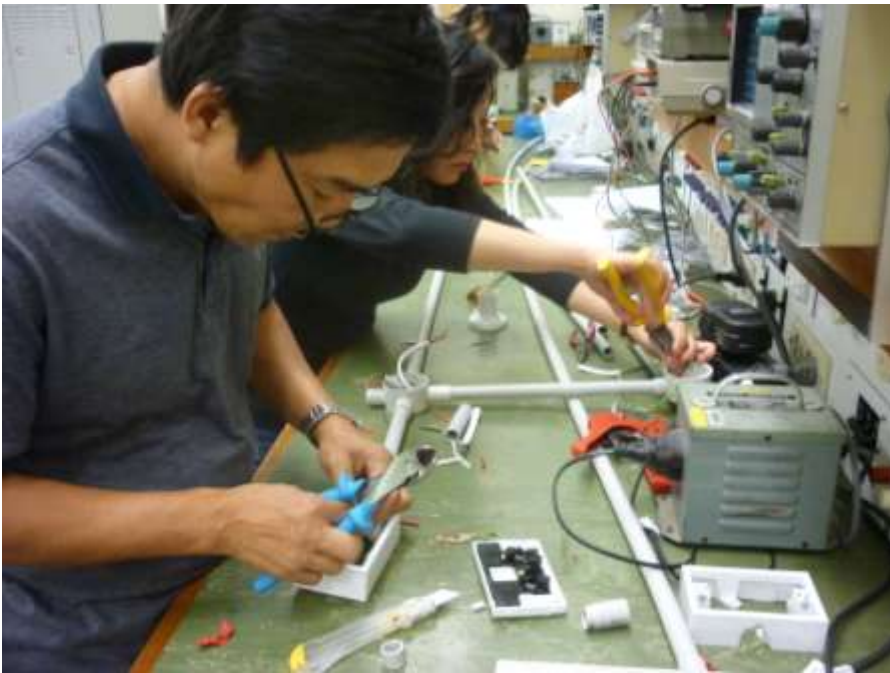

### **Practical (14 +15+ 16) Electrical Installation Safety Testing**

Perform the electrical installation safety by referring circuit safety testing and verification instruction book.

[http://www.filefactory.com/file/c4bbed5/n/Circuit\\_safety\\_Testing\\_and\\_Verification.zip](http://www.filefactory.com/file/c4bbed5/n/Circuit_safety_Testing_and_Verification.zip)

### **Practical 17+18 Motor Rewinding**

Rewind the motors as instructed by teacher