
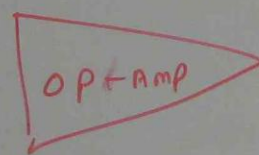



OPERATIONAL AMPLIFIER CHARACTERISTICS

FREQUENCY RESPONSE


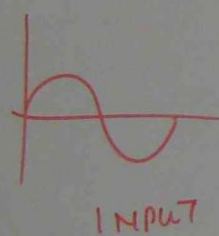
FREQUENCY RESPONSE DESCRIBES HOW THE OUTPUT OF AN AMPLIFIER RESPONDS TO VARIOUS INPUT FREQUENCIES.



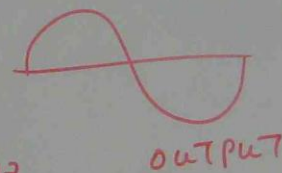10KHz \rightarrow 100MHz
OPERATION
FREQUENCY RANGE




IF 200MHz

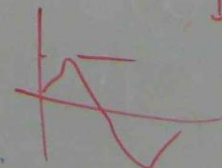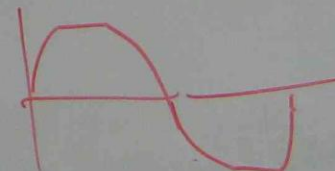


BAND WIDTH

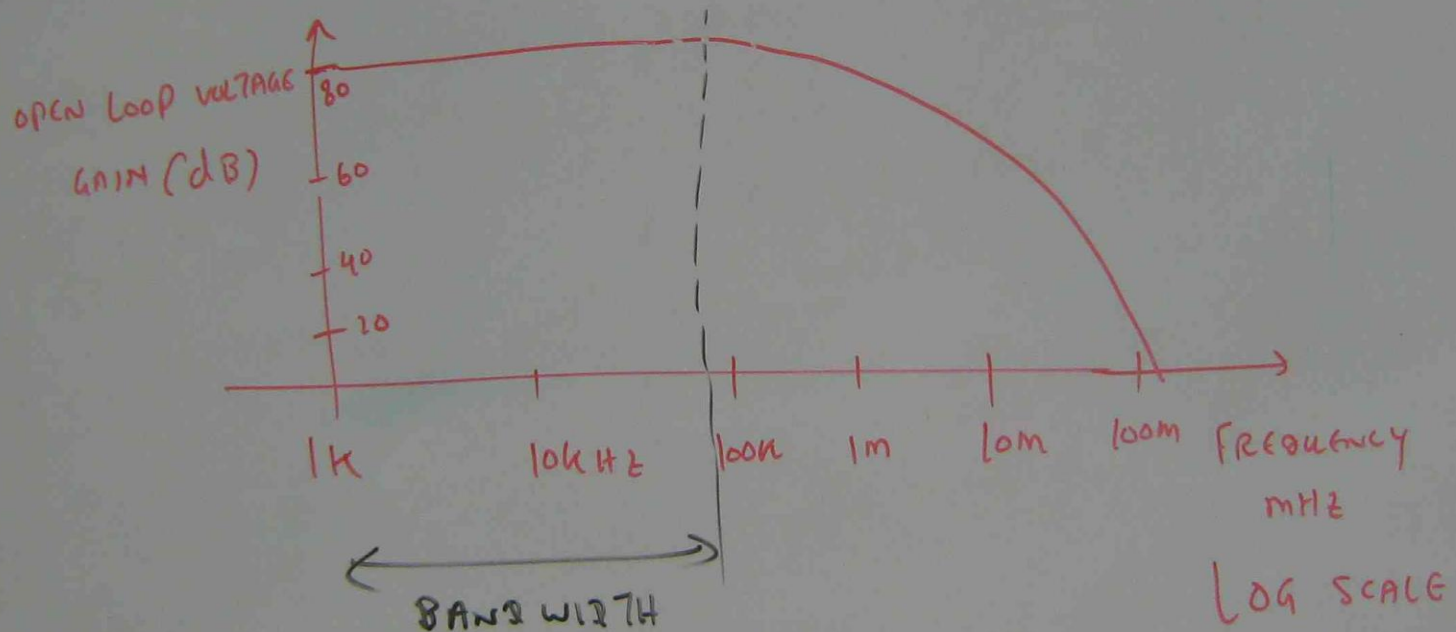THE RANGE OF FREQUENCIES AN AMPLIFIER CAN EFFECTUALLY
AMPLIFY IS REFERRED TO AS THE BAND WIDTH



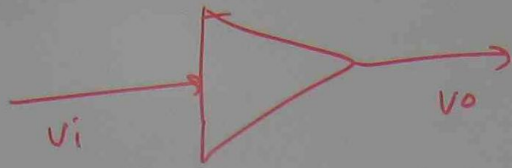BETTER QUALITY \rightarrow WIDER BANDWIDTH



$$\text{VOLTAGE GAIN } (A_V) = \frac{V_o}{V_i}$$

$$A_V \text{ (in dB)} = 20 \log_{10} A_V = 20 \log_{10} A_V$$


Pb
If dB of amplifier is 4, calculate voltage gain

$$\text{dB} = 20 \log_{10} A_V$$


$$4 = 20 \log_{10} A_V$$

$$0.2 = \log_{10} A_V \rightarrow A_V = 10^{0.2} = 1.58$$

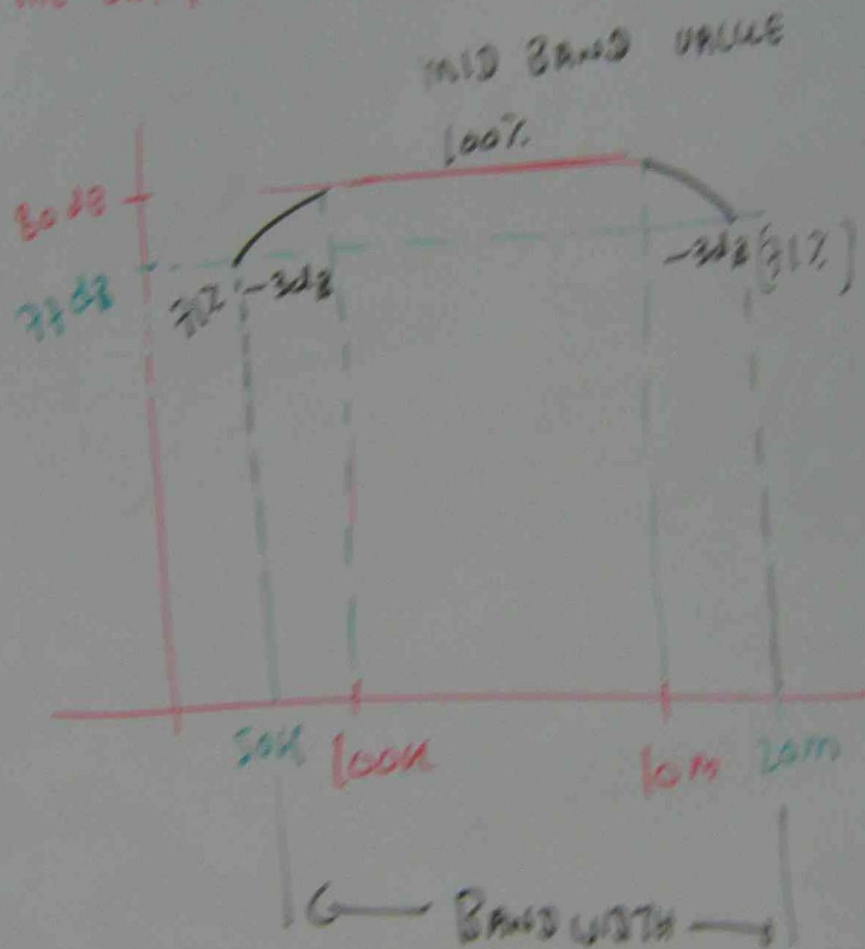* THE BANDWIDTH OF AN AMPLIFIER IS THAT RANGE OF FREQUENCIES
 BETWEEN -3dB POINTS WHERE -3dB EQUALS THE POINT
 WHERE THE OUTPUT HAS FALLEN TO 71% OF ITS MID BAND VALUE




PHASE SHIFT

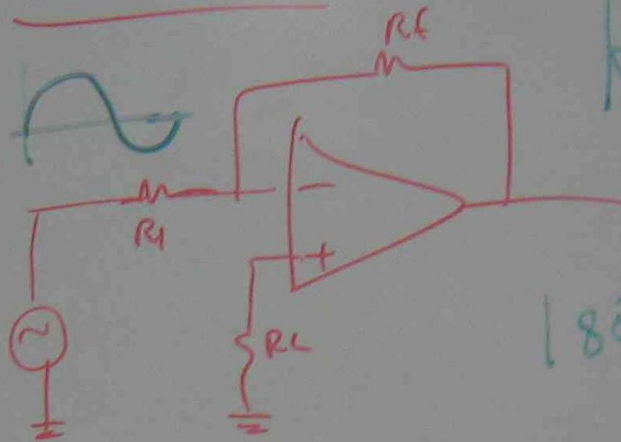

180° PHASE SHIFT

INVERTING

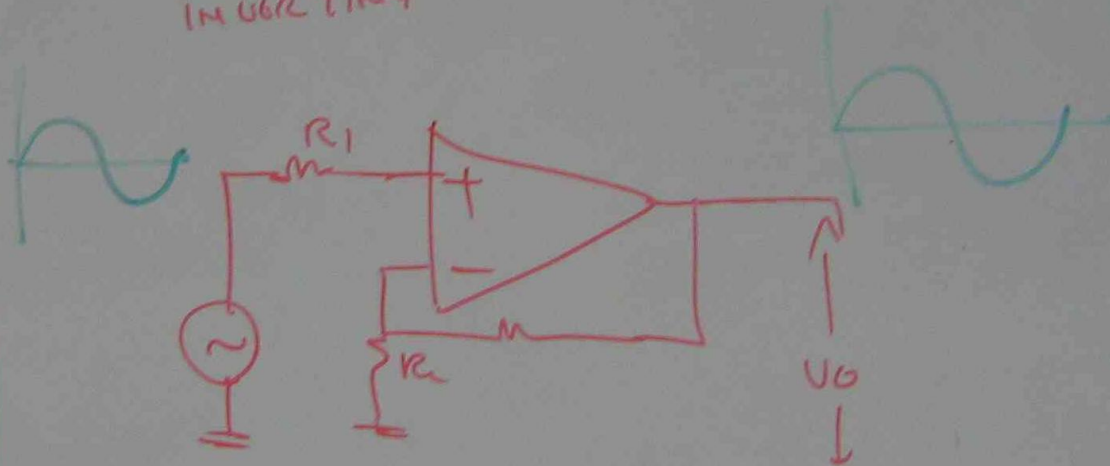

NON-INVERTING

0° PHASE SHIFT

ANOTHER IMPORTANT CONSIDERATION IS THE PHASE RELATIONSHIP BETWEEN THE INPUT AND OUTPUT VOLTAGES OF THE AMPLIFIER.

THE NORMAL PHASE DIFFERENCE IS EITHER 0° OR 180° BUT AS FREQUENCY INCREASES, THE OTHER PHASE SHIFTS ANGLES CAN OCCUR AND THE CIRCUIT CAN BECOME UNSTABLE.

COMPENSATION

- INTERNAL FREQUENCY COMPENSATION
741, TL071, TL081, LF411
- EXTERNAL FREQUENCY COMPENSATION

$$X_c = \frac{1}{2\pi f_c} \rightarrow f_c = \frac{1}{2\pi X_c \times C}$$


VERY STABLE BUT LIMITED
SMALL SIGNAL BANDWIDTH

IF WIDER FREQUENCY IS TO BE
APPLIED, EXTERNAL FREQUENCY
COMPENSATION MUST BE PROVIDED.


SINGLE CAPACITOR
COMPENSATION

FEED FORWARD
COMPENSATION

SINGLE CAPACITOR COMPENSATION

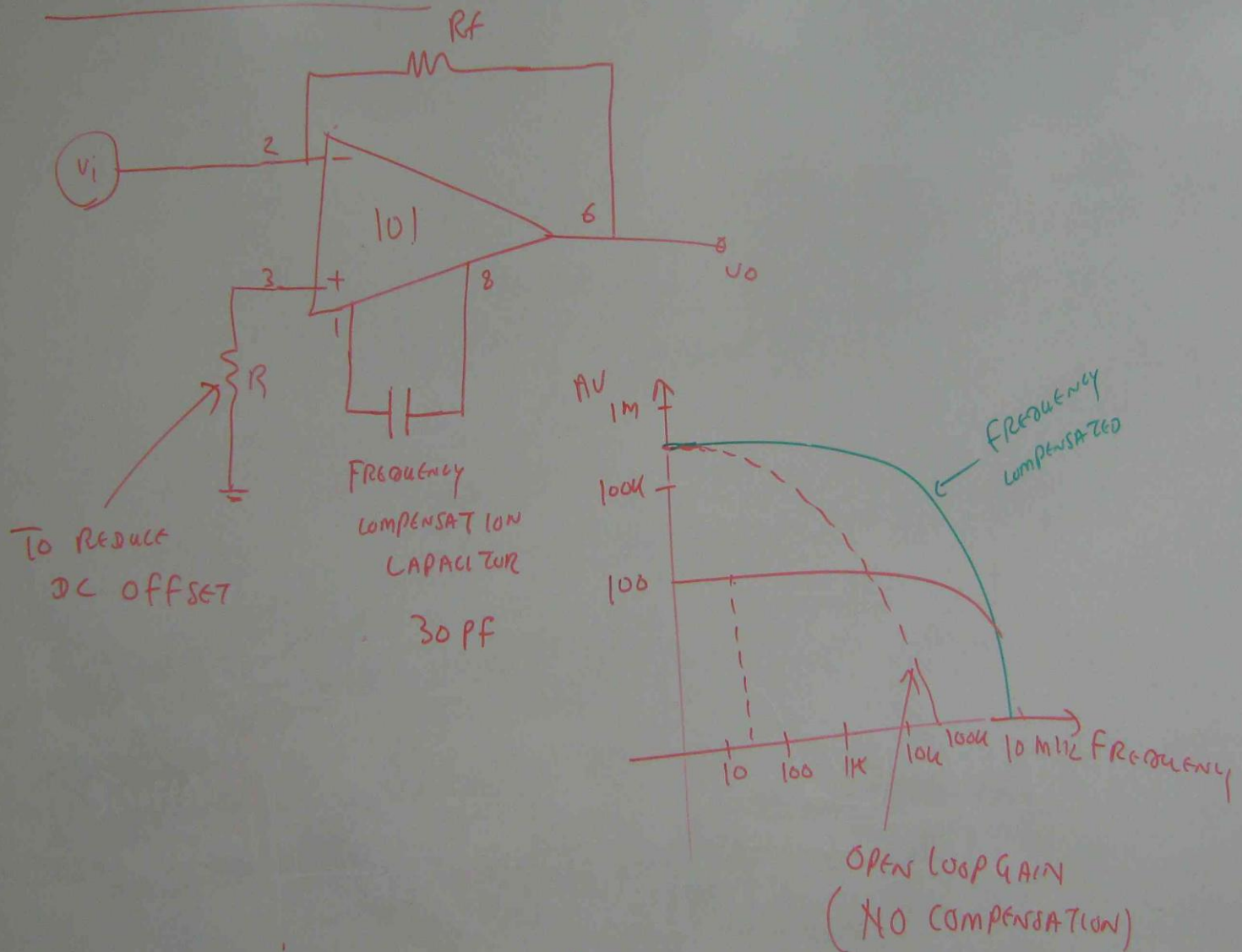

Feed Forward Compensation

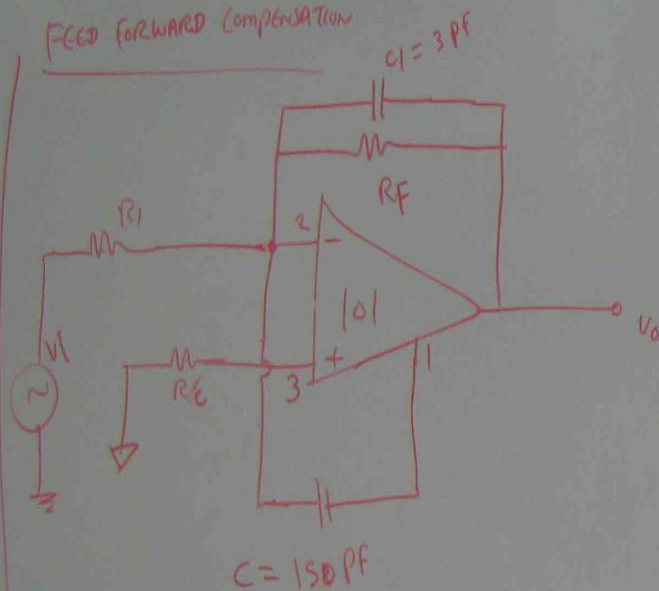

THE BANDWIDTH CAN BE
INCREASED BY FEED FORWARD
COMPENSATION

GAIN BANDWIDTH PRODUCT (GBP)

$$GBP = A_V (\text{closed loop}) \times BW = \text{UNITY GAIN } (UGB)$$

BANDWIDTH
↑
BANDWIDTH OF INTERNALLY
COMPENSATED OP-AMP

pb THE UGB FOR 741 OP-AMP IS 1 MHz AND
4 MHz FOR LF411. IF CLOSED LOOP VOLTAGE
GAIN IS 100, CALCULATE BANDWIDTH

LF411

$$A_V \times BW = UGB$$


$$100 \times BW = 4000 \text{ kHz}$$

$$BW = \frac{4000}{100} = 40 \text{ kHz}$$

741

$$100 \times BW = 1 \text{ MHz}$$
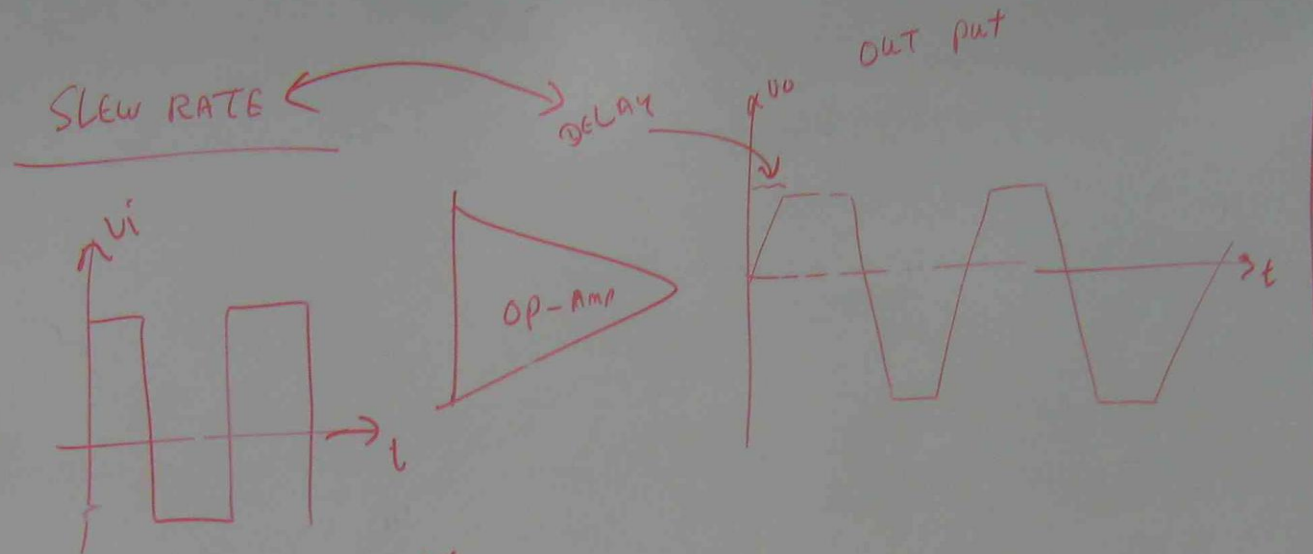
$$BW = \frac{1000 \text{ kHz}}{100} = 10 \text{ kHz}$$



INPUT SQUARE WAVE
STEP CHANGE IN
INPUT


THE SLEW RATE SPECIFICATIONS OF AN OP-AMP
SHOWS HOW FAST THE OUTPUT VOLTAGE OF OP-AMP
CAN CHANGE FOR A STEP CHANGE AT INPUT.

$$\text{SLEW RATE} = \frac{\text{MAXIMUM CHANGE IN } V_o}{\text{CHANGE IN TIME}}$$

ph. If $2V_{p-p}$ SQUARE WAVE AT A FREQUENCY OF 50 KHz IS APPLIED TO A VOLTAGE FOLLOWER WITH A SLEW RATE OF $0.5V/\mu s$

CALCULATE (i) PERIOD OF WAVE FORM

(ii) TIME TAKEN TO CHANGE BY $2V$.

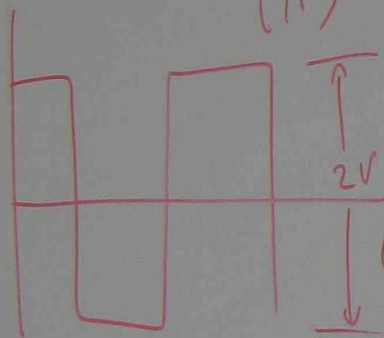

$$f = 50\text{ KHz}$$


$$(i) \quad T = \frac{1}{f} = \frac{1}{50 \times 10^3} = \frac{10^6}{50 \times 10^3} \mu s = 20 \mu s$$

$$\Delta V_o$$

$$(ii) \quad \text{SLEW RATE} = \frac{\Delta V_o}{\Delta t}$$

$$0.5 = \frac{2}{\Delta t} \rightarrow \Delta t = \frac{2}{0.5} = 4 \mu s$$



SLEW RATE
SINE WAVES

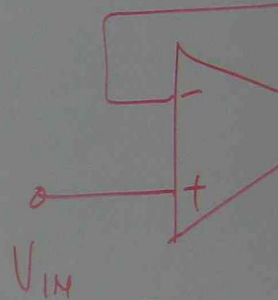

INPUT

f

SLEW RATE LIMITING OF SINE WAVES

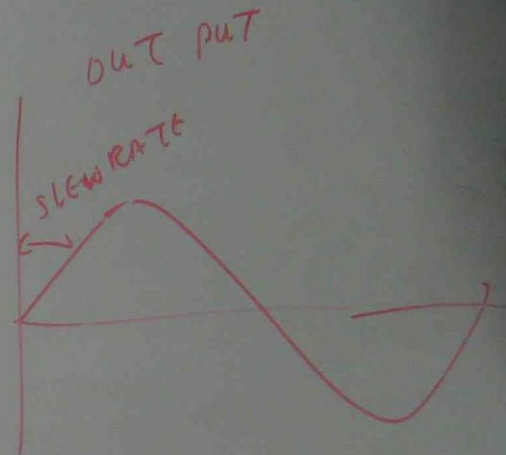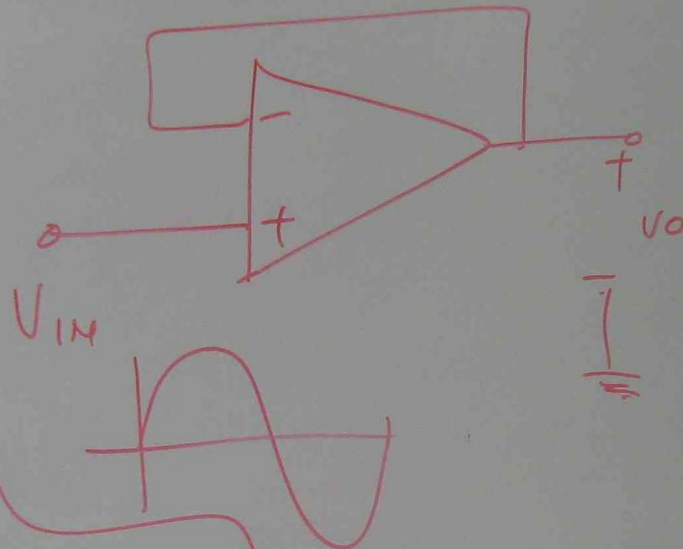

INPUT

$$f_{\text{max}} = \frac{\text{SLEW RATE}}{2\pi V_O \text{ max}}$$


$$= 4 \mu s$$

pb ①

THE SLEW RATE OF A 741 IS $0.5 \text{ V}/\mu\text{s}$. IT IS CONFIGURED AS A VOLTAGE FOLLOWER. DETERMINE THE MAXIMUM FREQUENCY THAT CAN BE OBTAINED FROM THE CIRCUIT FOR THE FOLLOWING VOLTAGES.


(a) A $20 \text{ V}_{\text{p-p}}$ SINE WAVE

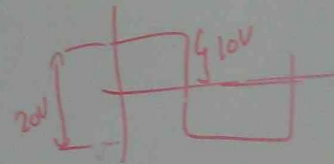(b) A $2 \text{ V}_{\text{p-p}}$ SINE WAVE



$$\begin{aligned} (a) f_{\text{max}} &= \frac{\text{SLEW RATE}}{2\pi V_{o \text{ max}}} = \frac{0.5}{2 \times 3.1416 \times 10 \times 10^6} \\ &= \frac{0.5 \times 10^6}{2 \times 3.1416 \times 10} \text{ Hz} \\ &= \frac{0.5 \times 10^3}{2 \times 3.1416 \times 10} \text{ kHz} \\ &= 7.96 \text{ kHz} \end{aligned}$$

$$\begin{aligned}
 (b) f_{\max} &= \frac{0.9}{2 \times 3.1416 \times 1 \times 10^5} \\
 &= \frac{0.5 \times 10^6}{2 \times 3.1416 \times 1} \text{ Hz} \\
 &= \frac{0.5 \times 10^3}{2 \times 3.1416 \times 1} \text{ kHz} \\
 &= 79.6 \text{ kHz}
 \end{aligned}$$

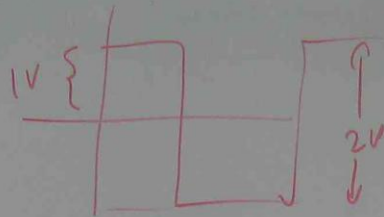

pb2

DETERMINE THE BANDWIDTH OF AN INVERTING AMPLIFIER WITH A CLOSED LOOP GAIN OF $(-)$ 150. THAT IS CONSTRUCTED WITH AN INTERNALLY COMPENSATED OP AMP THAT HAS A UNITY GAIN BANDWIDTH OF 2 MHz.

$$A_v(\text{closed loop}) \times BW = UGB$$

$$150 \times BW = 2 \text{ MHz}$$


$$BW = \frac{2000 \text{ kHz}}{150} = 13.33 \text{ kHz}$$

Pb 3

DETERMINE THE SLEW RATE OF THE OP-AMP

WHOSE OUTPUT RESPONSE TO A SQUARE WAVE IS SHOWN IN


FIGURE

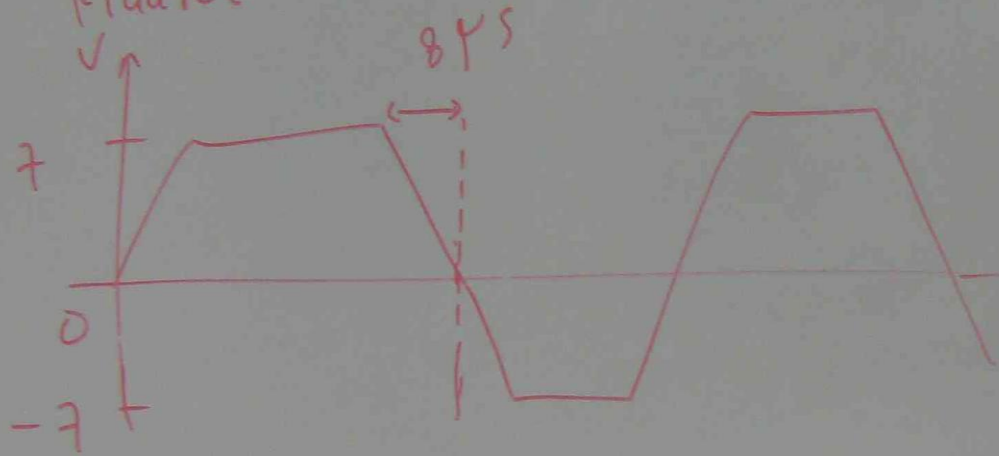

$$\text{SLEW RATE} = \frac{\text{MAX CHANGE IN } V_O}{\text{CHANGE IN TIME}} = \frac{7}{8 \mu s}$$

$$= 0.875 \text{ V} / \mu s$$

pb 4

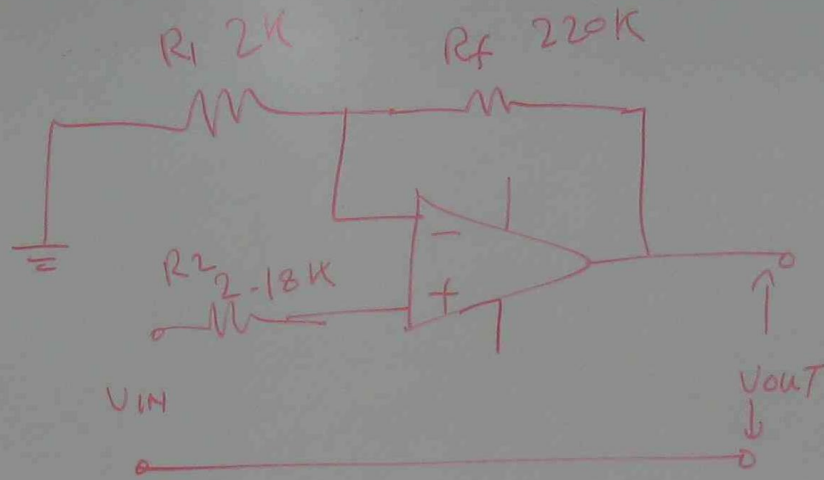

THE ABOVE CIRCUIT IS A NON-INVERTING AMPLIFIER
 CONSTRUCTED WITH A 741 OP-AMP. SLEW RATE
 IS 0.5 V/μs. UNITY GAIN BAND WIDTH IS 1 MHz
 DETERMINE (a) THE BANDWIDTH OF THE CIRCUIT
 (b) MAXIMUM PEAK TO PEAK OUTPUT
 VOLTAGE.

$$A_v \times BW = UGB$$

$$? \times BW = 1 \text{ MHz}$$

$$a) V_o = \frac{R_f}{R_1} V_i$$

$$V_o = \frac{220}{2} \times V_i$$

$$\frac{V_o}{V_i} = A_v = 110$$

$$110 \times BW = 1 \times 10^3 \text{ kHz}$$

$$BW = \frac{1000}{110} \text{ kHz} = 9.09 \text{ kHz}$$

b)

$$\text{Slew Rate} = \frac{V_o}{\text{CHANGE IN TIME}} \Rightarrow \frac{0.5 \text{ V}}{1 \mu\text{s}} = \frac{V_o}{1 \mu\text{s}}$$

$$V_o = 0.5 \text{ V}$$

$$T = \frac{1}{f} = \frac{1}{10^6} = 1 \mu\text{s}$$

$$N = \frac{120f}{p}$$

N = MOTOR SPEED

f = FREQUENCY


p = NO. OF POLES.


IF $f = 50 \text{ Hz}$

$p = 4 \text{ poles}$


$$N = \frac{120 \times 50}{4}$$

$$= 1500 \text{ RPM}$$

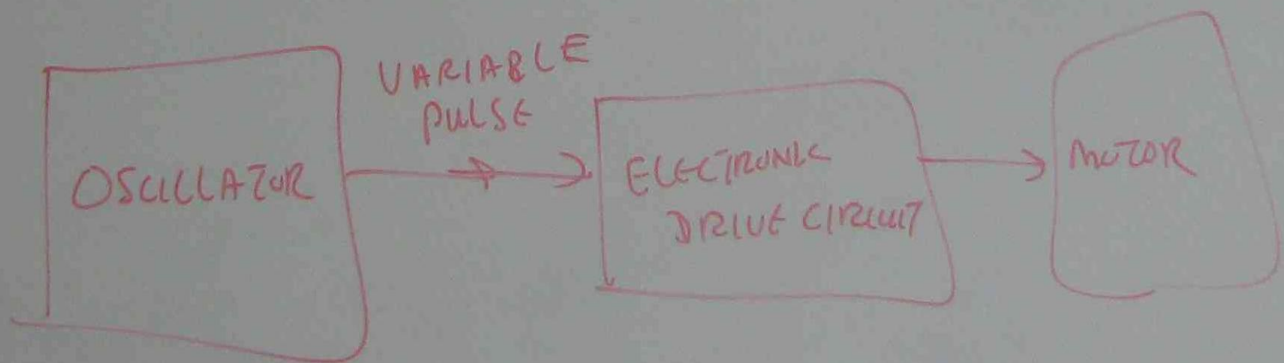

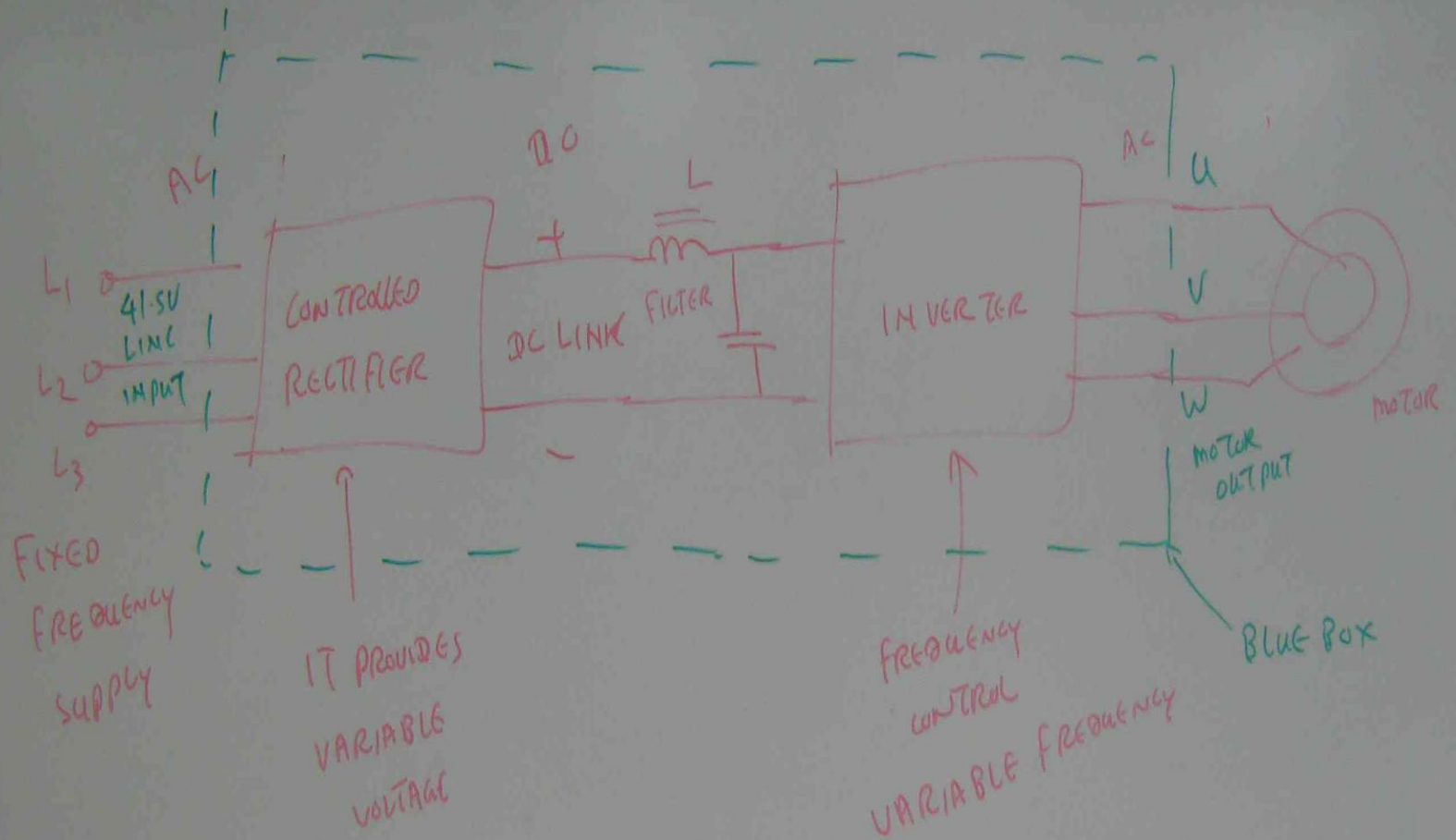

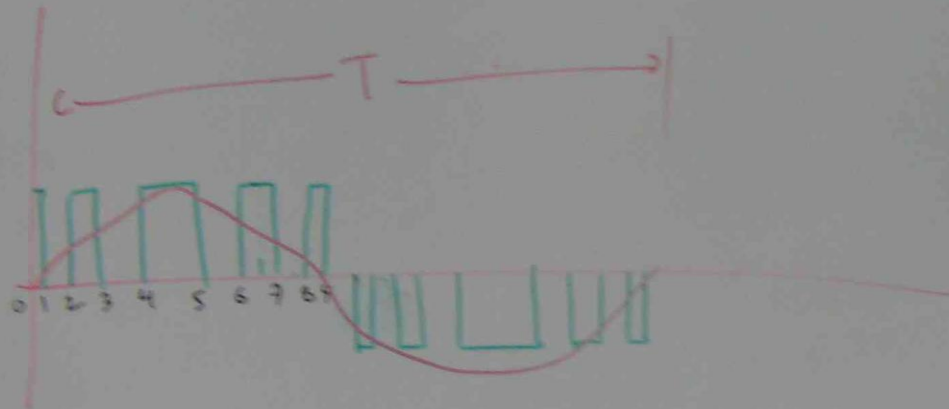PULSE WIDTH MODULATION SYSTEM \rightarrow FREQUENCY / OUTPUT VOLTAGE CONTROL



SWITCHING CIRCUITS. THEIR SWITCHING RATES ARE DIFFERENT.

$$0 \rightarrow 1 = 1 \mu s$$

$$2 \rightarrow 3 = 2 \mu s$$

$$4 \rightarrow 5 = 3 \mu s$$

$$6 \rightarrow 7 = 2 \mu s$$

$$8 \rightarrow 9 = 1 \mu s$$

By SWITCHING RATE, SINUSOIDAL OUTPUT VOLTAGE IS CREATED.

T DEPENDS ON TOTAL SWITCHING TIMES OF ELECTRONIC DEVICES

$$f = \frac{1}{T}$$

By adjusting the switching rates of electronic devices, the output frequency can be changed.

