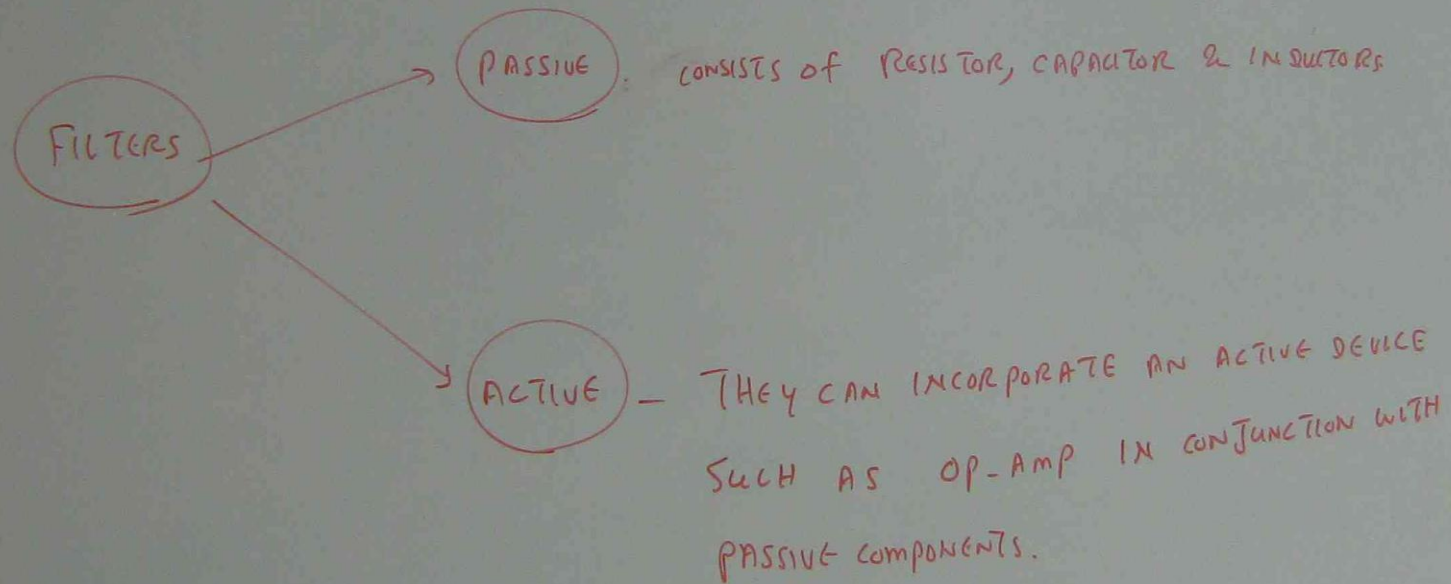


ACTIVE FILTERS

A FILTER IS A CIRCUIT DESIGNED TO PASS A SPECIFIED BAND OF FREQUENCIES AND TO REJECT OTHERS OUTSIDE THE BAND.



PRECISION CONTROL IS PROVIDED BY ACTIVE DEVICES

FREQUENCY RESPONSE OF FILTERS


(a) Low Pass

(b) High Pass


(c) Band Pass

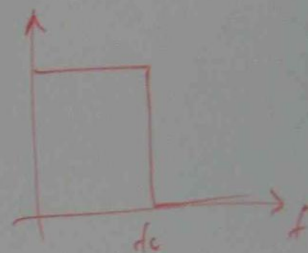(d) Band Stop Notch Filter

ACTIVE FILTER ATTENUATES THOSE FREQUENCIES OUTSIDE THE PASS BAND




(a) Low Pass FILTER

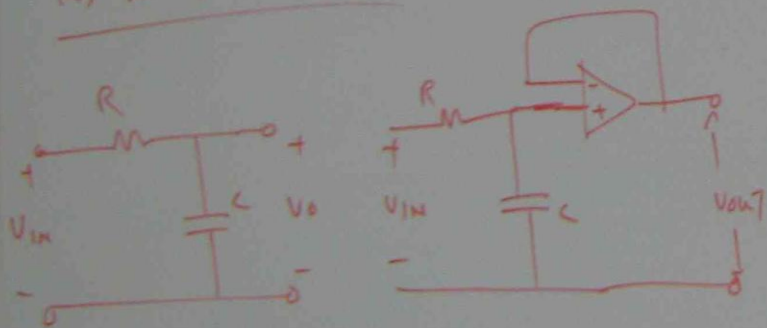


PASSIVE

ACTIVE


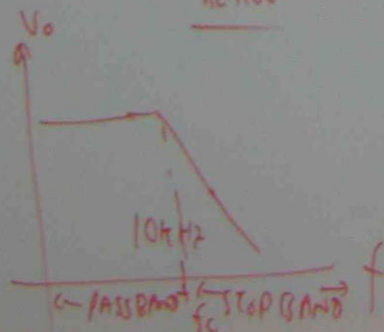


(b) HIGH PASS FILTER

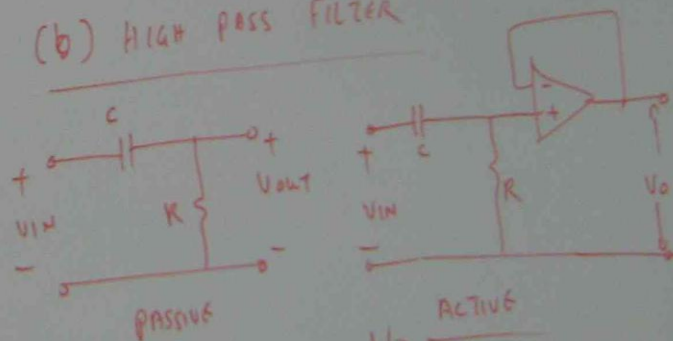

PASSIVE

ACTIVE

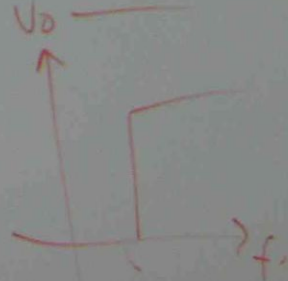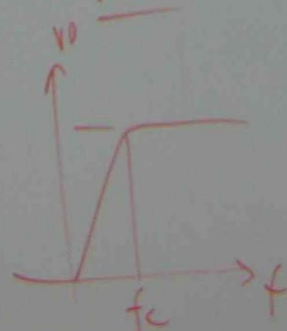


Cut off frequency $f_c = \frac{1}{2\pi\sqrt{R_0}}$

$-40 \frac{dB}{DECADE}$

FILTER CLASSIFICATION

VOLTAGE GAIN
A_v

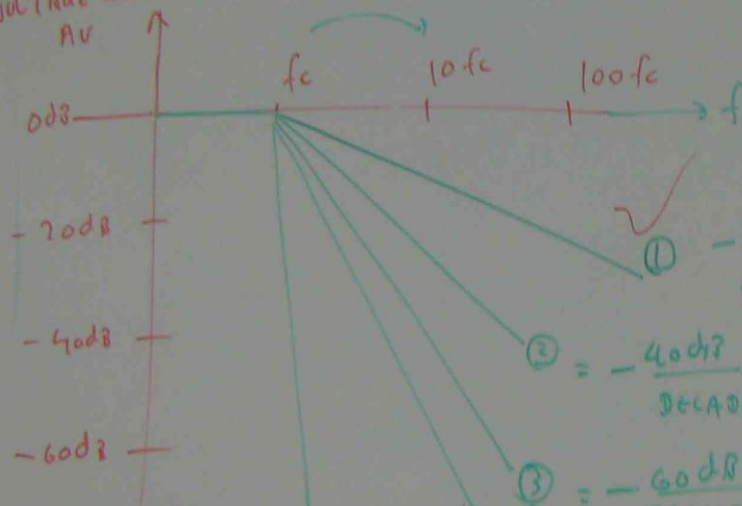




① $-20 \frac{dB}{DECADE}$ (FIRST ORDER)

② $-40 \frac{dB}{DECADE}$ (SECOND ORDER)

③ $-60 \frac{dB}{DECADE}$ (THIRD ORDER)

④ $-80 \frac{dB}{DECADE}$ (FOURTH ORDER)

⑤ IDEAL (TOTAL REJECTION)

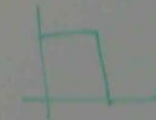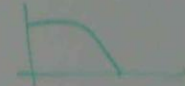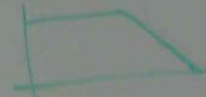



$$dB = 20 \log \frac{V_2}{V_1}$$

$$= 20 \log A_v$$

$$A_v = \frac{V_2}{V_1}$$

- 40 dB
DECADE

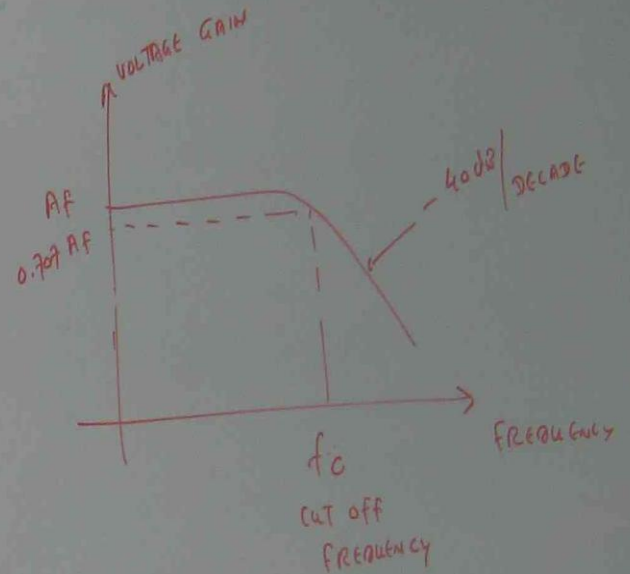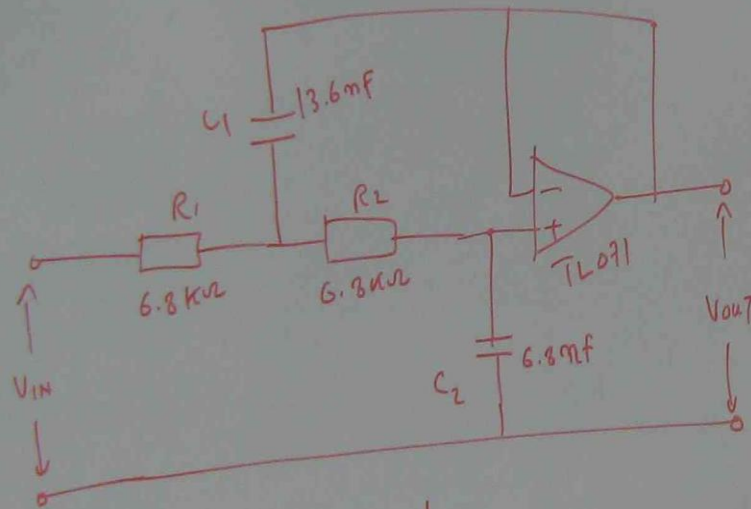THE SECOND ORDER LOW PASS BUTTERWORTH FILTER




$$f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

FOR CORRECT OPERATION

$R_1 = R_2$ AND $C_1 = 2C_2$

③ BAND PASS FILTER

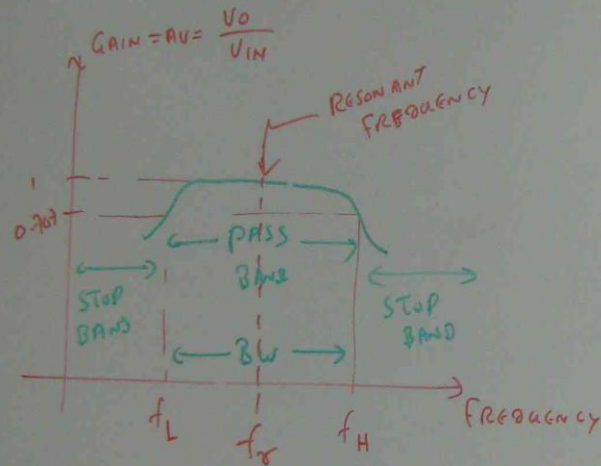


$$\text{Band width (BW)} = f_H - f_L$$



$$\text{Q Factor} = \text{Quality Factor} = \frac{\text{Resonant Frequency}}{\text{Band width}}$$

$$Q = \frac{f_r}{BW}$$

④ BAND STOP FILTER


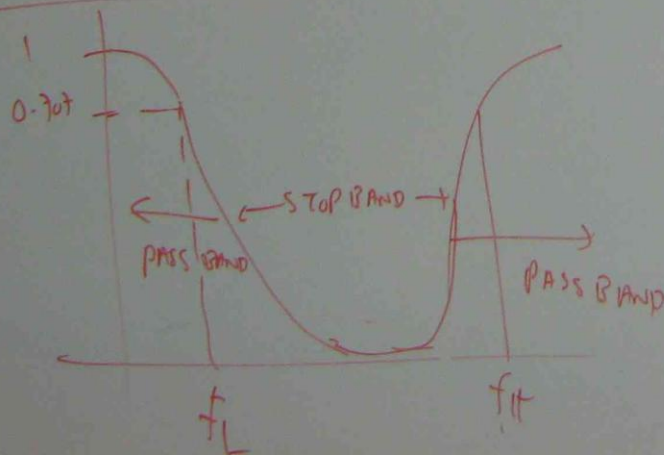


SECOND ORDER BAND PASS FILTER

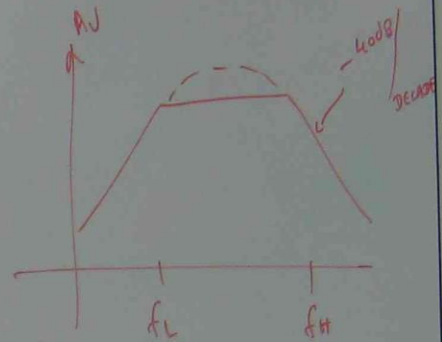
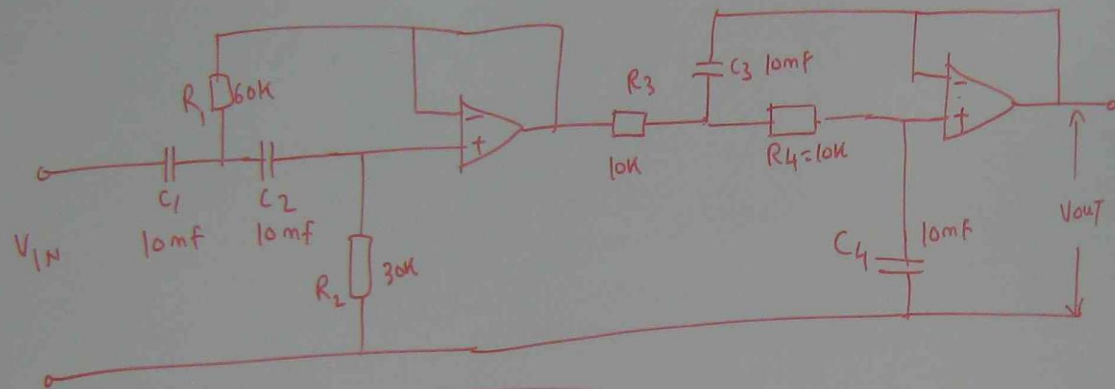


$$f_c = \sqrt{f_L \times f_H}$$

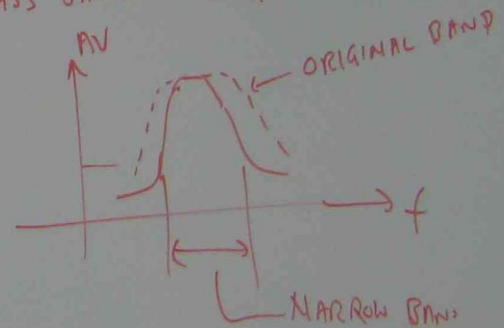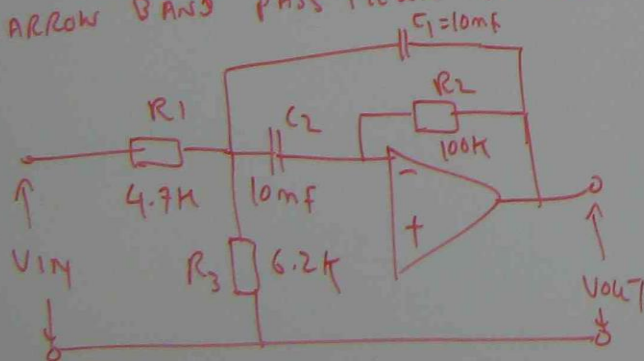IN PRECISION CONTROL SYSTEM, IT NEEDS TO NARROW THE PASS BAND. MULTIPLE FEED BACK NARROW BAND PASS FILTER IS REQUIRED.




BAND STOP (NOTCH) FILTER

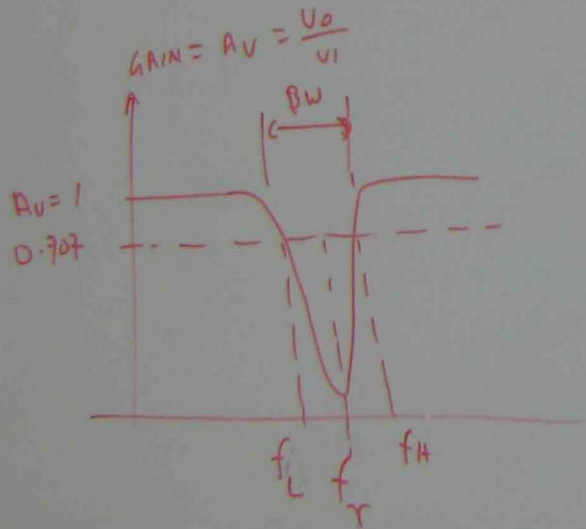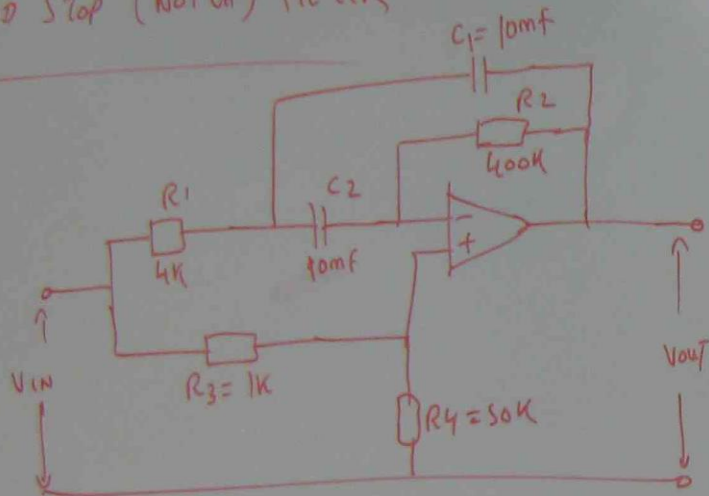

THE BAND STOP FILTER ALSO CALLED NOTCH FILTER IS USED TO REJECT AN UNWANTED FREQUENCY.


Pb ①

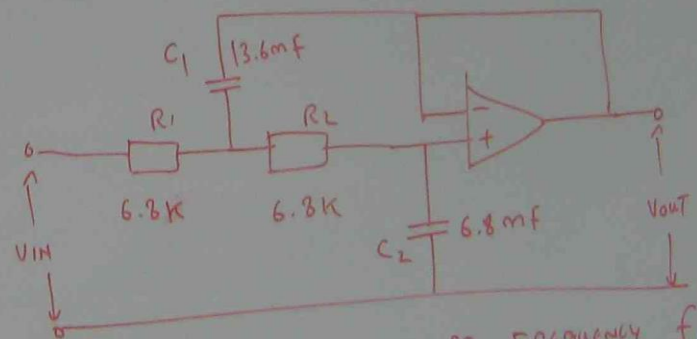- CALCULATE THE CUT-OFF FREQUENCY f_H
- SKETCH THE FREQUENCY RESPONSE, INDICATING THE RELATIVE OUTPUT LEVELS




Pb ②

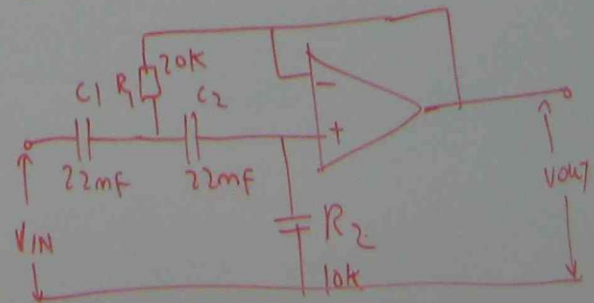- CALCULATE THE CUT OFF FREQUENCY f_L
- SKETCH THE FREQUENCY RESPONSE



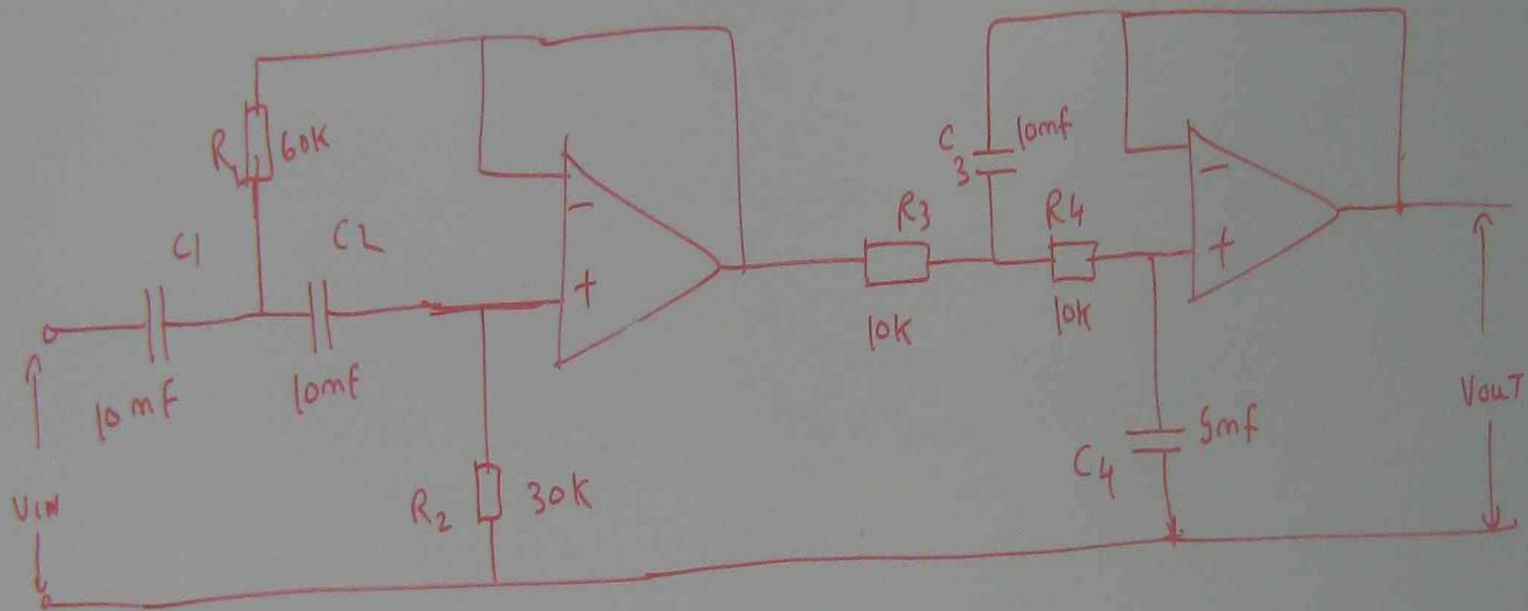- Prob 3
- (a) CALCULATE THE CUT OFF FREQUENCIES f_L AND f_H
- (b) SKETCH THE FREQUENCY RESPONSE, INDICATING THE RELATIVE OUTPUT LEVELS f_L, f_H



Prob 1 2nd ORDER LOW PASS BUTTERWORTH FILTER

$$f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$


$$= \frac{1}{2 \times 3.14 \sqrt{6.8 \times 10^3 \times 6.8 \times 10^3 \times 3.6 \times 10^{-9} \times 6.8 \times 10^{-9}}}$$

$$= \frac{1}{6.28 \sqrt{4276.2 \times 10^{12}}}$$

$$= \frac{1}{6.28 \times 65.39 \times 10^{-6}}$$

$$= \frac{1}{410} \times 10^6 = \frac{1000 \times 10^3}{410}$$

$$= 2.43 \text{ kHz}$$

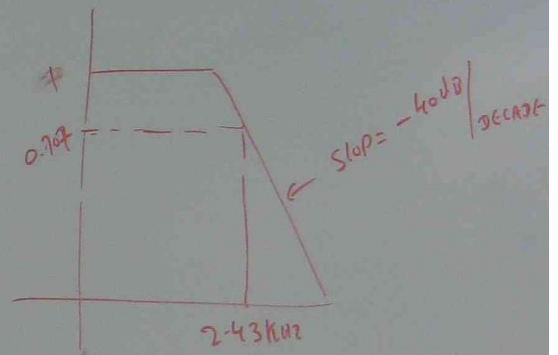

Q2) 2nd ORDER HIGH PASS BUTTERWORTH FILTER

$$f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$= \frac{1}{6.28 \sqrt{20 \times 10^3 \times 10 \times 10^3 \times 22 \times 10^{-9} \times 22 \times 10^{-9}}}$$


$$= \frac{1}{6.28 \sqrt{96800 \times 10^{-12}}}$$

$$= \frac{1}{6.28 \times 311 \times 10^{-6}}$$


$$= \frac{10^6}{1953} = \frac{1000 \times 10^3}{1953}$$

$$= 0.5 \text{ kHz}$$

$$= 500 \text{ Hz}$$

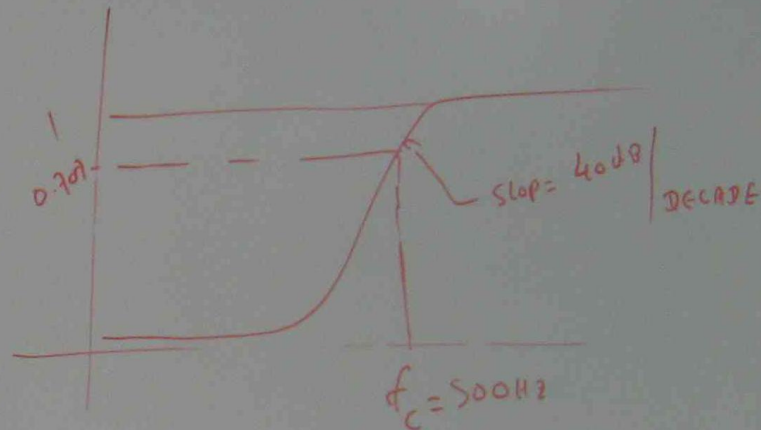

pb3

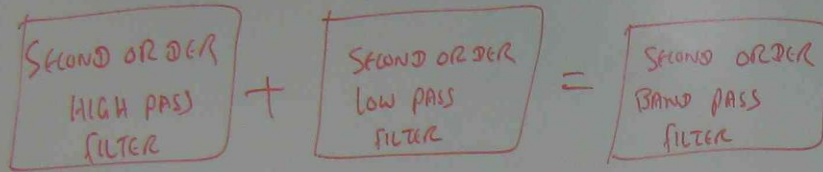

$$f_1 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$= \frac{1}{6.28 \sqrt{60 \times 10^3 \times 30 \times 10^3 \times 10 \times 10^{-9} \times 10 \times 10^{-9}}}$$

$$= \frac{1}{6.28 \sqrt{180000 \times 10^{-12}}}$$

$$= \frac{10^6}{6.28 \times 424.26}$$

$$= \frac{1000 \times 10^3}{2654} = 0.375 \text{ kHz}$$

$$f_L = 375 \text{ Hz}$$

$$f_2 = \frac{1}{2\pi \sqrt{R_3 R_4 C_3 C_4}}$$

$$= \frac{1}{6.28 \sqrt{10 \times 10^3 \times 10 \times 10^3 \times 10 \times 10^{-9} \times 5 \times 10^{-9}}}$$

$$= \frac{1}{6.28 \sqrt{5000 \times 10^{-12}}}$$


$$= \frac{10^6}{444}$$

$$= \frac{1000 \times 10^3}{444}$$

$$f_H = 2.25 \text{ kHz}$$

$$\log 375 =$$


$$\log 2250 =$$

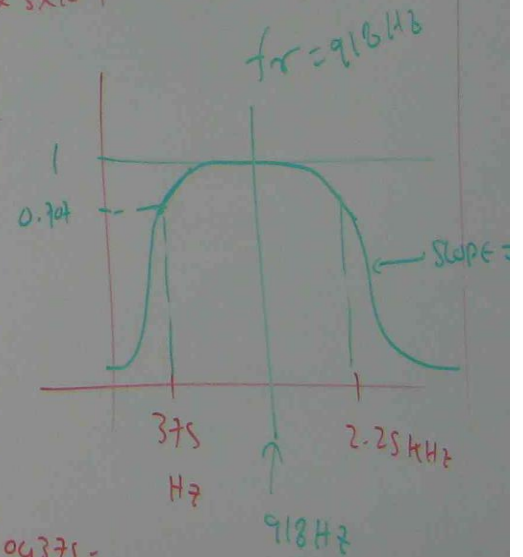

pb ②

(a) CALCULATE THE CUT OFF FREQUENCIES f_L AND f_H

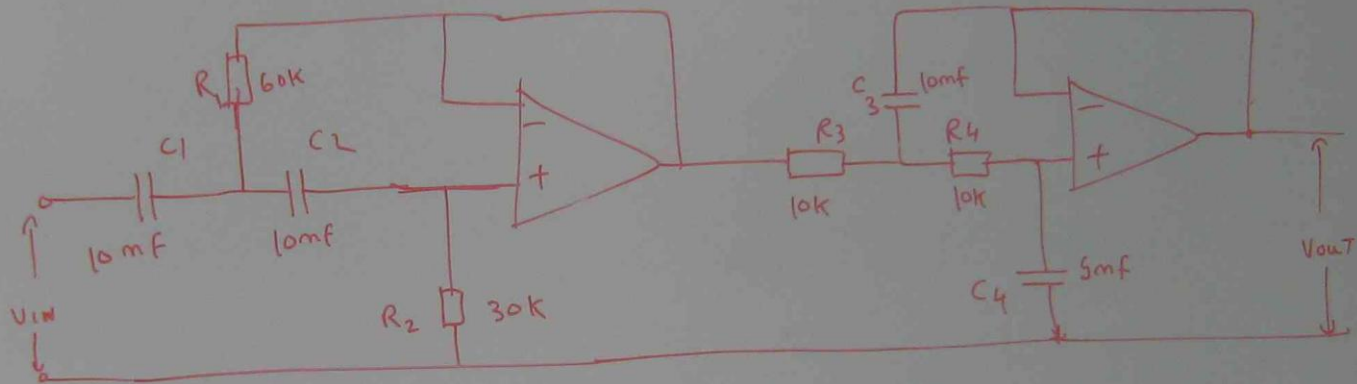(b) SKETCH THE FREQUENCY RESPONSE, INDICATING THE RELATIVE OUTPUT LEVELS f_L, f_H



SLLOPE = 40dB/
DC-GAIN

$$f_c = \sqrt{f_L \times f_H}$$


$$= \sqrt{375 \times 2250}$$

$$= 918 \text{ Hz}$$

Hz

MULTI STAGE OP-AMP CIRCUITS

LIGHT LEVEL INDICATOR

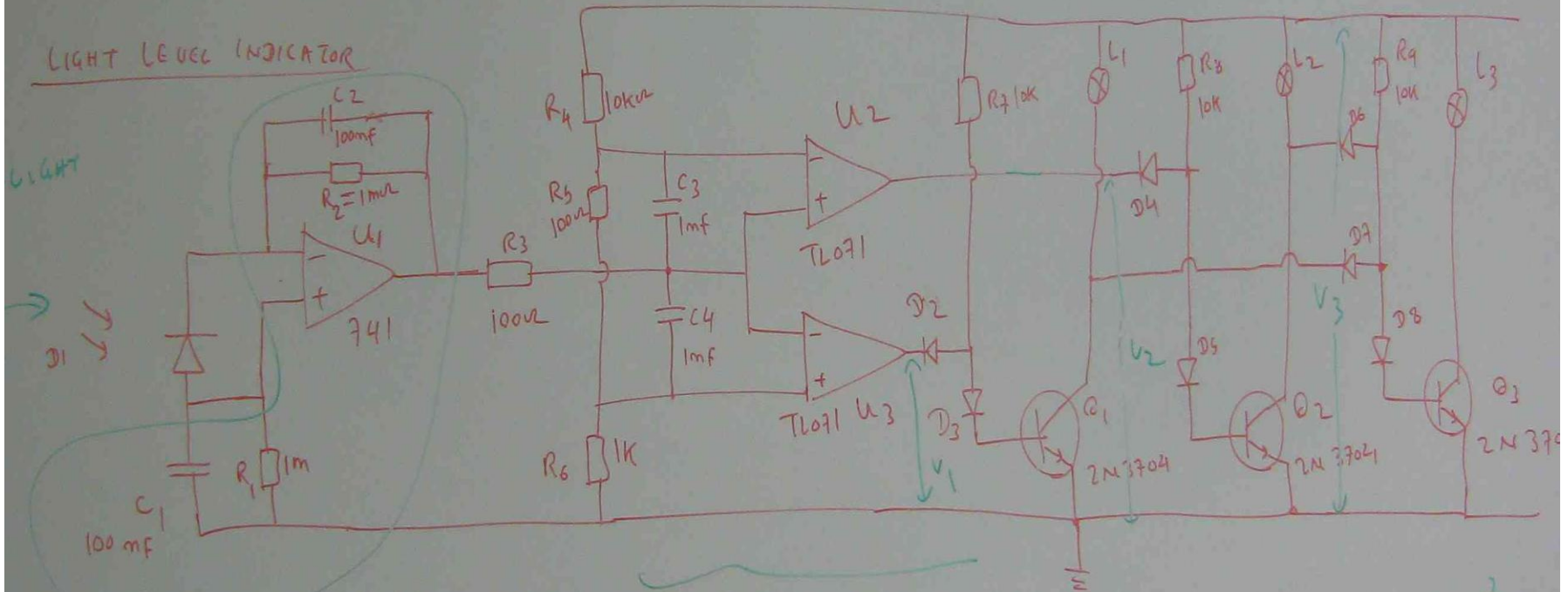

(2) U_1 - LOW PASS FILTER

CURRENT \rightarrow VOLTAGE CONVERTER

COMPARISON (3)

(4) LIGHT DRIVERS. SWITCHES FOR LAMPS.

(1) PHOTO DIODE D_1 CONVERTS THE LIGHT TO ELECTRICAL SIGNAL CURRENT

(2) LOW PASS FILTER U_1 PREVENTS THE HIGH FREQUENCIES. IT ACTS AS LOW PASS FILTER / CONVERTS THE CURRENT TO VOLTAGE.

(3) OP-AMP U_2, U_3 ACT AS COMPARATORS. DEPENDING ON OUTPUT,

(4) THE DRIVER TRANSISTORS Q_1, Q_2, Q_3 SWITCH ON THE LAMPS
 L_1, L_2 AND L_3

DIODES D_4, D_6, D_7 PREVENTS REVERSED CURRENT FLOWS.

DIODES D_3, D_5, D_8 DIRECT THE BIASING CURRENTS INTO TRANSISTORS.


LIGHT LEVEL TOO LOW OR HIGH ARE INDICATED BY L_1, L_2, L_3

SAMPLE AND HOLD CIRCUIT

SAMPLE & HOLD

DIFFERENTIATOR

COMPARATOR

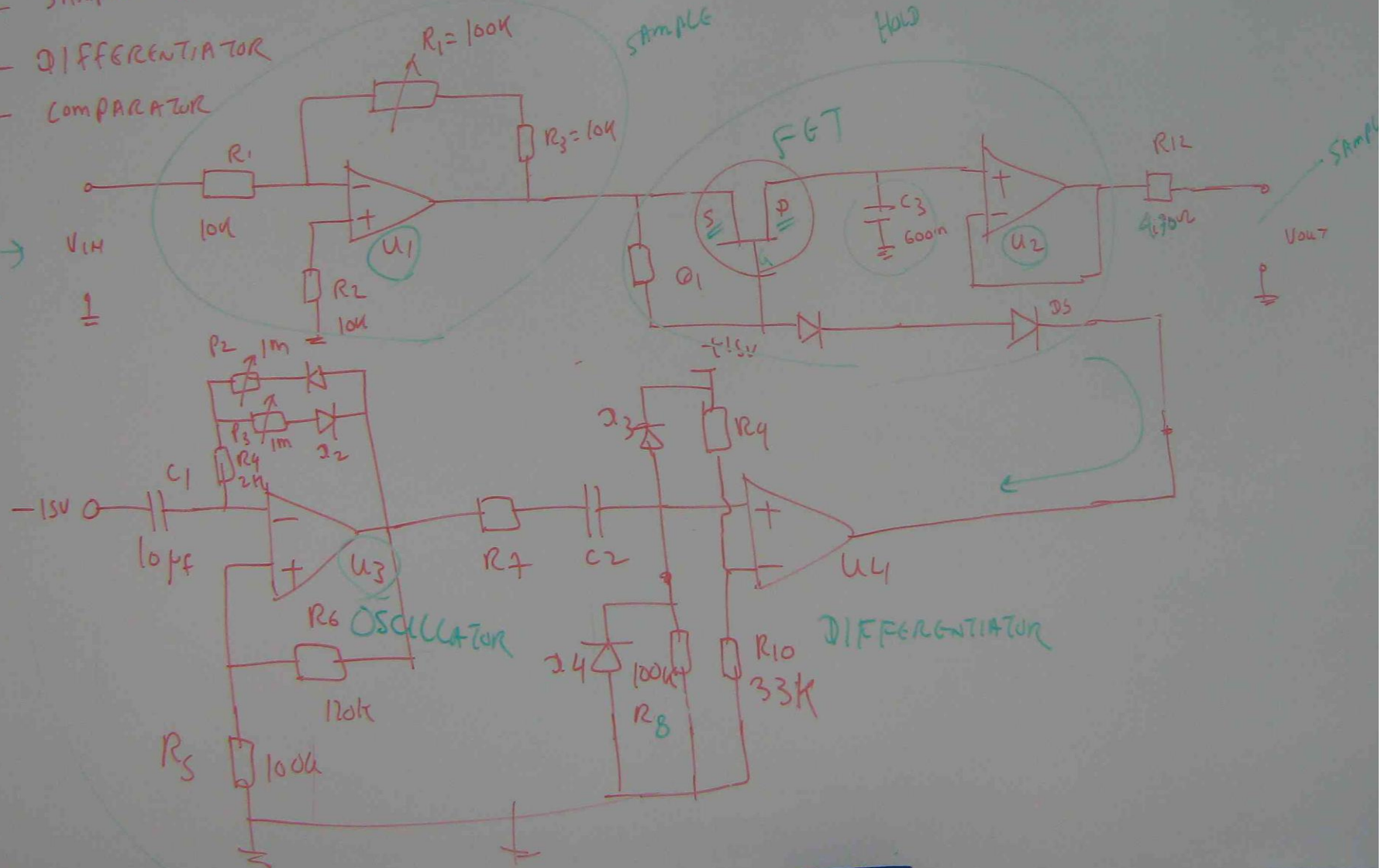

OP-AMP U_1 AND U_2 PROCESS THE DC INPUT VOLTAGE AND PRESENT THE
SAMPLE LEVEL AT THE OUT PUT OF U_2

OP-AMP U_3 IS OSCILLATOR. ITS OUTPUT IS APPLIED TO
DIFFERENTIATOR U_4 .

OP-AMP U_4 IS WIRED AS COMPARATOR

THE OUT PUT OF COMPARATOR SWITCHES THE REVERSING DIODE D_S .

UNDER THESE CONDITION, THE GATE/SOURCE VOLTAGE OF FET Q_1 WILL EQUAL 0V.

CAUSING C_3 TO CHARGE TO OUT PUT LEVEL OF Q_1 .

THE OUT PUT OF U_4 QUICKLY SWITCHES NEGATIVE AGAIN, FORWARD-BIASING D_S & TURN OF FET

SAMPLE AND HOLD CIRCUIT

- Sample & Hold
- DIFFERENTIATOR
- COMPARATOR

