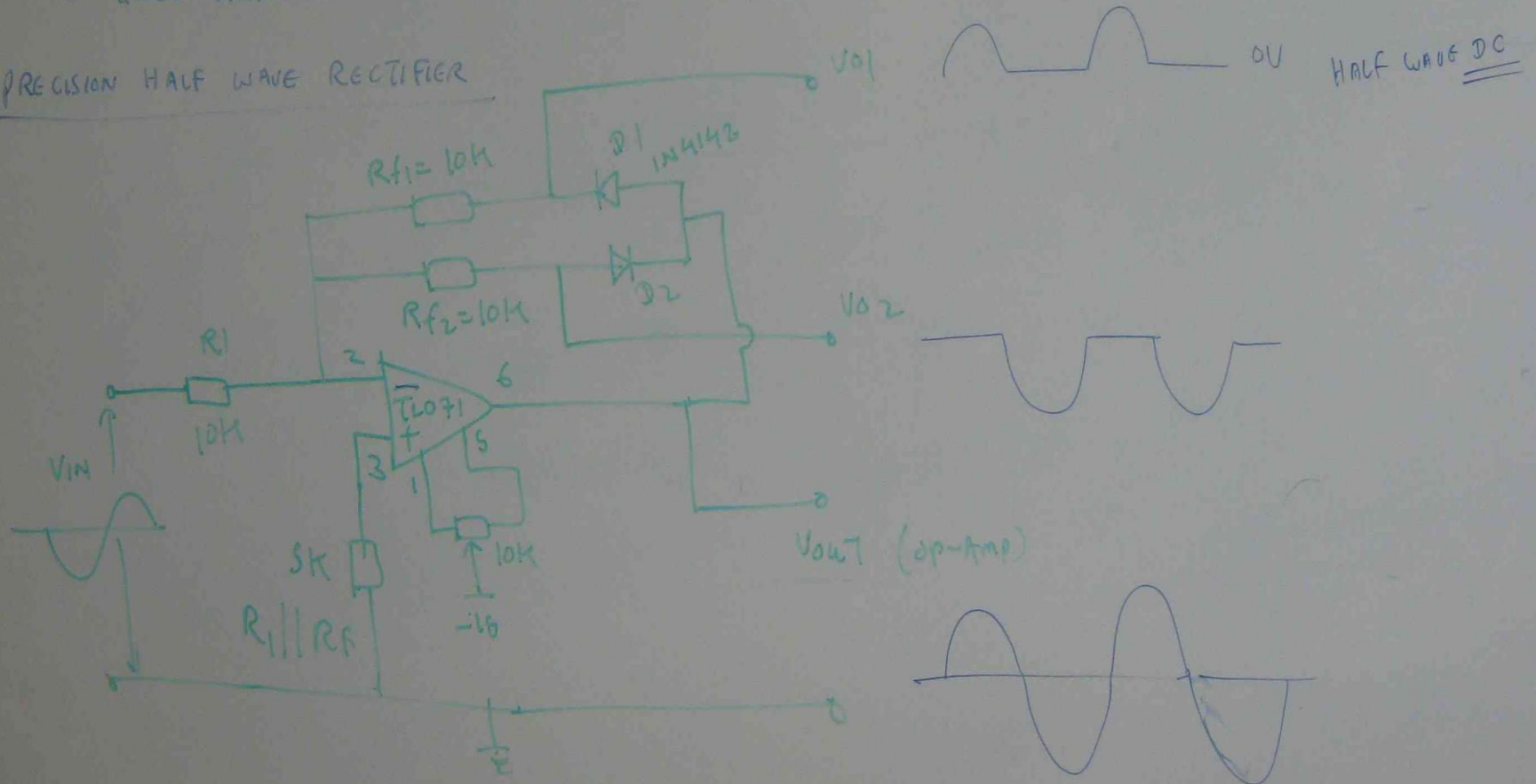


OP-AMP DIODE CIRCUITS


THERE ARE A WIDE RANGE OF OP-AMP CIRCUITS THAT USE DIODES IN THE FEED BACK PATH. IN GENERAL, THESE CIRCUITS FALL INTO TWO BROAD CATEGORIES.

- PRECISION RECTIFIERS
- DIODE LIMITERS.

PRECISION HALF WAVE RECTIFIER



PRECISION FULL WAVE RECTIFIER

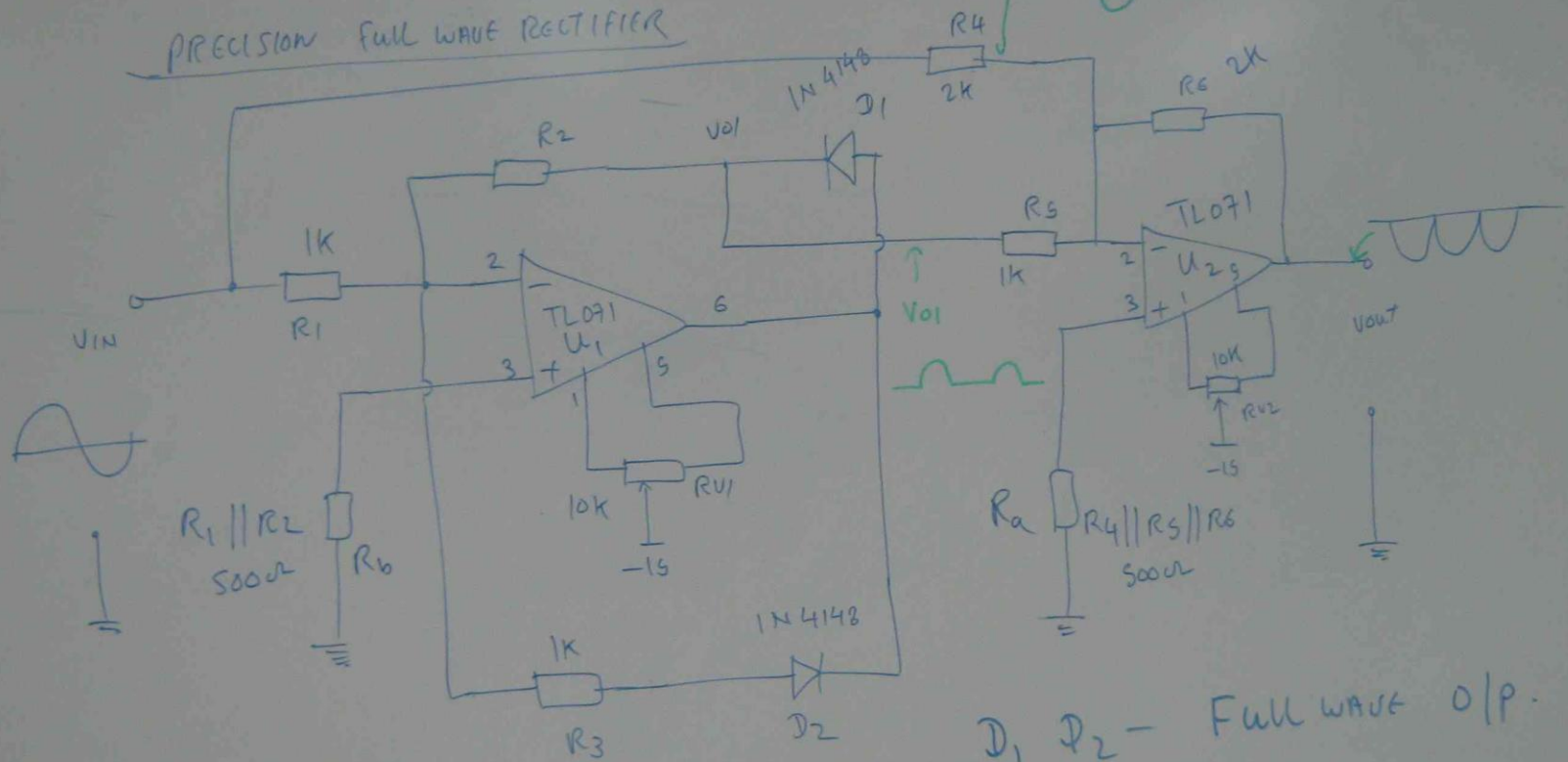

R_{V1} = OFFSET ADJUSTING
RESISTOR

D_1, D_2 - Full wave O/P.
 R_1, R_3 - INPUT INTO - TERMINAL
 R_4, R_6 - FEEDBACK RESISTOR
(TO MAINTAIN THE GAIN
STABILITY)

A PRECISION FULL WAVE RECTIFIER CAN BE CONSTRUCTED USING A SUMMING INVERTER WITH ONE OF ITS INPUTS CONNECTED TO AN OUTPUT OF A PRECISION HALF WAVE RECTIFIER.

$$\frac{1}{R_a} = \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6}$$


$$\frac{1}{R_b} = \frac{1}{R_1} + \frac{1}{R_2}$$

↑
COMPENSATION


THE RELATIONSHIP BETWEEN INPUT AND OUTPUT SIGNALS OF A CIRCUIT CAN BE

GRAPHICALLY REPRESENTED BY A
TRANSFER CURVE.

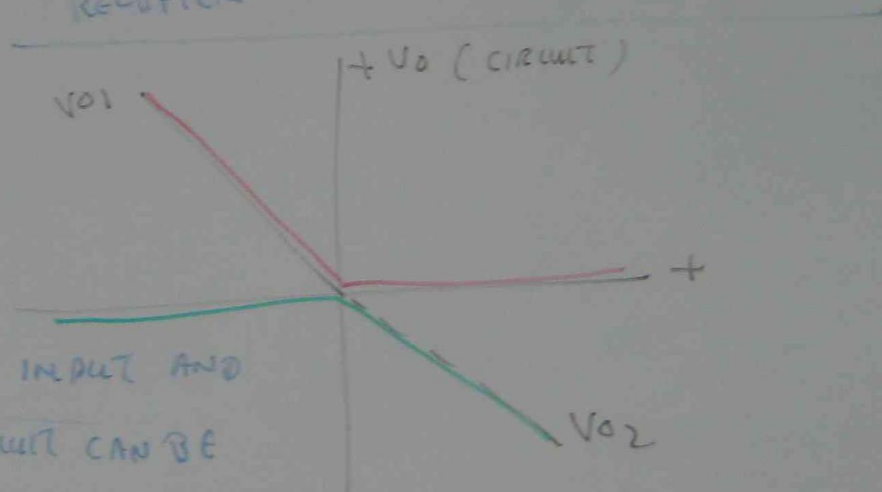TRANSFER CHARACTERISTICS OF THE HALF WAVE
RECTIFIER






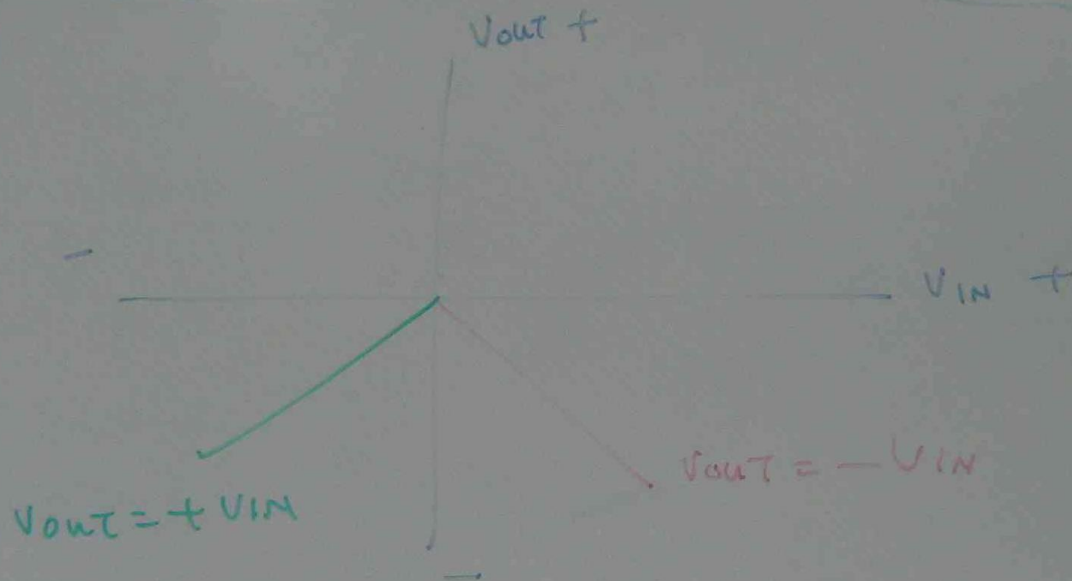
FULL WAVE PRECISION RECTIFIER TRANSFER CHARACTERISTICS






LIMITING CIRCUITS

A LIMITING CIRCUIT (ALSO CALLED A CLIPPING CIRCUIT) LIMITS THE OUTPUT SIGNAL TO PRECISE LIMITS. TO ACHIEVE THIS, ZENER DIODES ARE TO BE INCLUDED IN FEEDBACK PATH.



UNI POLAR LIMITER

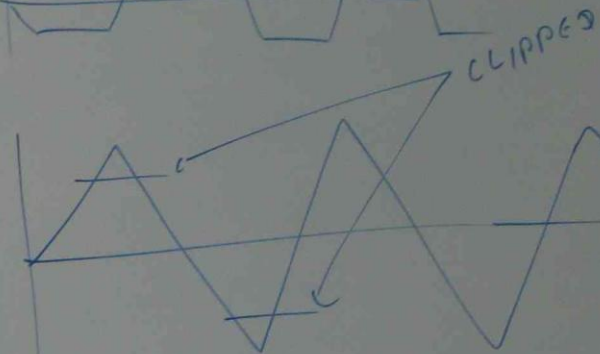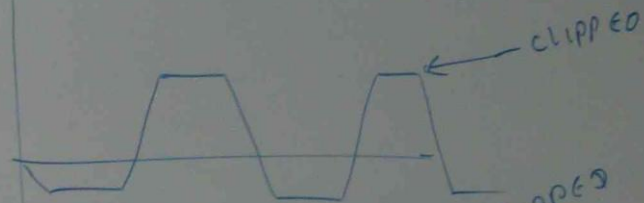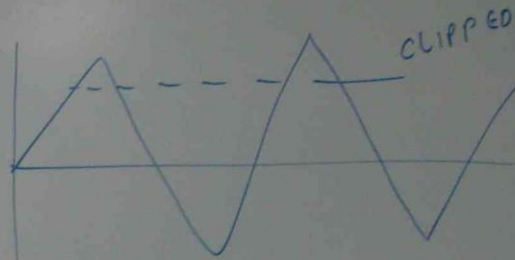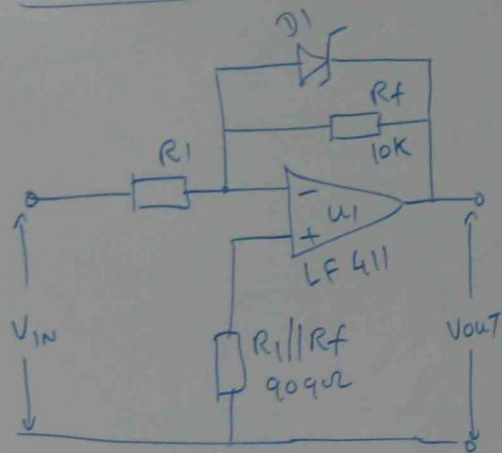



BIPOLAR LIMITER

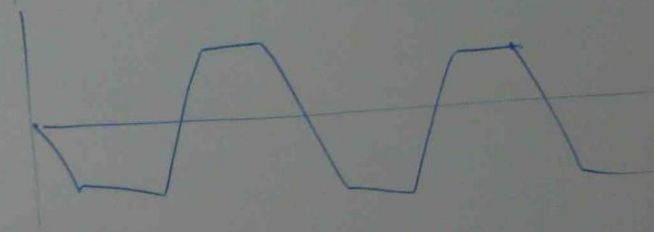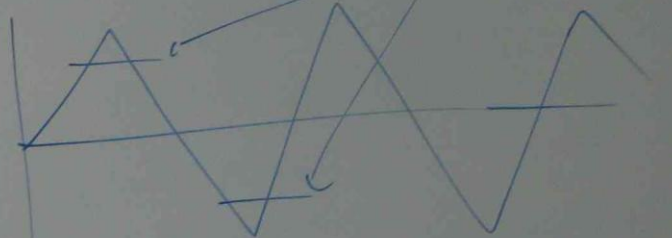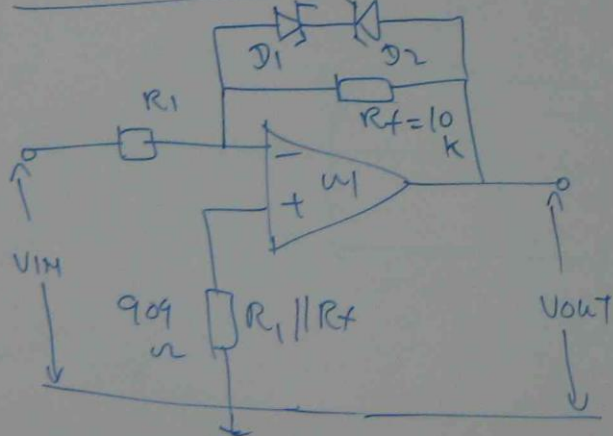

PRECISION CLIPPER

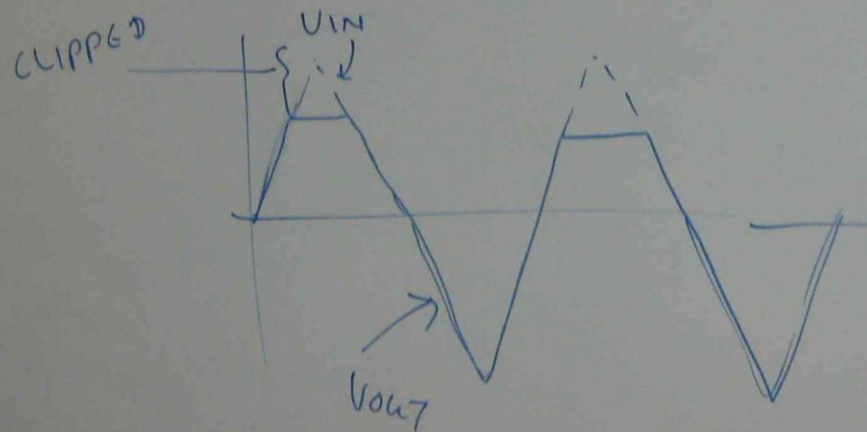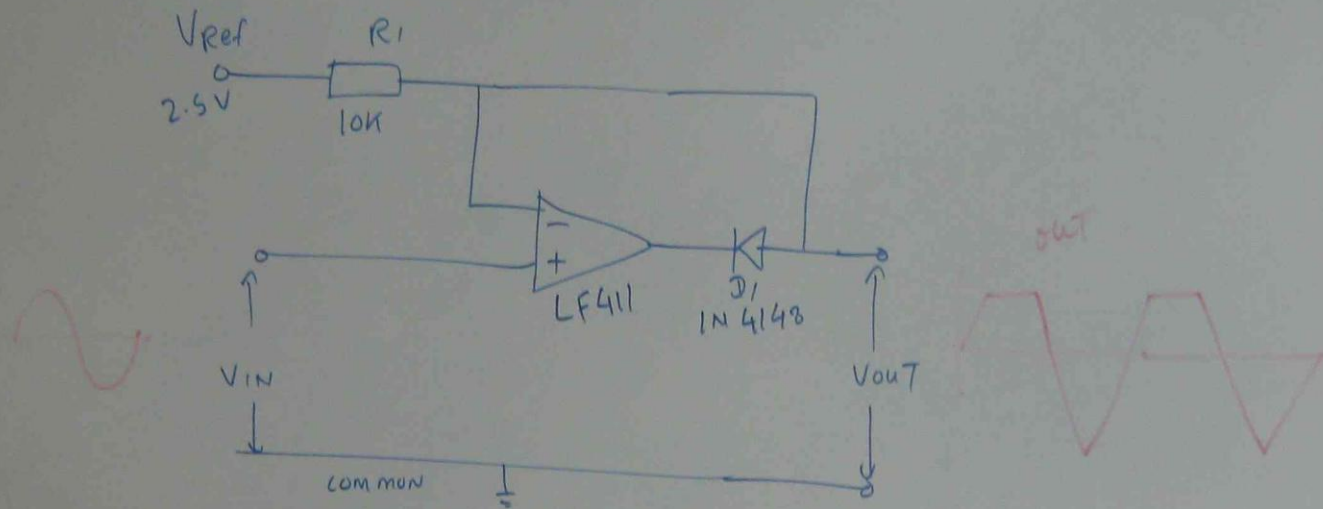

PEAK DETECTOR

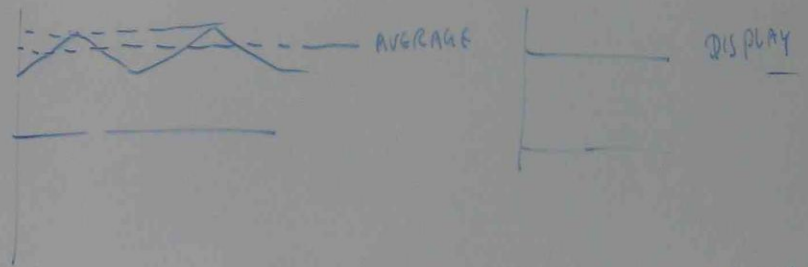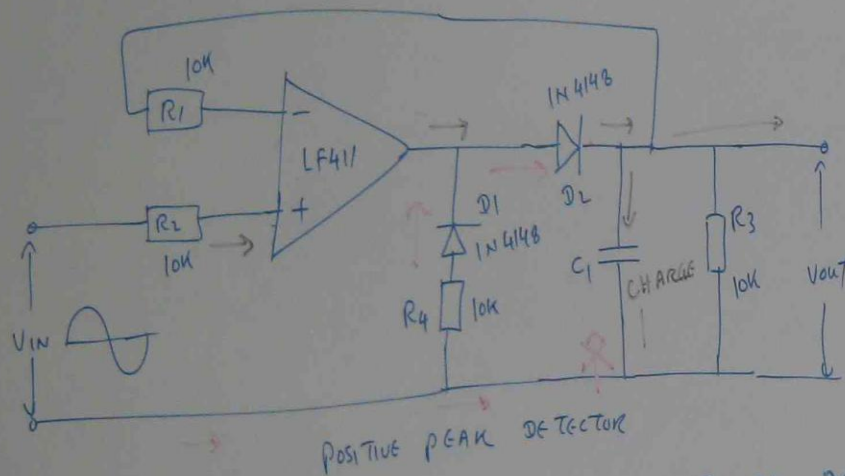


C_1 IS CHARGED


- A CONVENTIONAL AC VOLT METER IS USUALLY CALIBRATED TO DISPLAY THE RMS VALUE OF A SINE WAVE. THE PEAK DETECTOR ALLOWS A METER TO DISPLAY THE PEAK VALUE OF A WAVE FORM.
- DURING POSITIVE CYCLE, CAPACITOR C_1 IS CHARGED. IN NEGATIVE CYCLE, DIODE D_2 BLOCKS THE REVERSE CURRENT FLOWS IN TO CAPACITOR.
- THE CAPACITOR MAINTAINS THE PEAK VALUE OF VOLTAGE.
- THE PEAK VALUE IS FED TO OUTPUT DISPLAY.

SINE AND SQUARE WAVE OSCILLATORS

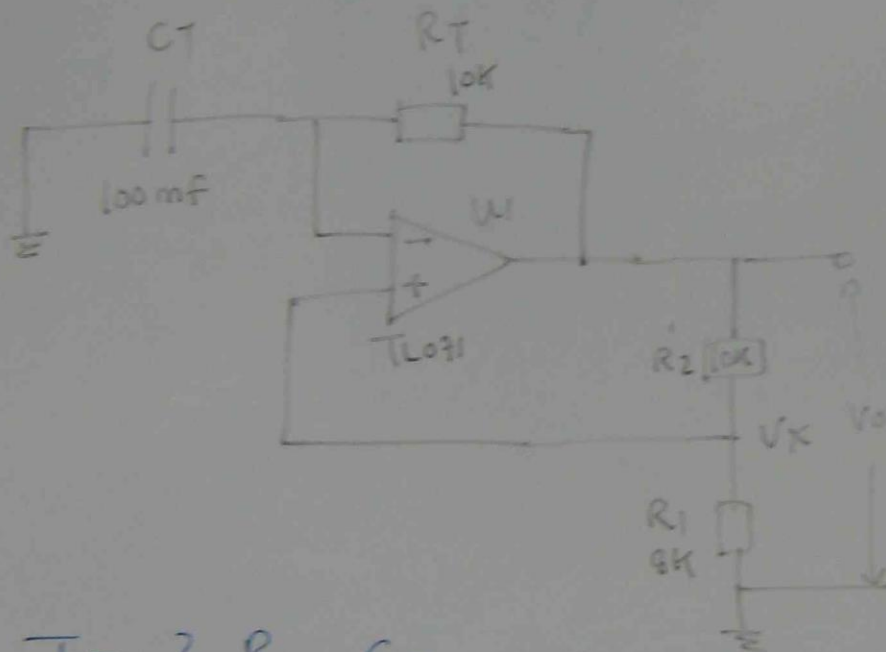THE OP-AMP ASTABLE CIRCUIT PRODUCES SQUARE WAVE OUT PUT.



SYMMETRICAL

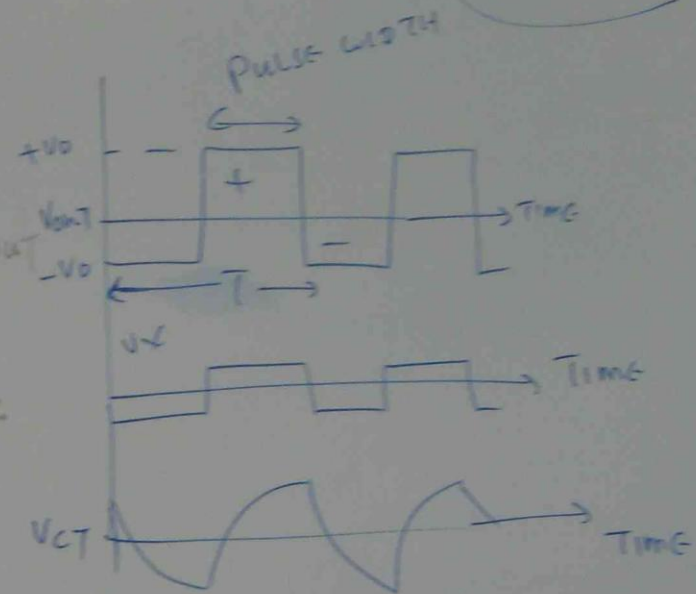


$$T = 2 R_T C_T$$

$$f = \frac{1}{2 R_T C_T}$$

+ , - WAITS PORTIONS HAVE THE SAME PULSE WIDTHS.


NON SYMMETRICAL ASTABLE CIRCUIT

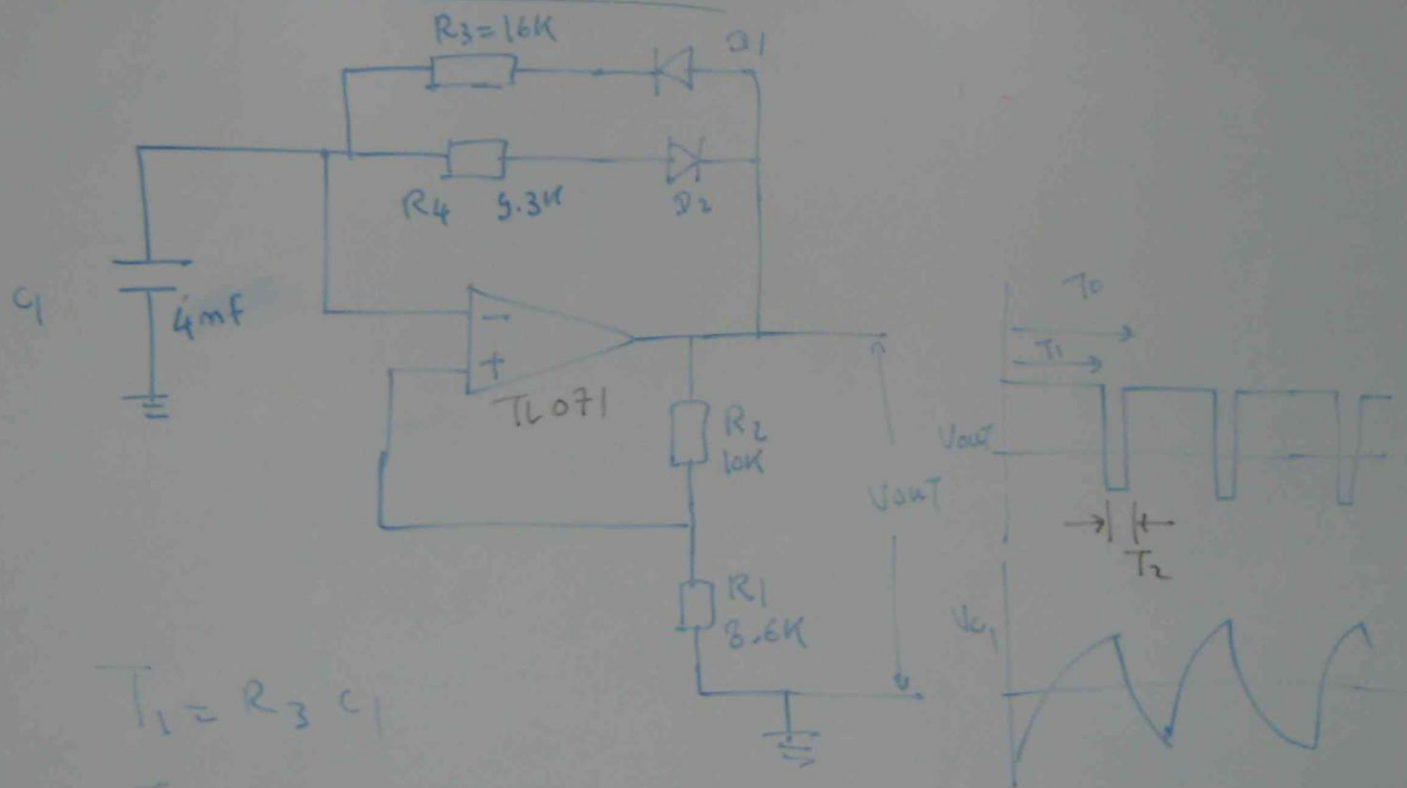

$$T_1 = R_3 C_1$$

$$T_2 = R_4 C_1$$

THE PHASE SHIFT OSCILLATOR


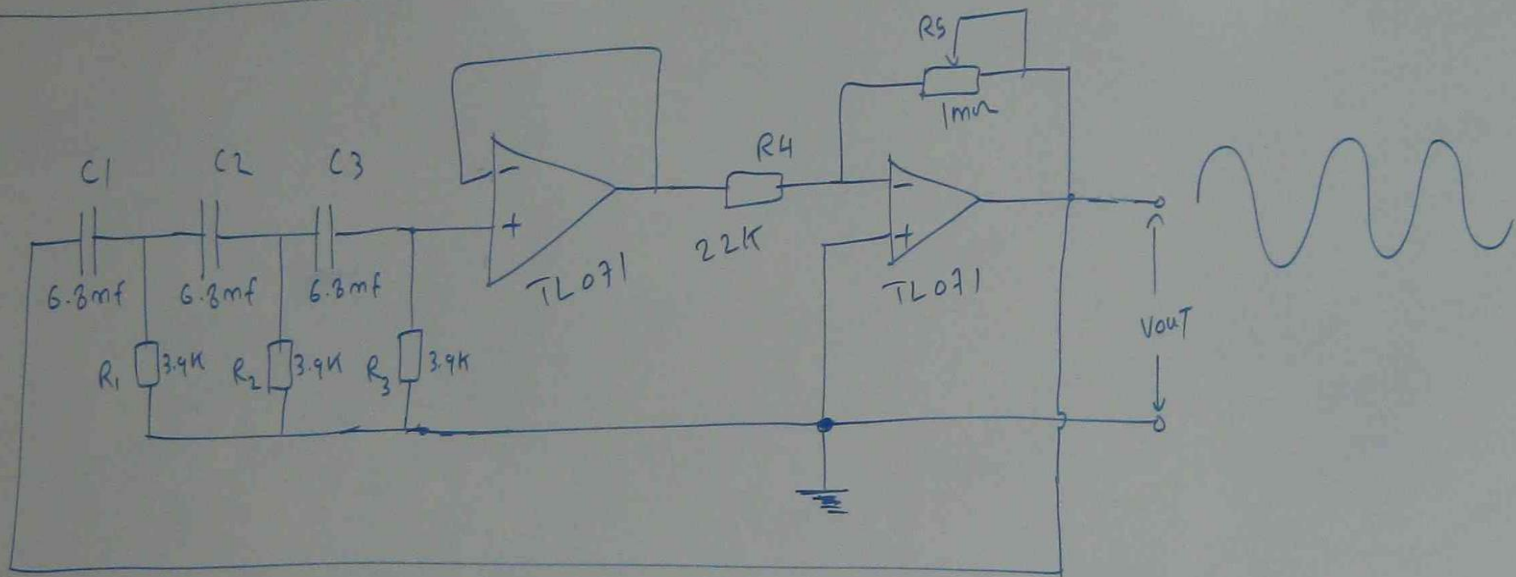


$$f_0 = \frac{1}{15.4 R C}$$

$$R = R_1 = R_2 = R_3$$


$$C = C_1 = C_2 = C_3$$

OP-AMP RC CIRCUITS

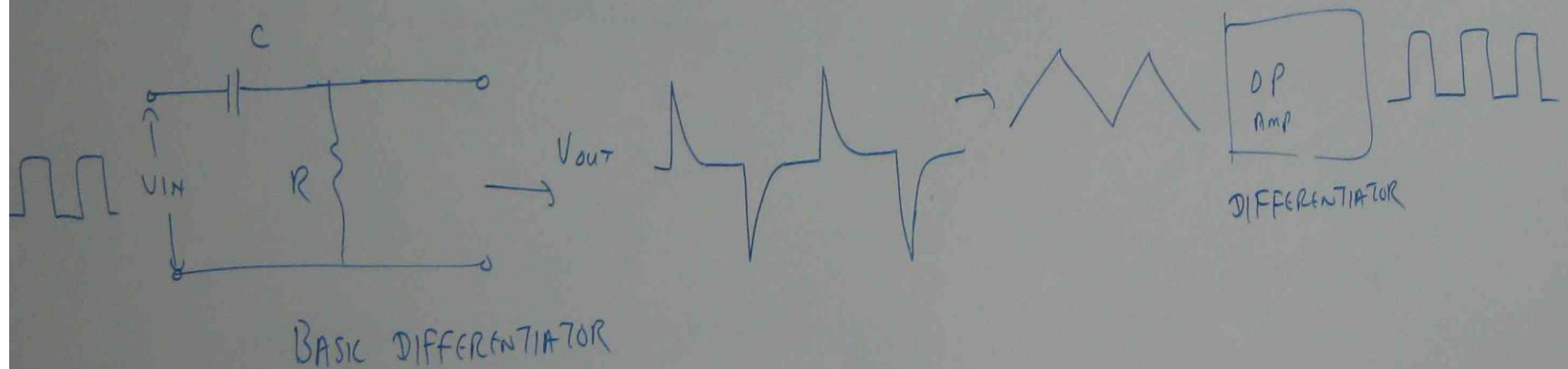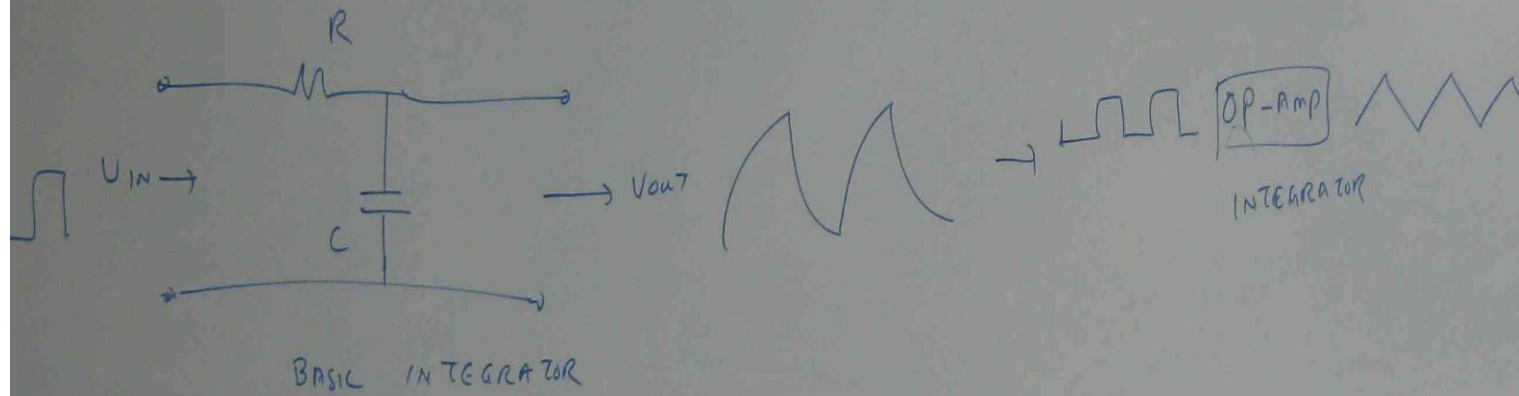

RC CIRCUITS CAN CONVERT SQUARE WAVE TO SAWTOOTH WAVE (INTEGRATOR)
AND SAWTOOTH WAVE TO SQUARE WAVE (DIFFERENTIATOR).


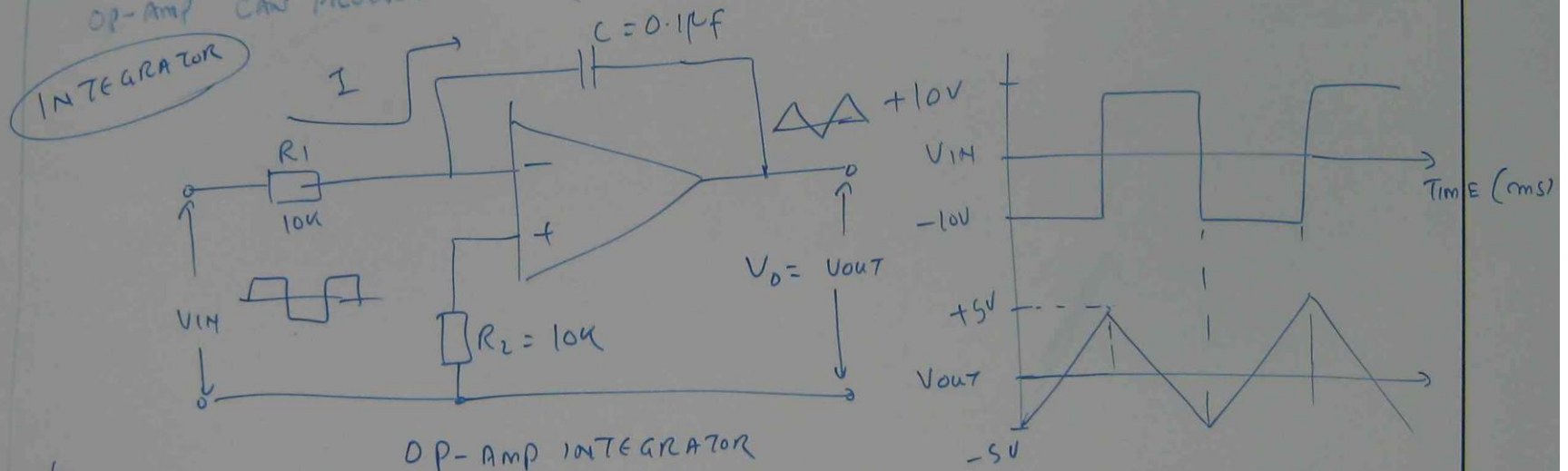
OP-AMP CAN PROVIDE FINELY ADJUSTED OUTPUT WAVE SHAPES.



$$V_O = (-) V_{IN} \times \frac{1}{R_1 C} \times \text{TIME IN SECOND}$$

$$I = \frac{V_{IN}}{R_1}$$


DIFFERENTIATOR

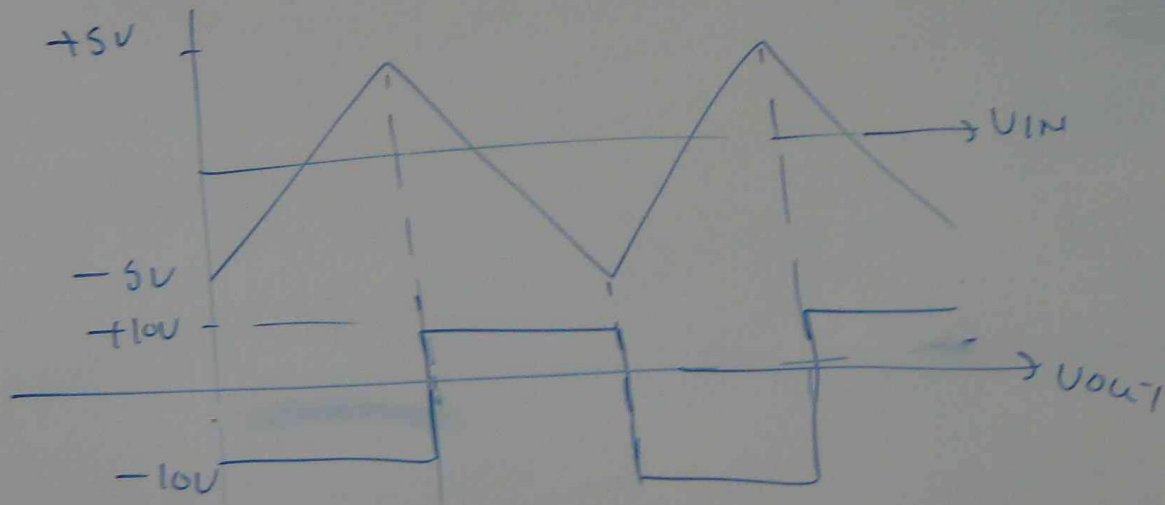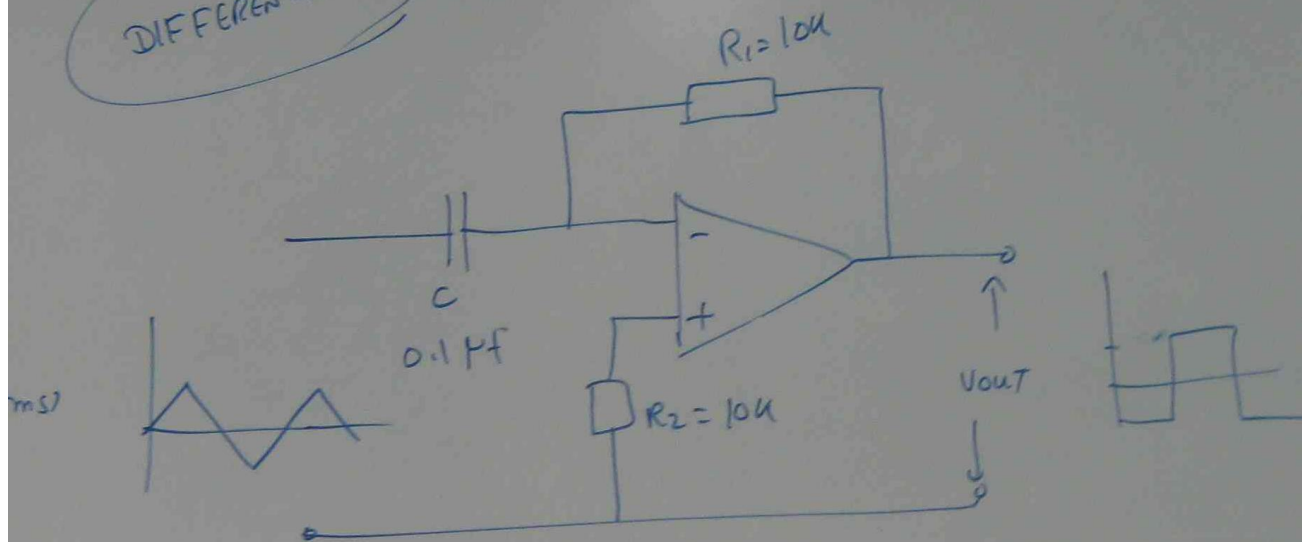

$$V_{OUT} = (-) R_1 C \times \text{RATE OF CHANGE OF } V_{IN} \left(\frac{\text{VOLTS}}{\text{SECOND}} \right)$$

pb For THE GIVEN CIRCUIT, CALCULATE THE OUTPUT VOLTAGE AFTER 2ms.

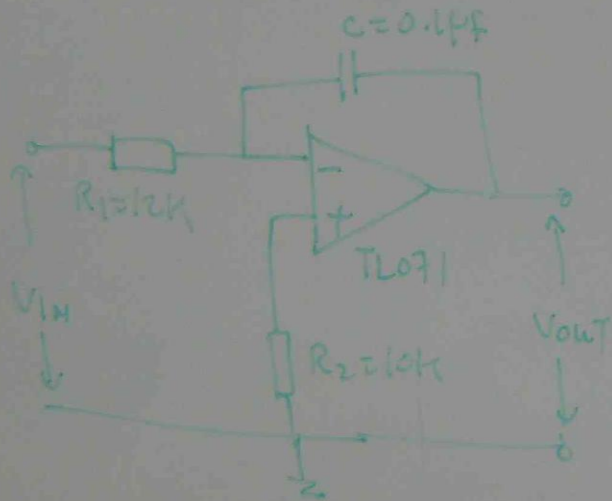IF $-5V$ IS APPLIED TO THE INPUT. ASSUME THE OUTPUT VOLTAGE WAS $0V$ PRIOR TO CONNECTING $-5V$ INPUT.



$$V_o = (-) V_{IN} \times \frac{1}{R_1 C} \times \text{Time IN SECOND}$$

$$= -(-5V) \times \frac{1}{12 \times 10^3 \times 0.1 \times 10^{-6}} \times 2 \times 10^{-3}$$

$$= \frac{5 \times 2 \times 10^{-3}}{1.2 \times 10^{-3}} = \frac{10}{1.2} = 8.3V$$

FUNCTION GENERATOR

