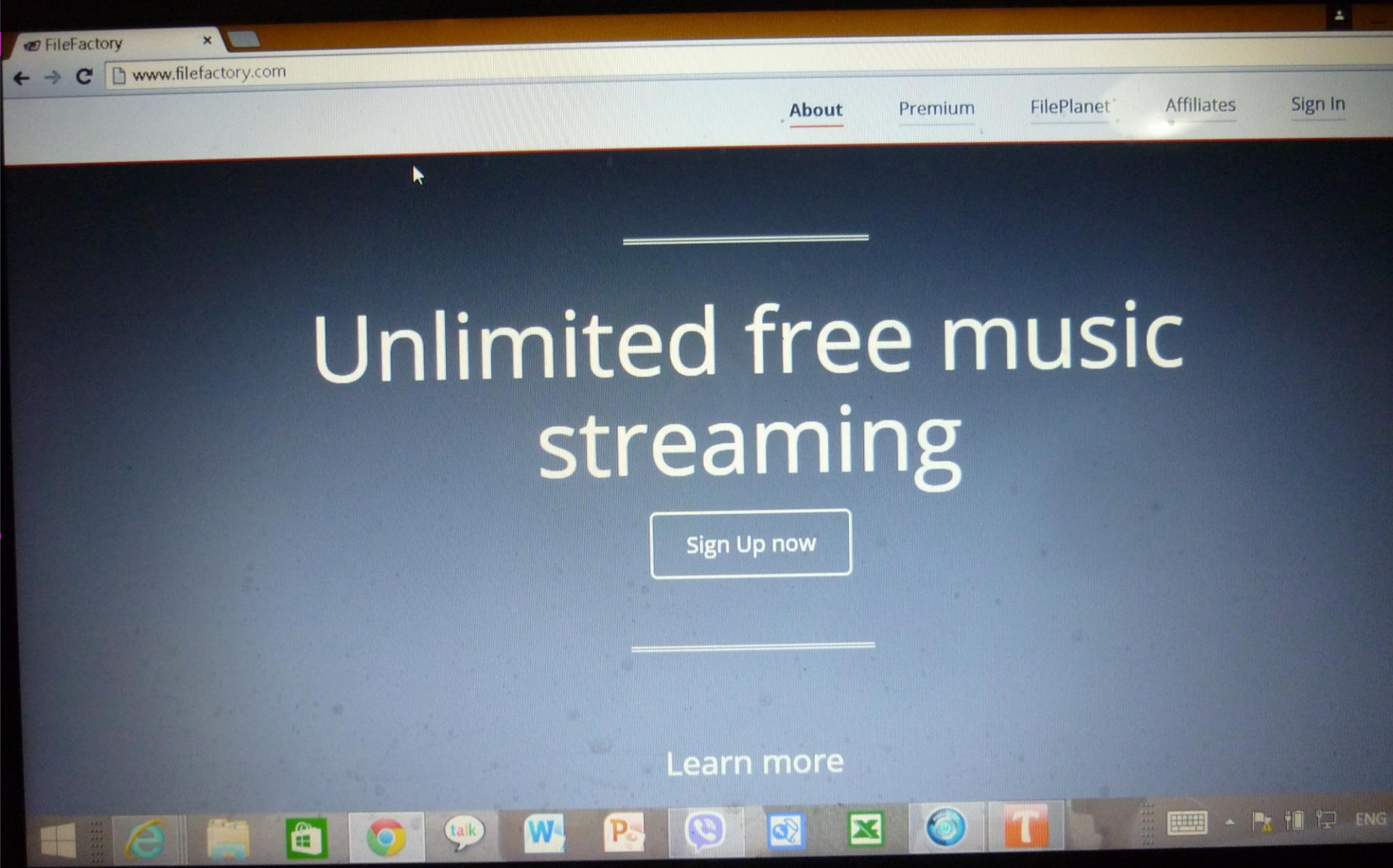




Making online lessons

Uploading the lessons to file sharing sites

www.filefactory.com



Unlimited free music streaming

Sign Up now

Learn more

ctory

www.filefactory.com/member/signin.php

[About](#)

[Premium](#)

[FilePlanet](#)

[Affiliates](#)

[Sign In](#)

If you have an existing FileFactory account and have a support issue please [visit our support portal](#) or email support@filefactory.com.

Sign In

Facebook

Twitter

Google Plus

or

Email Address

✉ kyawnaing125@yahoo.com.au

Password

🔒



My Files

Search

Upload

Account

Summary

Filebox

TrafficShare

Redeem Voucher

Social Connect

Notifications

Delete Account

Account Summary

Home

Account

Summary

You are currently signed in as **kyawnaing125@yahoo**



Account Summary

Premium

Member

62

Days R

22,440

Downloads



Download Settings

FileFactory

← → ↺

www.filefactory.com/account/

My Files

Search

Upload

Computer

Remote

FTP

Account

Products

Affiliates

Tools

Legal

Support

Account Summary

Home Account Summary

You are currently signed in as **kyawnaing125@yahoo.**

Account Summary

Premium

Member

62

Days R

22,440

Downloads

Download Settings

ON


Local Upload

Remote Upload

FTP Upload

Drag and drop files to upload
(or click here)

Maximum file size is 5GB per file

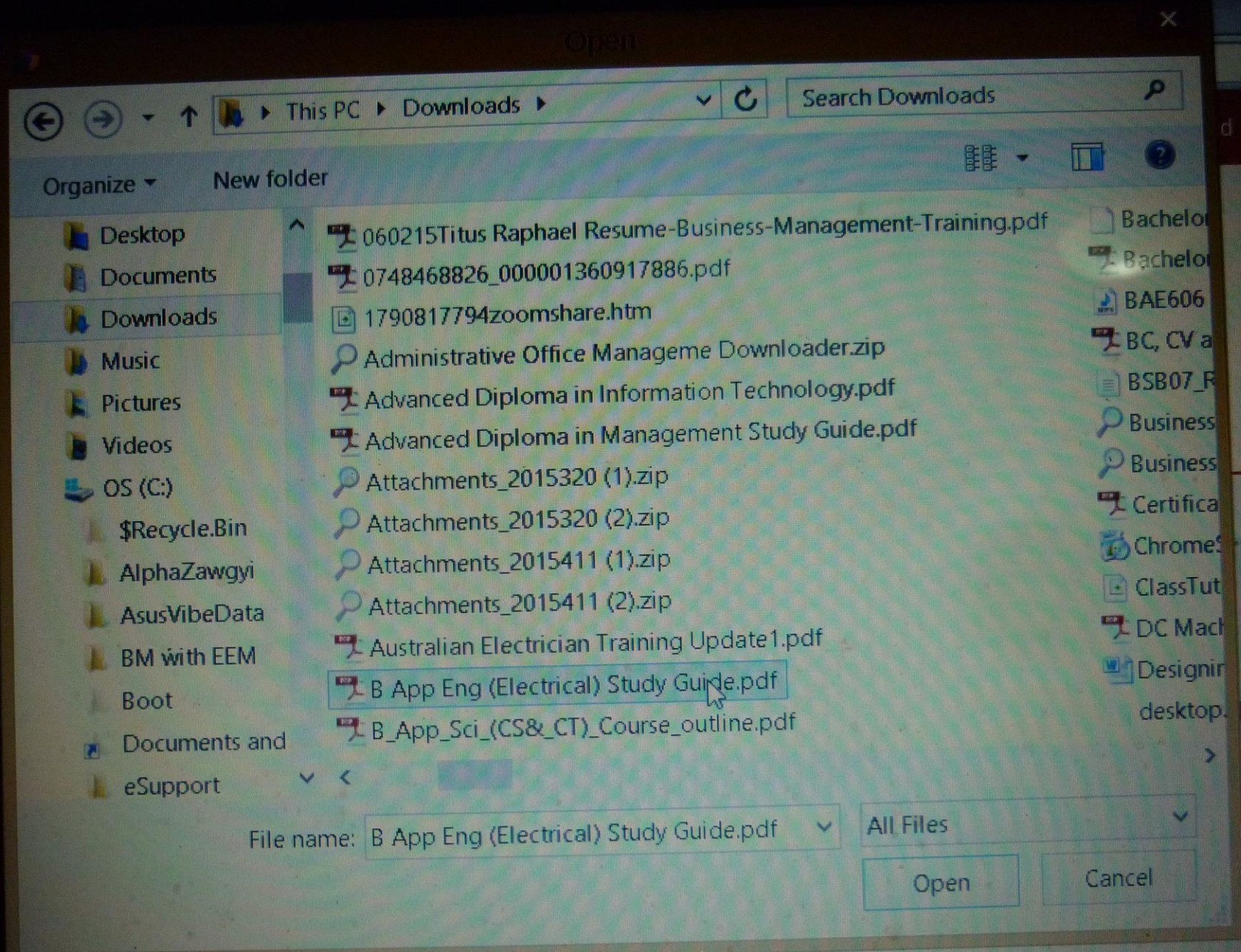

FileFactory

www.filefactory.com/upload/

Local Upload

Remote Upload

FTP Upload

Drag and drop files to upload
(or click here)

Maximum file size is 5GB per file

1.2 MIB

Cancel

Uploads Complete

Thanks for uploading! Your file is now available for download.

Make a selection below to access additional options

| <input type="checkbox"/> Filename | Size | Folder |
|---|---------|---------|
| <input type="checkbox"/> B App Eng (Electrical) Study Guide.pdf | 1.16 MB | Default |

Export Links ▼

Select Files Above to Export



Local Upload

Remote Upload

FTP Upload

Uploads Complete

Thanks for uploading! Your file is now available for download.

Make a selection below to access additional options

| <input type="checkbox"/> | Filename | Size | Folder |
|--------------------------|--|---------|---------|
| <input type="checkbox"/> | B App Eng (Electrical) Study Guide.pdf | 1.16 MB | Default |

Export Links

Select Files Above to Export



Uploads Complete

Thanks for uploading! Your file is now available for download.

Select Destination Folder

Default

Move to Folder

Email Selected



Filename

Size

Folder



B App Eng (Electrical) Study Guide.pdf

1.16 MB

Default

Export Links

Plain Text Links

<http://www.filefactory.com/file/1jx3e5sm9v7t/B%20App%20Eng%20%28Electrical%29%20Study%20Guide.pdf>

www.filefactory.com/upload/results.php?files=1jx3e5sm9v7t

Local Upload

Remote Upload

FTP Upload

Uploads Complete

Thanks for uploading! Your file is now available for download.

Select Destination Folder

Default

Move to Folder


Email Selected

| <input type="checkbox"/> | Filename | Size | Folder |
|-------------------------------------|--|---------|---------|
| <input checked="" type="checkbox"/> | B App Eng (Electrical) Study Guide.pdf | 1.16 MB | Default |

Export Links

Plain Text Links
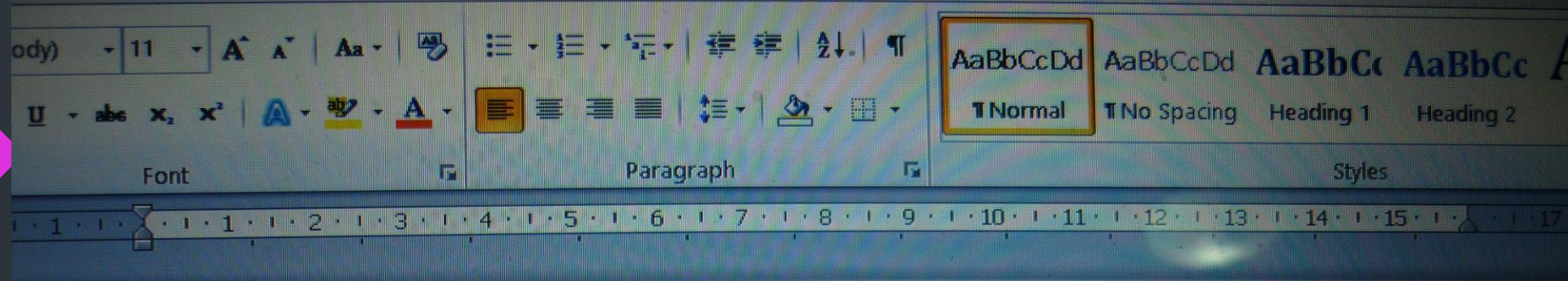
<http://www.filefactory.com/file/1jx3e5sm9v7t/B%20App%20Eng%20%28Electrical%29%20Study%20Guide.pdf>



<http://www.filefactory.com/file/1jx3e5sm9v7t/B%20App%20Eng%20%28Electrical%29%20Study%20Guide.pdf>



Use the link & then create the learning platform

Learning platform sample



Online Test Preparation

www.easytestmaker.com

**Free account is available upto limited
number of test**

http://www.easytestmaker.com/



EasyTestMaker



View Favorites Tools Help



The easy way to make and grade your tests!

Username

Log in

[Forgot username or password?](#)



EasyTestMaker is an online test generator to help you create, format and grade your tests!

Create, print and publish your tests online! **EasyTestMaker** makes it easy for you to perfectly format multiple question types, print alternate versions, and publish to the web for online tests!

It's Free!

Sign up now

Features Why you should use EasyTestMaker!

Perfectly formatted tests

Create multiple choice, fill-in-the-blank, matching, short answer and true or false questions. Add instructions and divide your test into multiple sections. [Learn more...](#)

Alternate versions helps reduce cheating

Alternate versions and answer sheets provided with no extra work. Questions and answer choices are automatically resorted in a different order. [Learn more...](#)

Online tests graded automatically

Published online tests are graded automatically. View and print student's results and override grading when necessary. **The same test you print, is the same test you can publish online!** [Learn more...](#)

Build exams with ease


Create an exam from your existing tests with just a few clicks. At any time you can copy a question from one

A+

EasyTestMaker is great! I save lots of time creating tests because all the formatting is done for me.



| Name | Folder |
|---|---------------------------------------|
| [blank] | Assign to folder... |
| 17794+UEE62211 Computer Programming+Computer Control+Network Strand Enrolment (1) | Students Information |
| 17794+UEE62211 Electronics+Telecommunication Unit Enrolment | Students Information |
| 17794+UEE62211 Power+Power Electronics+RE Strand Enrolment | Students Information |
| 17794+UEE62211 Power+Power Electronics+RE unit enrolment (1) | Students Information |
| 17908+UEE62111 Electronics + Telecommunication Unit Enrolment | Students Information |
| 17908+UEE62111 Power+Power Electronics+RE Enrolment 1 | Assign to folder... |
| 17908+UEE62111 Power+Power Electronics+RE Enrolment 2 | Students Information |
| 17908+UEE62111 Power+Power Electronics+RE Units Enrolment | Students Information |
| 17908+UEE62111 Power+Power Electronics+RE Units Enrolment (3) | Students Information |
| 17908+UEE62211 Computer Programming+Computer Control+Network Unit Enrolment | Students Information |
| DRIS 71A | 2012 Semester 2 Tests |
| E003+E004 Test 1 | Assign to folder... |
| E003+E004 Test 2 | Assign to folder... |
| E003+E004 Test 3 | Assign to folder... |
| E011+E017 Test | Assign to folder... |

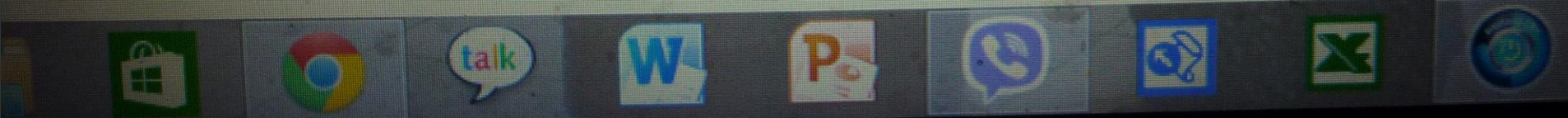

All tests Manage Folders Create new Test...

| Name | Folder |
|---|---------------------------------------|
| [blank] | Assign to folder... |
| 17794+UEE62211 Computer Programming+Computer Control+Network Strand Enrolment (1) | Students Information |
| 17794+UEE62211 Electronics+Telecommunication Unit Enrolment | Students Information |
| 17794+UEE62211 Power+Power Electronics+RE Strand Enrolment | Students Information |
| 17794+UEE62211 Power+Power Electronics+RE unit enrolment (1) | Students Information |
| 17908+UEE62111 Electronics + Telecommunication Unit Enrolment | Students Information |
| 17908+UEE62111 Power+Power Electronics+RE Enrolment 1 | Assign to folder... |
| 17908+UEE62111 Power+Power Electronics+RE Enrolment 2 | Students Information |
| 17908+UEE62111 Power+Power Electronics+RE Units Enrolment | Students Information |
| 17908+UEE62111 Power+Power Electronics+RE Units Enrolment (3) | Students Information |
| 17908+UEE62211 Computer Programming+Computer Control+Network Unit Enrolment | Students Information |
| DRIS 71A | 2012 Semester 2 Tests |
| E003+E004 Test 1 | Assign to folder... |
| E003+E004 Test 2 | Assign to folder... |
| E003+E004 Test 3 | Assign to folder... |
| E011+E017 Test | Assign to folder... |



G042-Transmission Lines Test—Semester 2-2012

Question Paper-Click [G042 Test Question Paper](#)

http://www.filefactory.com/file/12pcsbpgbkhx/n/G042_Online_Test_1_Question_pdf

Answer sheet- Click [G042 Test Answer Sheet](#)

<http://www.classroomclipboard.com/503511/Home/Test/047fd1ce1bc44929a6a97aefef738ac9#/InitializeTest.xaml>

First Name - TAFE-ID Number

Surname - Your full name

Access Code-- 2WKNN33

English (Australia)



G042 Online Test

Ref352

Circuit breaker is

| | | | |
|--------|--|---|---|
| A | To cut off the circuit when fault occurs | B | To cool the arc after disconnecting the circuit |
| C | To reclose the switch | D | All above |
| Answer | | | |

Ref354

Find the input impedance and VSWR of a transmission line 4.3λ long when $Z_0=100\Omega$ & $Z_L=200-j150\Omega$


| | | | |
|---|------------------------------|---|--------------------------------|
| A | $1+j2\ \Omega, 0.592\lambda$ | B | $2-j1.5\ \Omega, 0.592\lambda$ |
| C | $3+j4\ \Omega, 1.6\lambda$ | D | $3-j4\ \Omega, 3.6\lambda$ |

Find the input impedance and power of a transmission line 1.5λ long when $Z_L = 100 \Omega$ & $Z_0 = 200$

j150Ω

| | | | |
|--------|-----------------|---|-------------------|
| A | 1+j2 Ω, 0.592 λ | B | 2-j1.5 Ω, 0.592 λ |
| C | 3+j4 Ω, 1.6 λ | D | 3-j4 Ω, 3.6 λ |
| Answer | | | |

Ref356

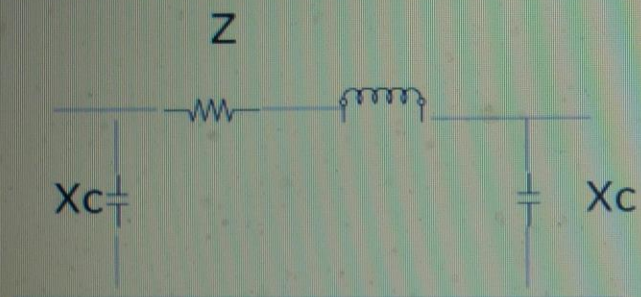

$$Z = 13 + j 92.6 \Omega, X_c = -j2700 \Omega$$

Find A, B, C, D constants

| | | | |
|--------|----------------------------------|---|--------------------------------------|
| A | A=1.8, B= 180, C =0.0007, D= 1.8 | B | A=2, B= 360, C =0.0012, D= 2 |
| C | A=3, B= 400, C =0.015, D= 5 | D | A=0.967, B= 93.5, C =0.0007, D=0.967 |
| Answer | | | |

Ref358

A 50Ω transmission line is connected to a load impedance $75+j60\Omega$. The forward wave voltage RMS value on line is 25V. Calculate

- Power delivered to resistive part of load impedance
- RMS current in impedance reflected wave voltage RMS size
- Peak voltage , forward and backward waves
- Voltage standing wave ratio (VSWR)
- Return loss in decibel

| | | | |
|--------|--|---|-----------------------------------|
| A | 12.5W, 0.101A, 35.6V, 16.57V, 2.764,4.4dB | B | 25W, 0.38A, 70V, 32V, 5.3,8.8dB |
| C | 5W, 0.39A, 70V, 16V, 3, 4dB | D | 25W, 0.38A, 40V, 32V, 2.764,4.4dB |
| Answer | | | |

FileFactory

→ http://www.filefactory.com/file/12pcsbpgbkhx/n/G042_Online_Test_1_Question_pdf

http://www.filefactory.com/file/12pcsbpgbkhx/n/G042_Online_Test_1_Question_pdf

http://www.filefactory.com/file/12pcsbpgbkhx/n/G042_Online_Test_1_Question_pdf - Google Search

You have successfully signed out

It is now safe to close your browser window. Alternatively, you can sign in again using the form below.





If you have an existing FileFactory account and have a support issue please [visit our support portal](#) or email support@filefactory.com.

Sign In

Facebook

Twitter








Google Plus

 1/Home/Test/047fd1ce1bc449479a6a97aefef738ac9#/InitializeTest.xml E

Web Search Suggestions

Searching...

Turn off suggestions (stop sending keystrokes to Web Search)



Add



your tests!

Create, print and publi
to perfectly format mu
the web for online test

You are about to take the following test:

G042 Test 1(2012 Semester 2)

First name

Last name

Access code

Start Test >>

System Requirements

Any of the following browsers and version or newer. IE 9, Firefox 12, Chrome 20, Opera 12, Safari 5.

You are about to take the following test:

G042 Test 1(2012 Semester 2)

First name

E046

Last name

Kyaw Naing

Access code

2WKNN33


×

Start Test >>

G042 Test 1(2012 Semester 2)

#1

[http://www.filefactory.com/file/12pcsbpgbkhx/n/G042_Online_Test_1_Question_pdf\(\)](http://www.filefactory.com/file/12pcsbpgbkhx/n/G042_Online_Test_1_Question_pdf())

- ☒ A
- ☐ B 
- ☐ C
- ☐ D

- ☒ A
- ☐ B
- ☐ C
- ☐ D

< Back

Next >



http://www.classroomclipboard.com/503511/Test/047FD1CE1BC44929/



Classroom Clipboard

File Edit View Favorites Tools Help

G042 Test 1(2012 Semester 2)

Review

| # | Status | |
|------|----------|-----------------------|
| # 1 | Answered | Go To |
| # 2 | Answered | Go To |
| # 3 | Answered | Go To |
| # 4 | Answered | Go To |
| # 5 | Answered | Go To |
| # 6 | Answered | Go To |
| # 7 | Answered | Go To |
| # 8 | Answered | Go To |
| # 9 | Answered | Go To |
| # 10 | Answered | Go To |
| # 11 | Answered | Go To |

Click "Finish" below to
complete your test!

Finish



Finish Test



Are you sure you want to complete your test?


Changes cannot be made once finished!

Finish Test

You have completed the following test:

G042 Test 1(2012 Semester 2)

Your results **1 / 11 pts. (9%)**

 [Download](#) your test results.

Download test results link expires after 30 minutes.

[Click here](#) to close this window.

[Click here](#) to return to test menu.






Online/ Off line simulated practical

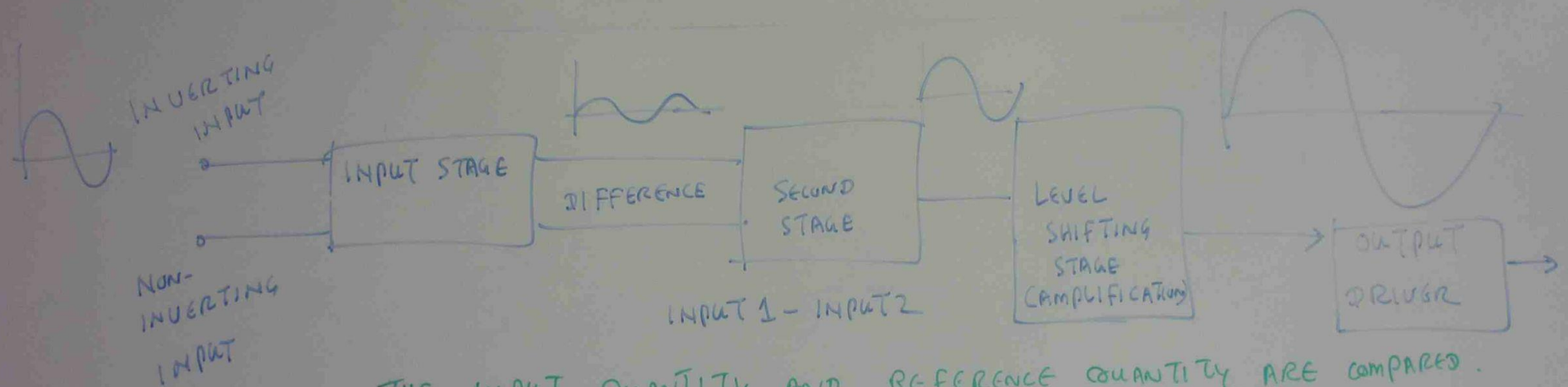
Part 1- Practical Photos

INTRODUCTION TO THE OPERATIONAL AMPLIFIER




THE INPUT QUANTITY AND REFERENCE QUANTITY ARE COMPARED. THE DIFFERENCE IS FED INTO THE SECOND STAGE, WHICH DOES THE AMPLIFICATION. THE VOLTAGE LEVEL IS THEN SHIFTED AND IS FED TO OUTPUT DRIVER STAGE WHICH DRIVES THE OUTPUT CONTROL CIRCUITS.

ph
DETER
OF G

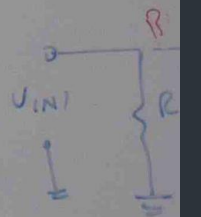

$$\begin{aligned}
 &= V_B - V_E \\
 &= 0 - 0.6 \\
 &= -0.6
 \end{aligned}$$

DRIVE SYSTEM

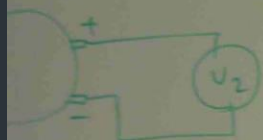


TER

1000
RPM

OR.

| VARIABLE RESISTOR | V_1 | V_2 | $RPM = V_2 \times \frac{1000}{50}$ | SPEED (slow or) fast |
|----------------------|-------|-------|------------------------------------|----------------------|
| Position (1) | | | | |
| Position (2) | | | | |
| Position (3) | | | | |
| Position (4) | | | | |

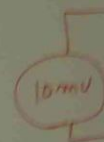
IF ELECTRONIC CIRCUIT CAN ONLY ACCEPT 10mV.
TO CONTROL THE MAXIMUM SPEED, FIND THE RATIO OF POTENTIAL DIVIDER



Electronic

| V_2 | $Rpm = V_2 \times \frac{1000}{50}$ | SPEED (SLOW OR) FAST |
|-------|------------------------------------|----------------------|
| | | |
| | | |
| | | |
| | | |
| | | |

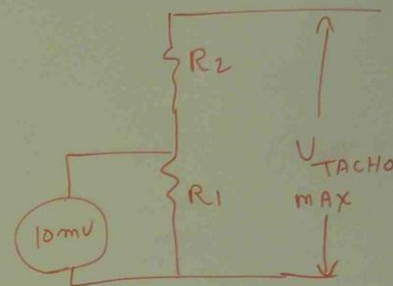ELECTRONIC CIRCUIT CAN ONLY ACCEPT 10mV.
 IF MAXIMUM SPEED, FIND THE RATIO OF POTENTIAL DIVIDER



$$V_{ELECTRONIC} = V_{TACHO MAX SPEED} \times \frac{R_1}{R_1 + R_2}$$

$$\therefore \frac{R_1}{R_1 + R_2} = \frac{V_{ELECTRONIC}}{V_{TACHO MAX}}$$

THEN FIND $\frac{R_1}{R_2}$

PRACT




SET TH


1x

0

EM



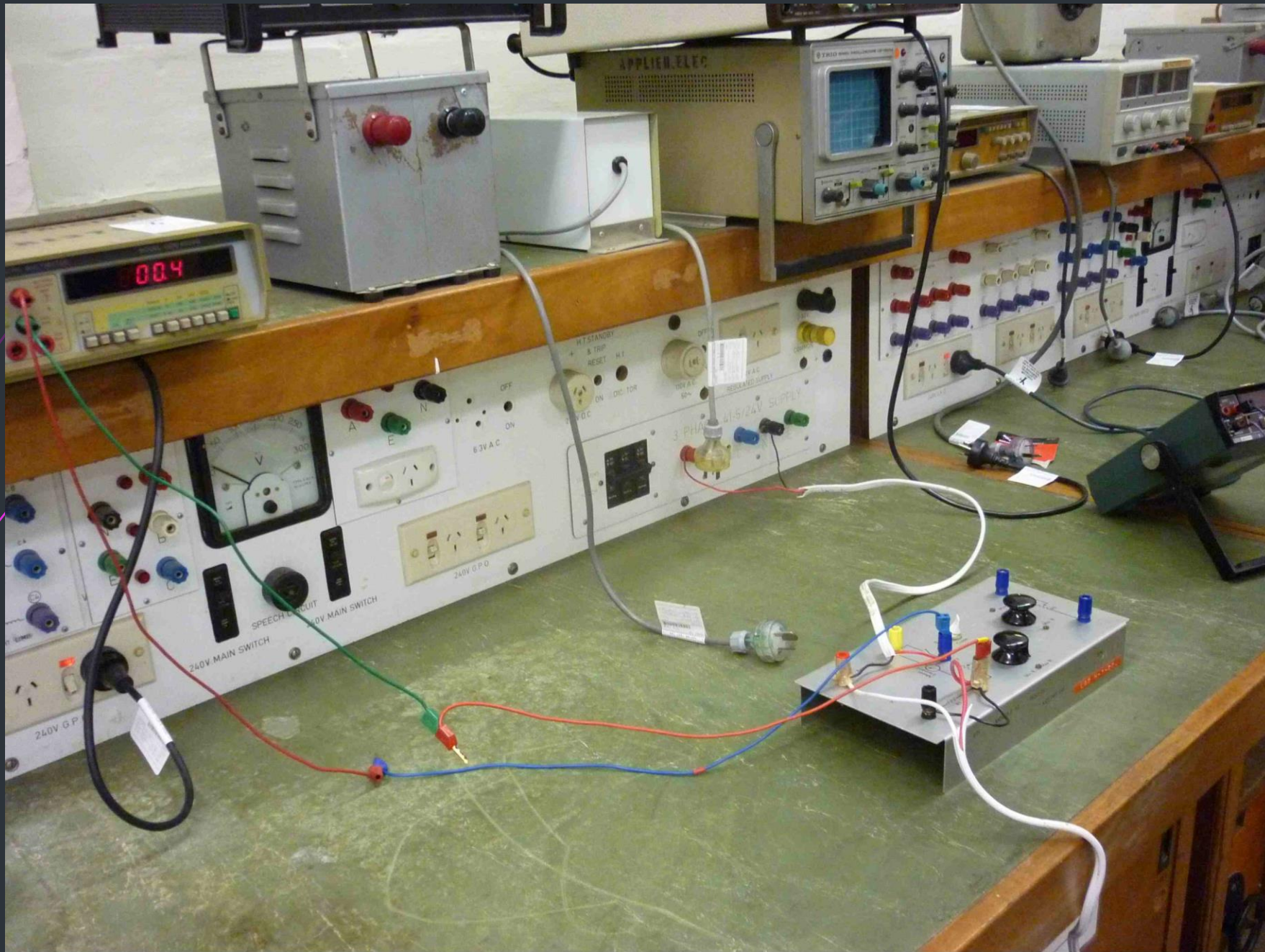


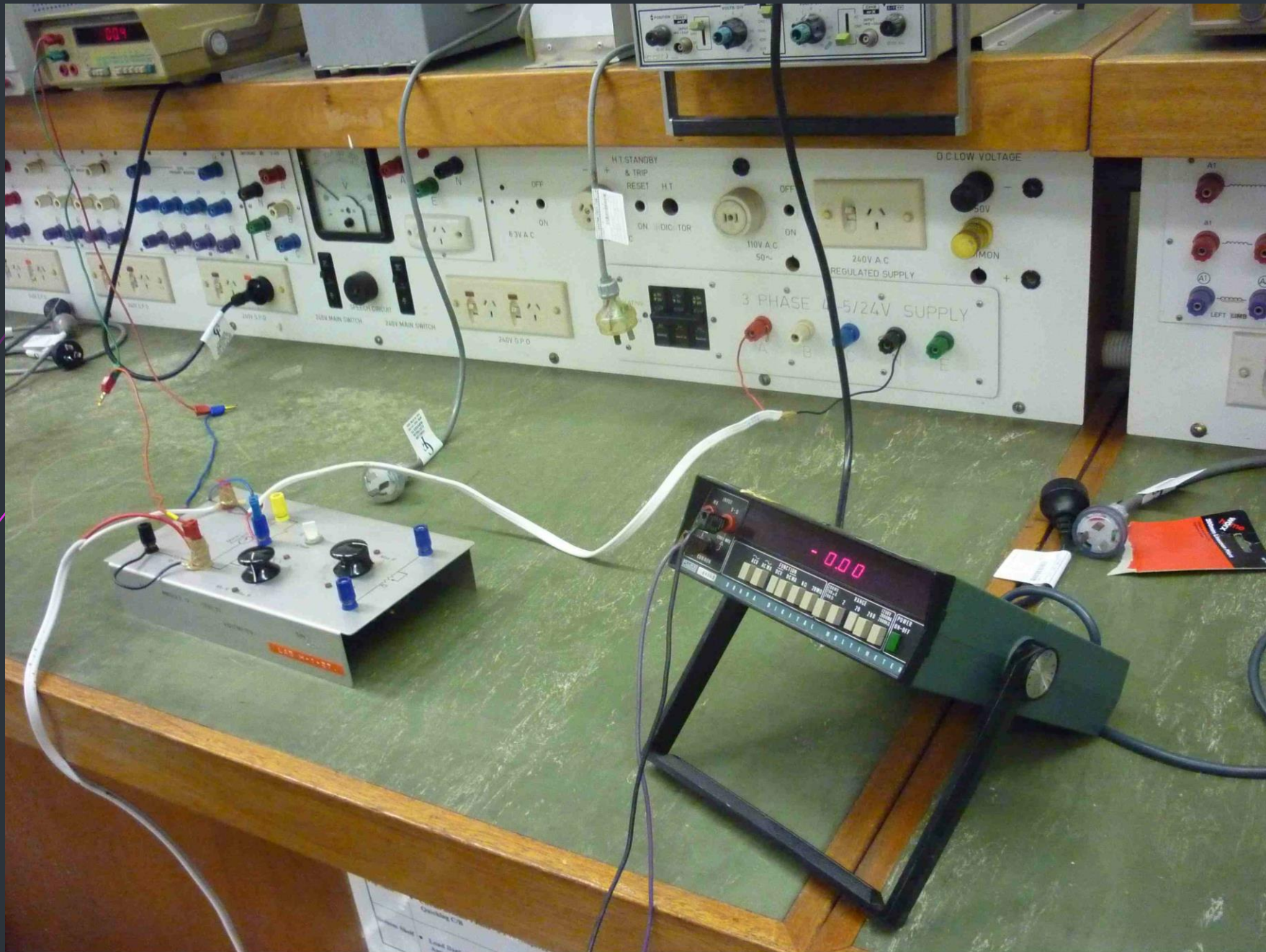



PRACTICAL (2)

AMPLIFIER GAIN

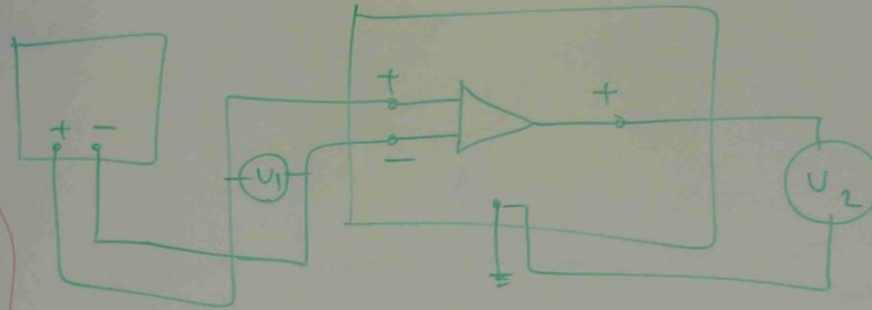

SET THE INPUT | OUTPUT VOLTAGE WITHOUT ADJUSTING

| GAIN | | | |
|---------------------|-------|-------|-------------------------------|
| INITIAL CONDITION | U_1 | U_2 | $AU = GAIN = \frac{U_2}{U_1}$ |
| GAIN ADJUSTMENT (1) | | | |
| GAIN ADJUSTMENT (2) | | | |
| GAIN ADJUSTMENT (3) | | | |


R_2
 U_{TACHO}
 MAX
 R_1


$$\times \frac{R_1}{R_1 + R_2}$$

U_{TACHO}
 MAX
 $U_{ELECTRONIC}$


$$= \frac{U_{TACHO}}{U_{ELECTRONIC}}$$

$$FIND \frac{R_1}{R_2}$$

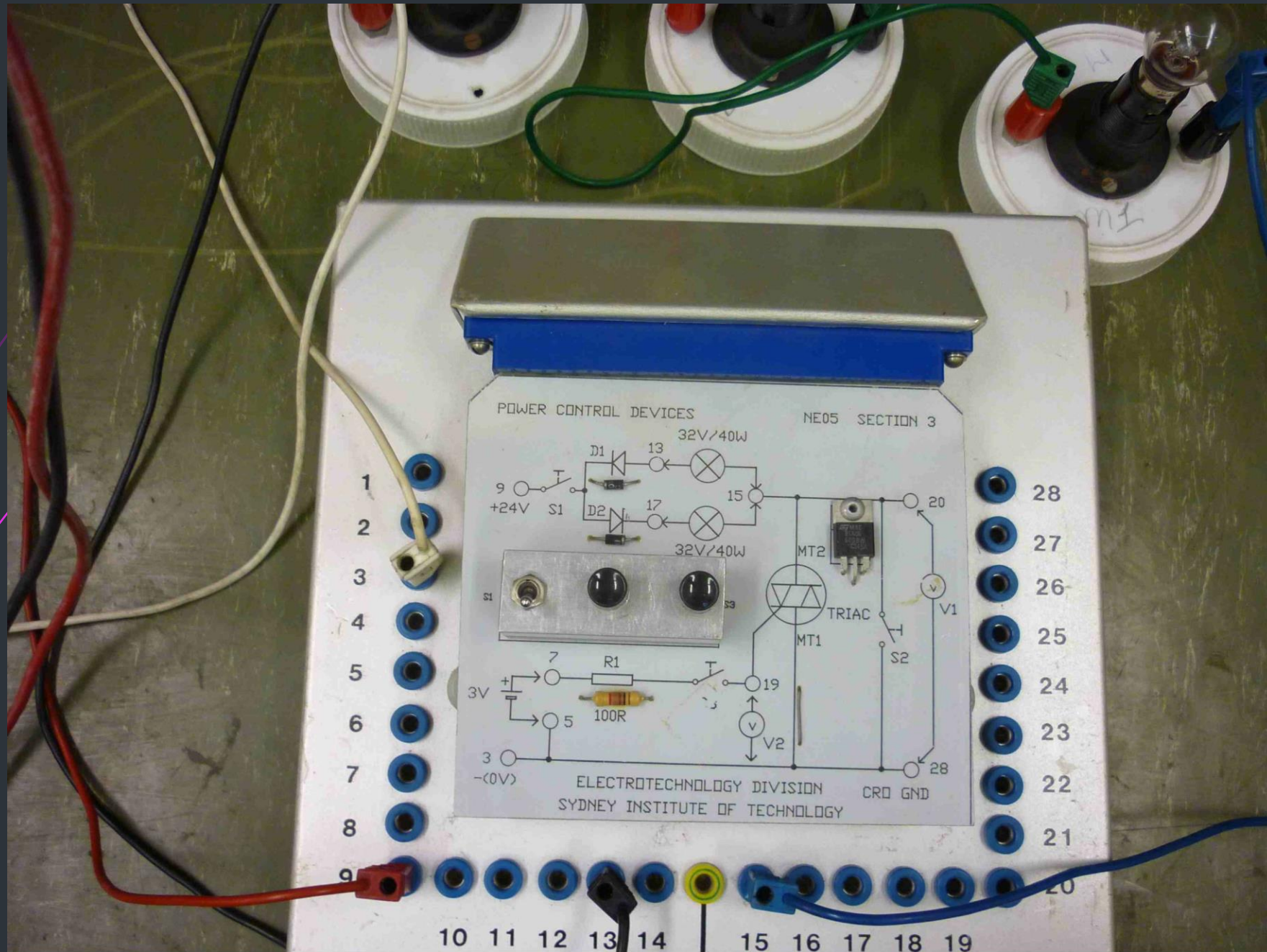


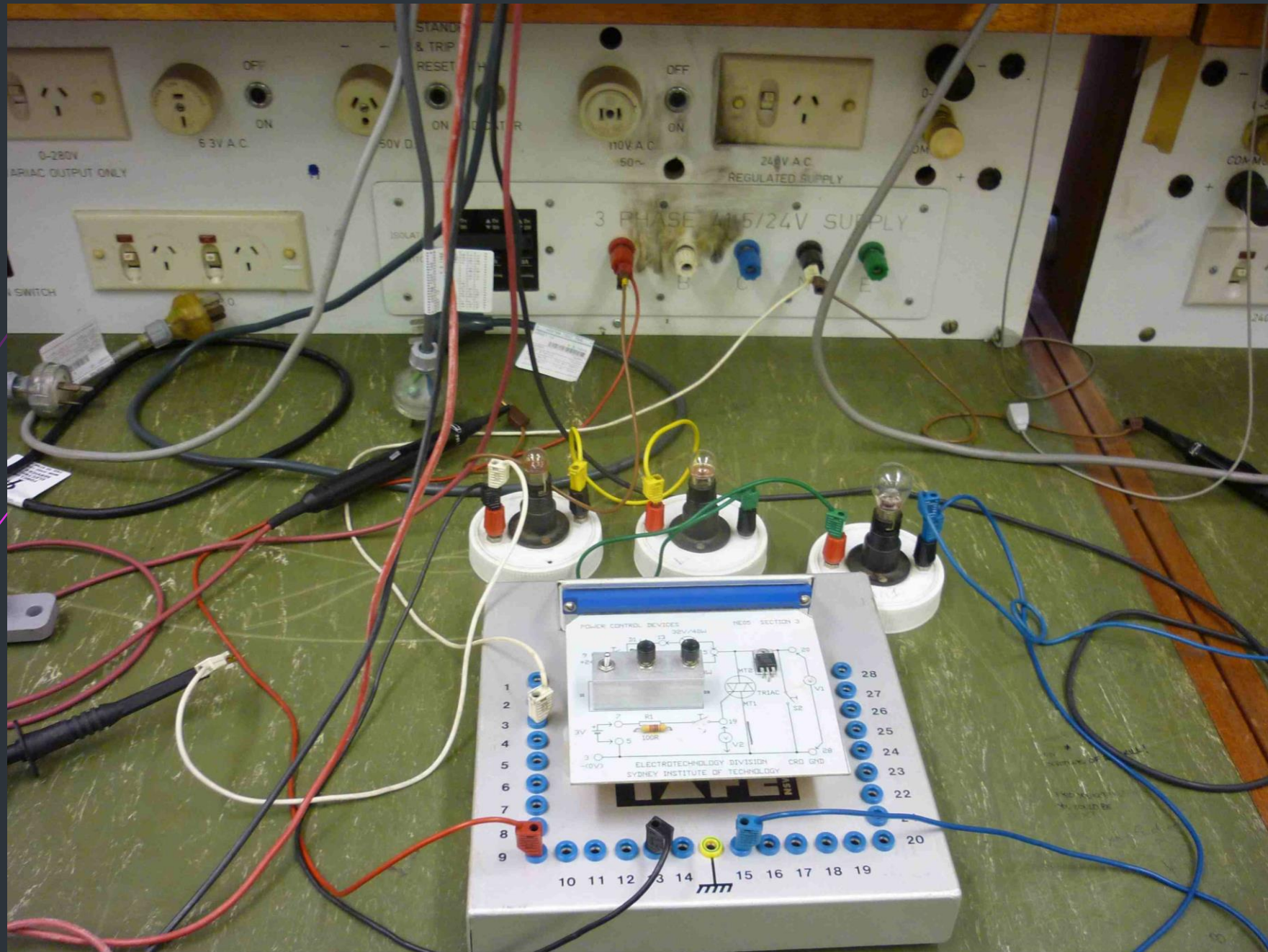





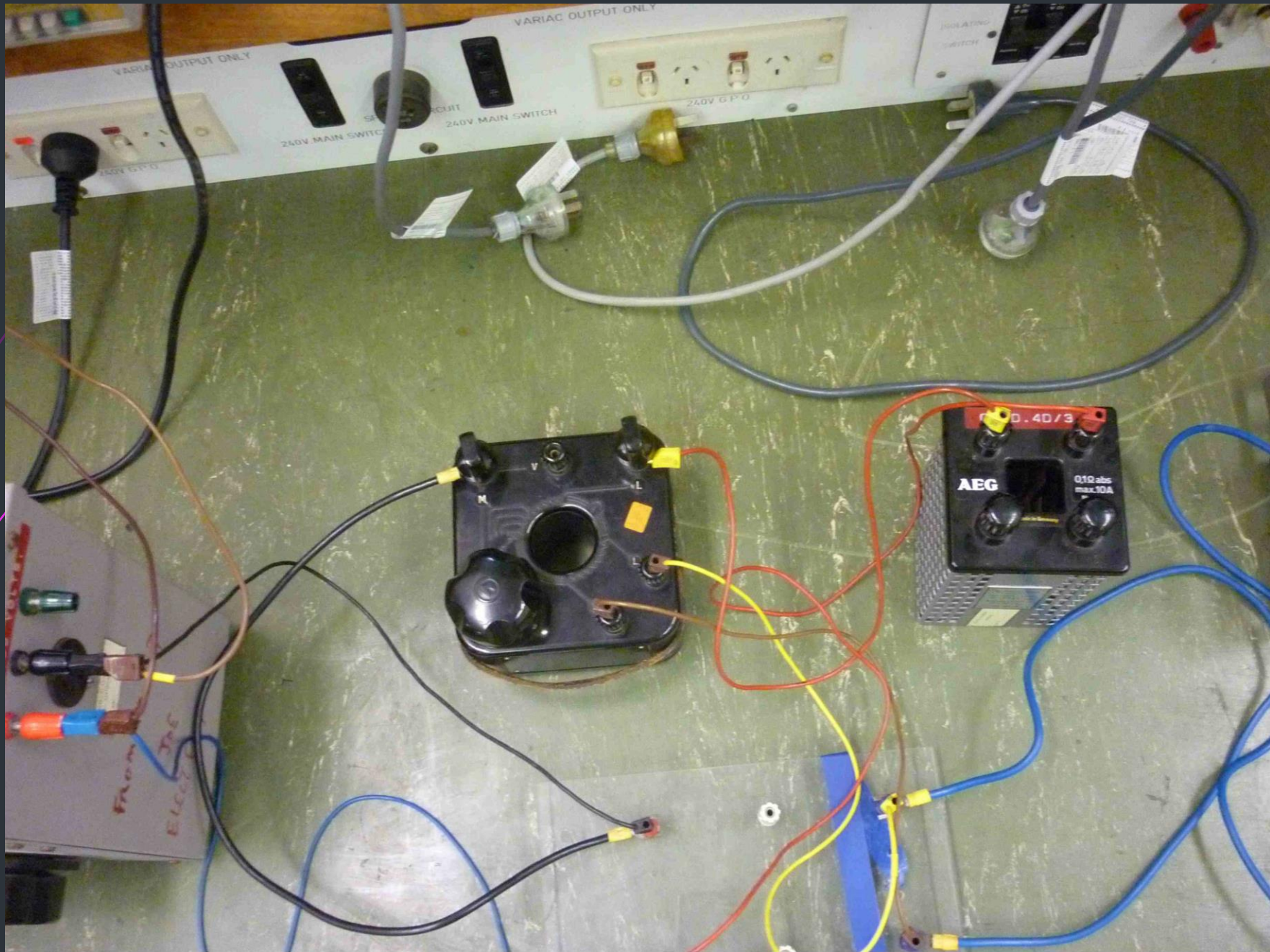




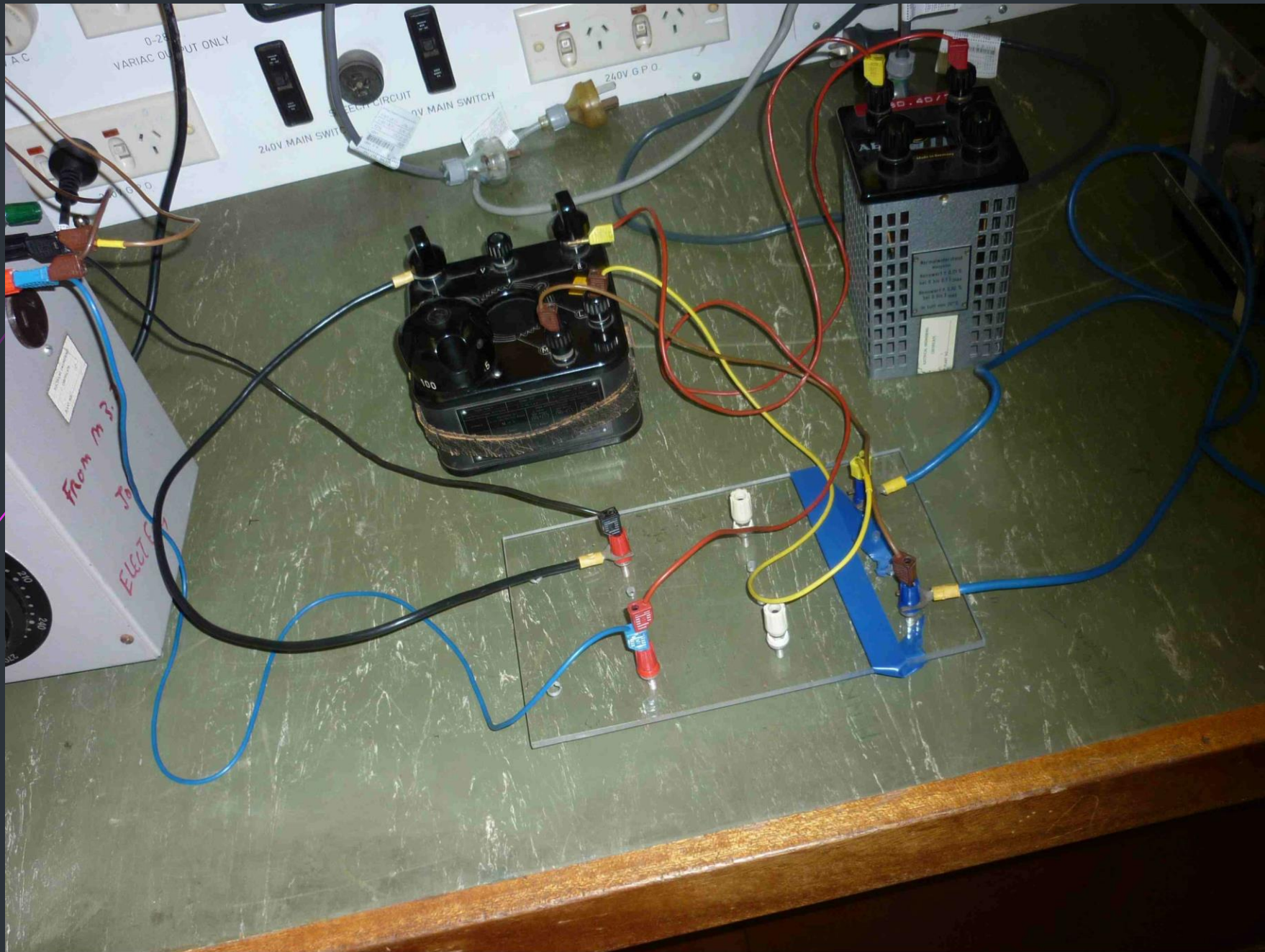

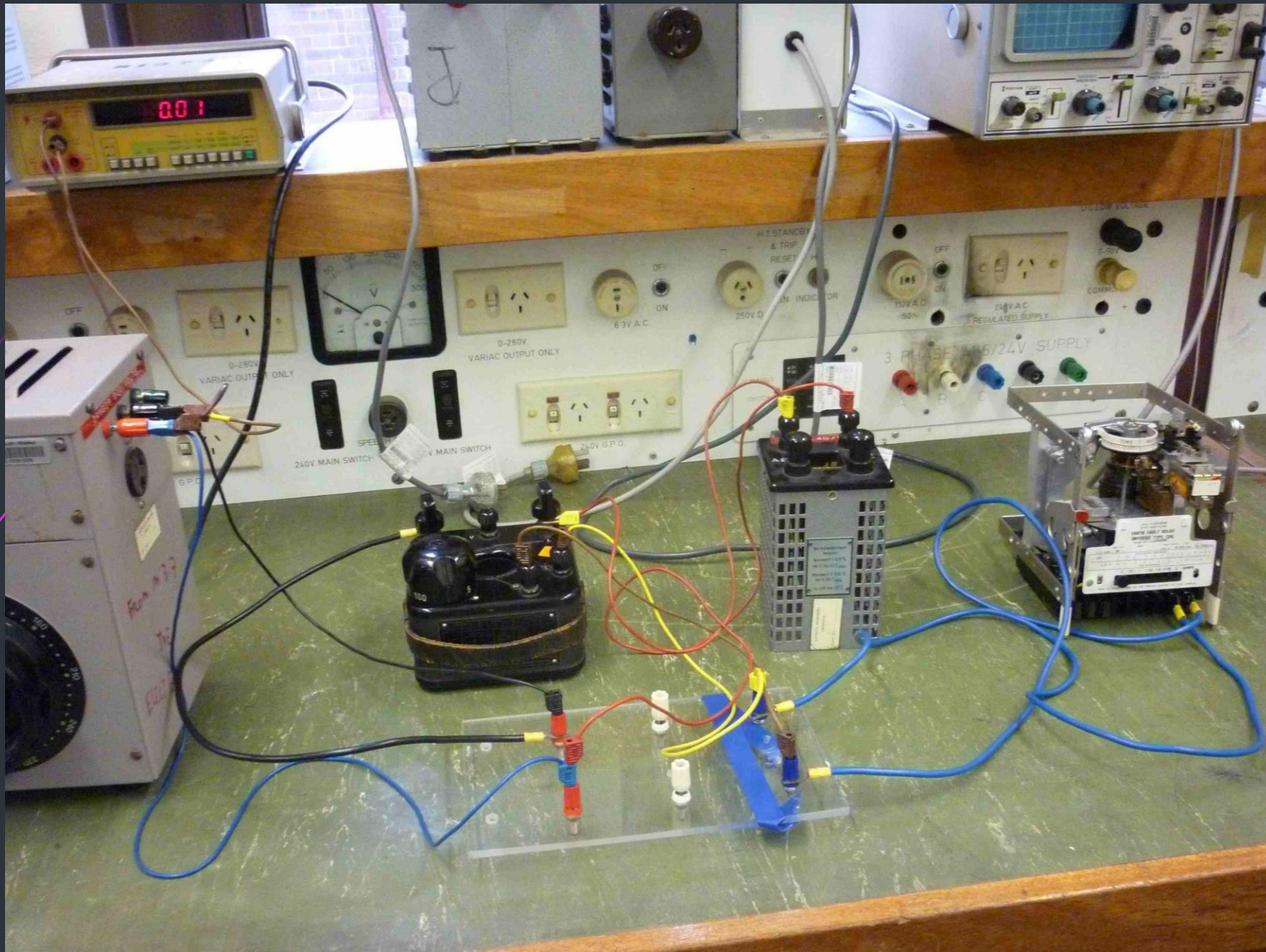

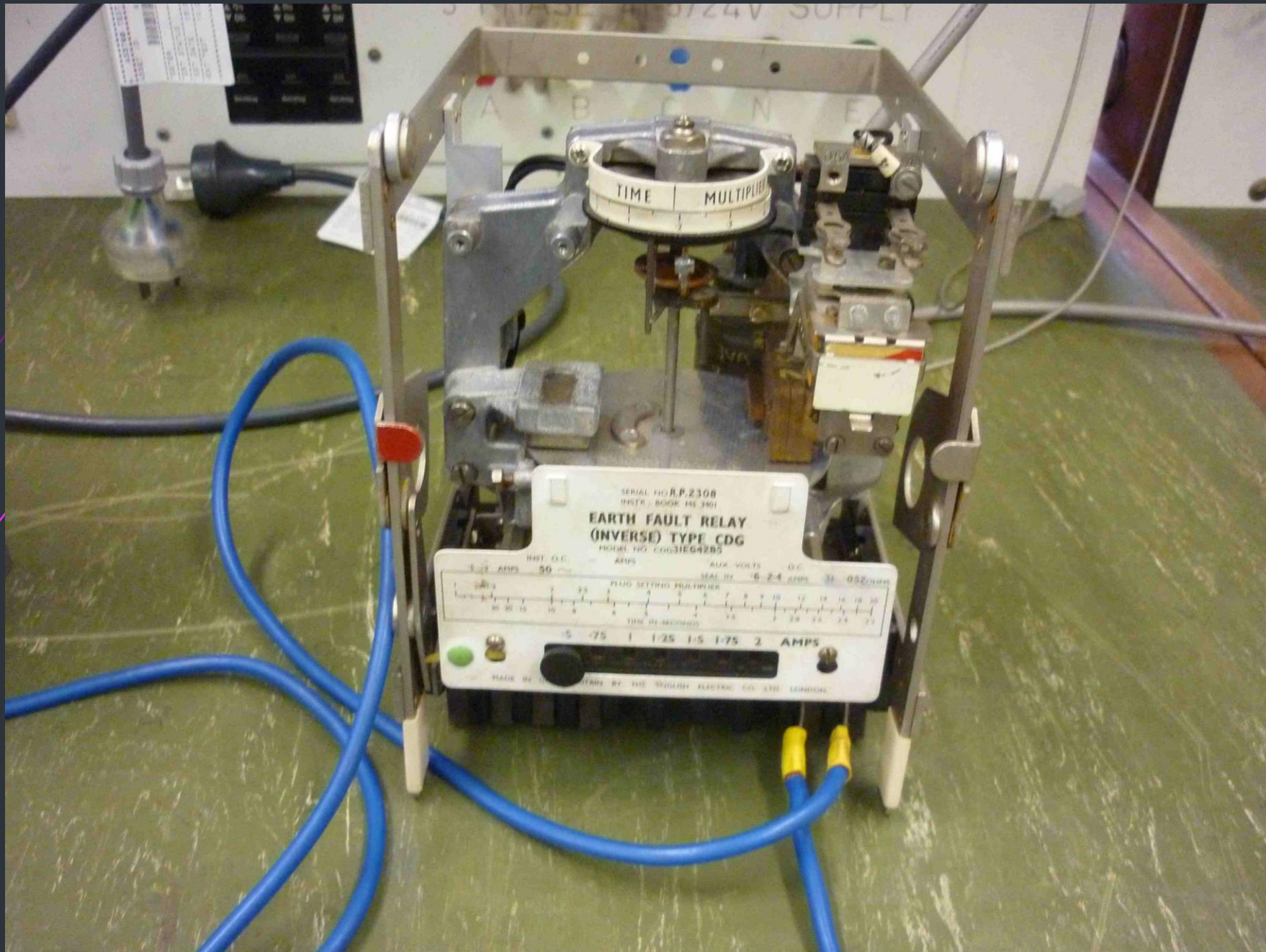



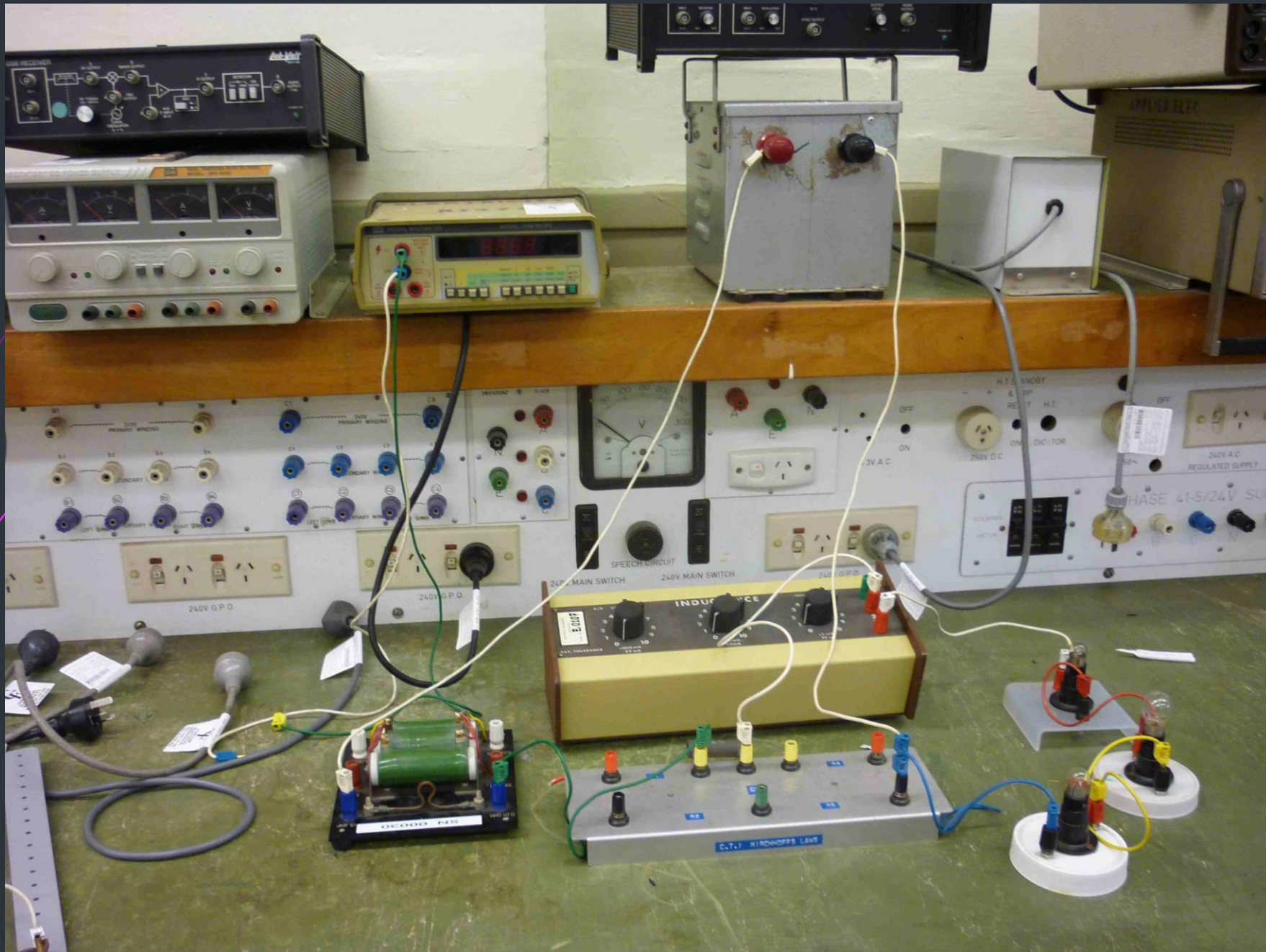



Engineering Practicals

www.highlightcomputer.com/practical.htm

Link


Basic Skill Training-Civil-Bricklaying



Production Operator Training-Electrical –Coil Manufacturing



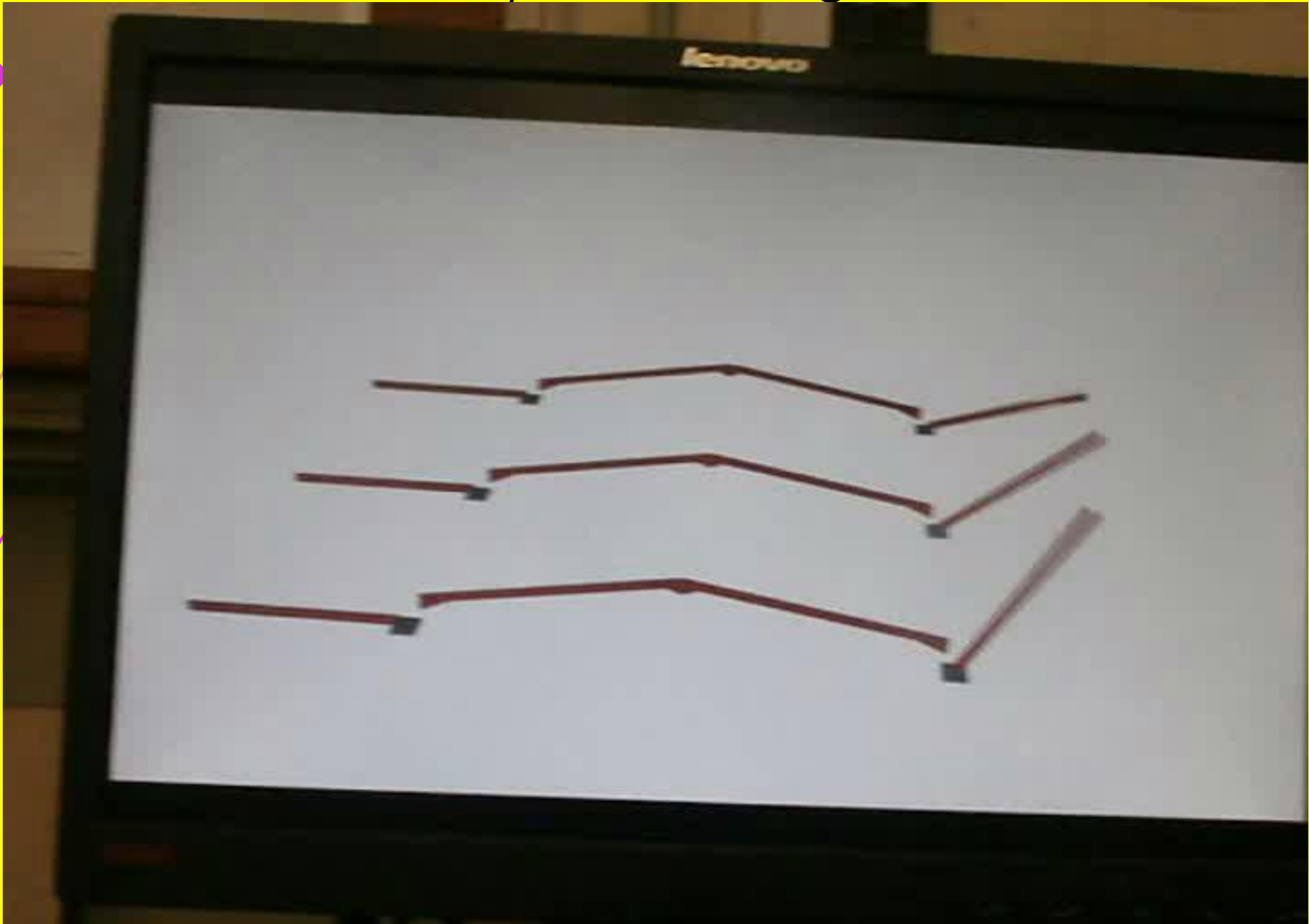
Overall construction system training-Civil Construction




Detailed Concept Training-Mechanical-Engine Assembly



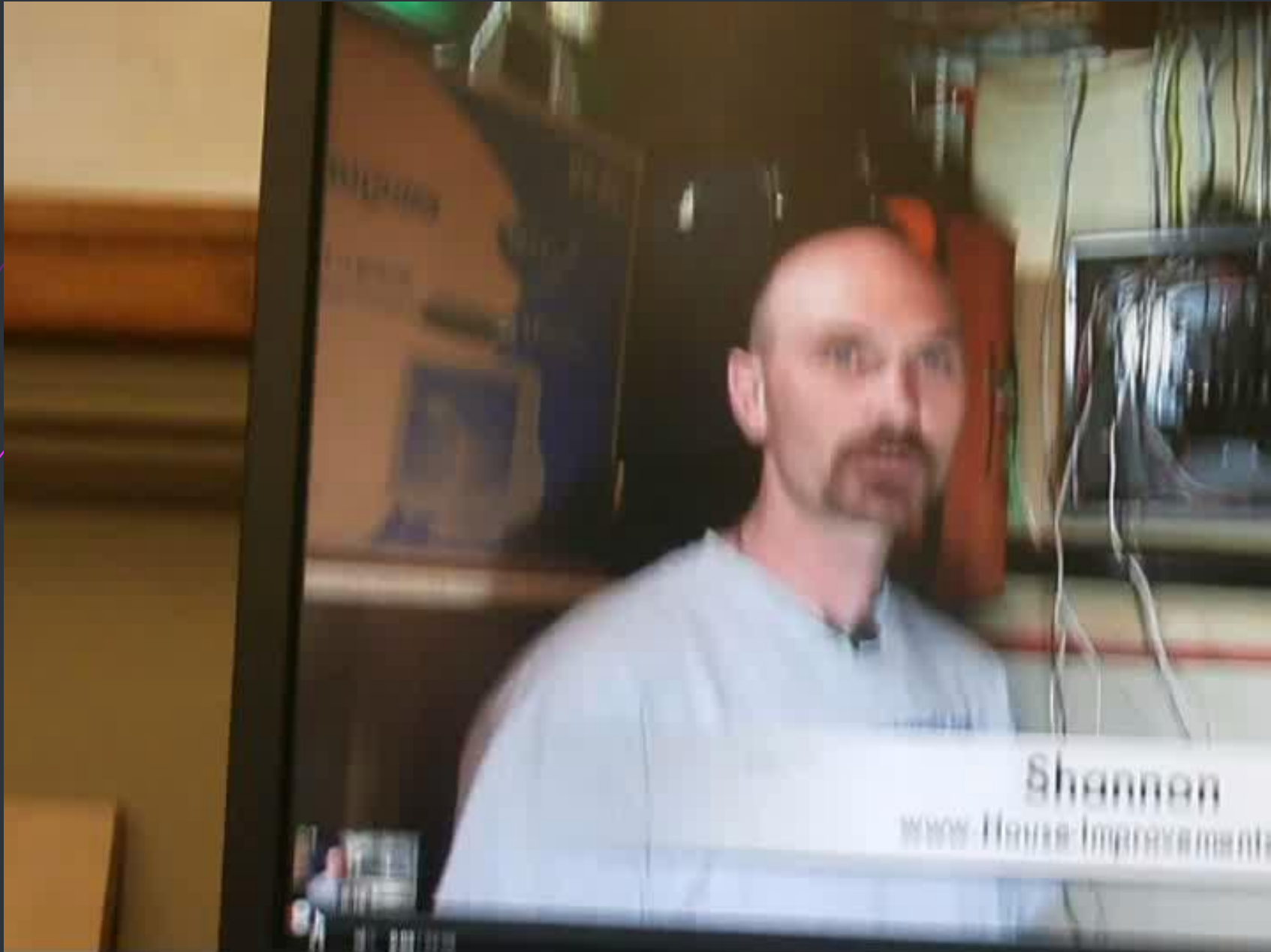Advanced Skills Training Electrical-Switchboard Installation



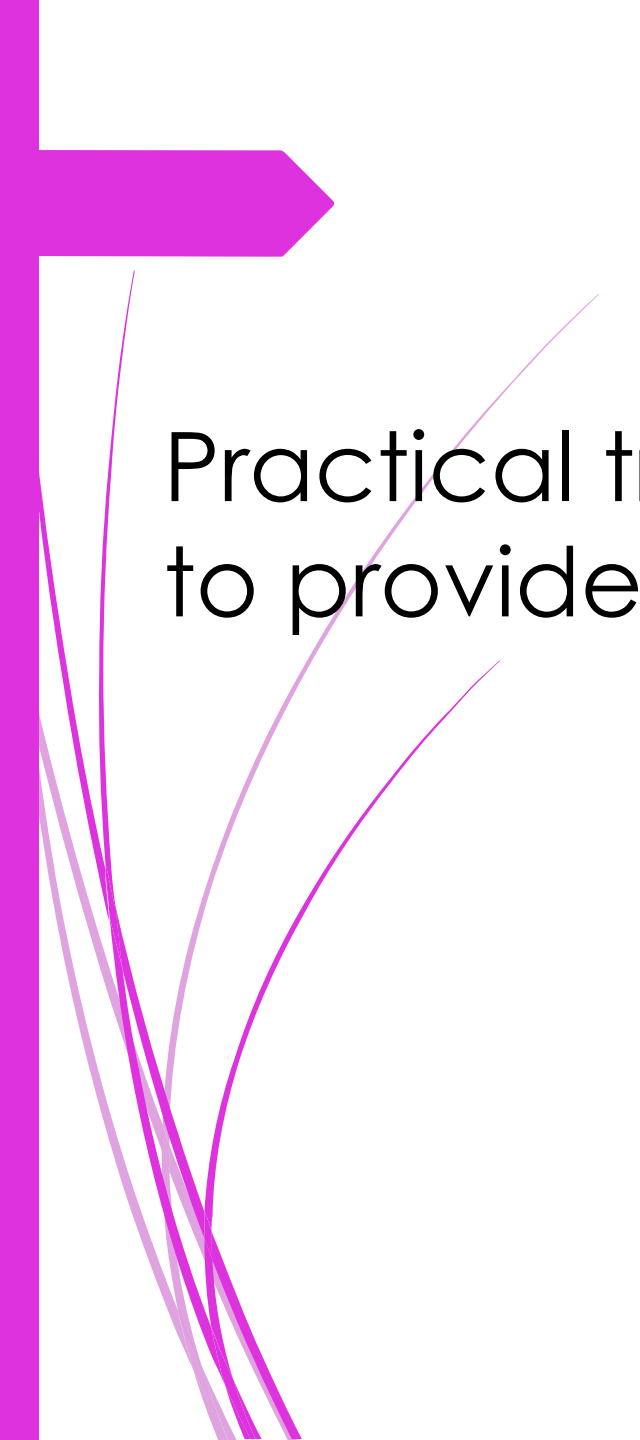A decorative graphic on the left side of the slide. It features a solid purple arrow pointing to the right, positioned at the top. Below the arrow, several thin, curved purple lines sweep upwards and to the right, creating a dynamic, abstract shape.

Practical training videos are to be developed
to provide the specific skills at the different levels



Learning Platform example

<http://www.highlightcomputer.com/onlineteaching1.htm>

Using multimedia & videos in teaching & Learning

<http://www.highlightcomputer.com/videos1.htm>

Using Youtube in teaching & learning

<http://www.highlightcomputer.com/videos2.htm>



Sample Course Construction & Learning System

[Link 1](#)

[Link 2](#)